



ECE 621

Signaling and Synchronization

Fall 2020

Topic 8

PLL & DLL Basics

Sameh A. Ibrahim
Ain Shams University
ICL


**(Courtesy of S. Pamarti & B. Razavi – UCLA and S. Palermo
– TAMU)**

Outline


- **PLL**
 - Components
 - Models
 - Noise Transfer Functions
 - Circuits
- **DLL**
 - Types
 - Models
 - Noise Transfer Functions
- **PLL/DLL comparison**



Introduction

 

PLL

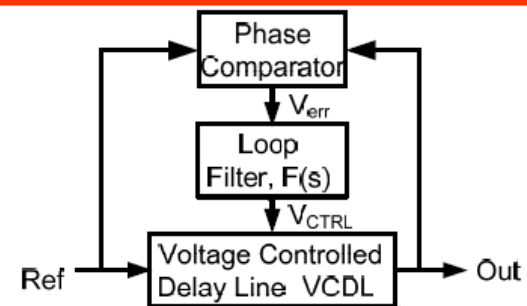

DLL

- **Negative Feedback Loop**
 - Generated clock
 - Same frequency and phase
- **PLLs applications**
 - Frequency synthesis
 - Skew cancellation
 - Clock recovery
 - Modulation/De-modulation
- **Negative Feedback Loop**
 - No clock generation
 - Defined phase relationship
- **DLLs applications**
 - Chip-to-chip communication
 - De-skew circuits



Loop Filter




- **Many implementations**
 - Passive, active, sampled
- **Filter classification**
 - Based on number of integrators in $F(s)$
 - Type I: no integrators
 - Type II: one integrator
 - Based on number of poles in $F(s)$
 - 1st order, 2nd order, 3rd order, etc.

$$\begin{aligned} \text{Type I: } F(s) &= 1, \quad F(s) = \frac{1 + s\tau_2}{1 + s\tau_1}, \\ \text{Type II: } F(s) &= \frac{1 + s\tau_2}{s}, \quad F(s) = \frac{1 + s\tau_2}{s(1 + s\tau_p)}. \end{aligned}$$



Voltage Control Oscillators

  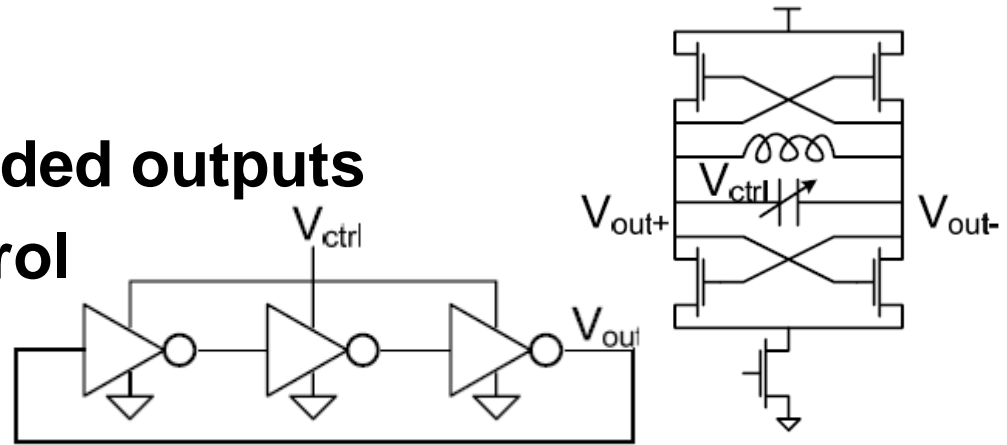
- Ring or LC oscillators
- Differential or single-ended outputs
- Voltage or current control



$$\omega_{VCO}(t) = K_{VCO} V_{ctrl}(t) \text{ rad/s},$$

$$\phi_{VCO}(t) = \int_{-\infty}^t K_{VCO} V_{ctrl}(\tau) d\tau \text{ radians}$$


Frequency Divider

 

- **Counts integer number of VCO cycles**
 - Synchronous or asynchronous implementations
- **Many implementations**
 - Static CMOS, dynamic logic, current mode logic (CML)

$$\phi_{div}(t) = \frac{1}{N} \phi_{vco}(t)$$


Phase Comparator / Detector

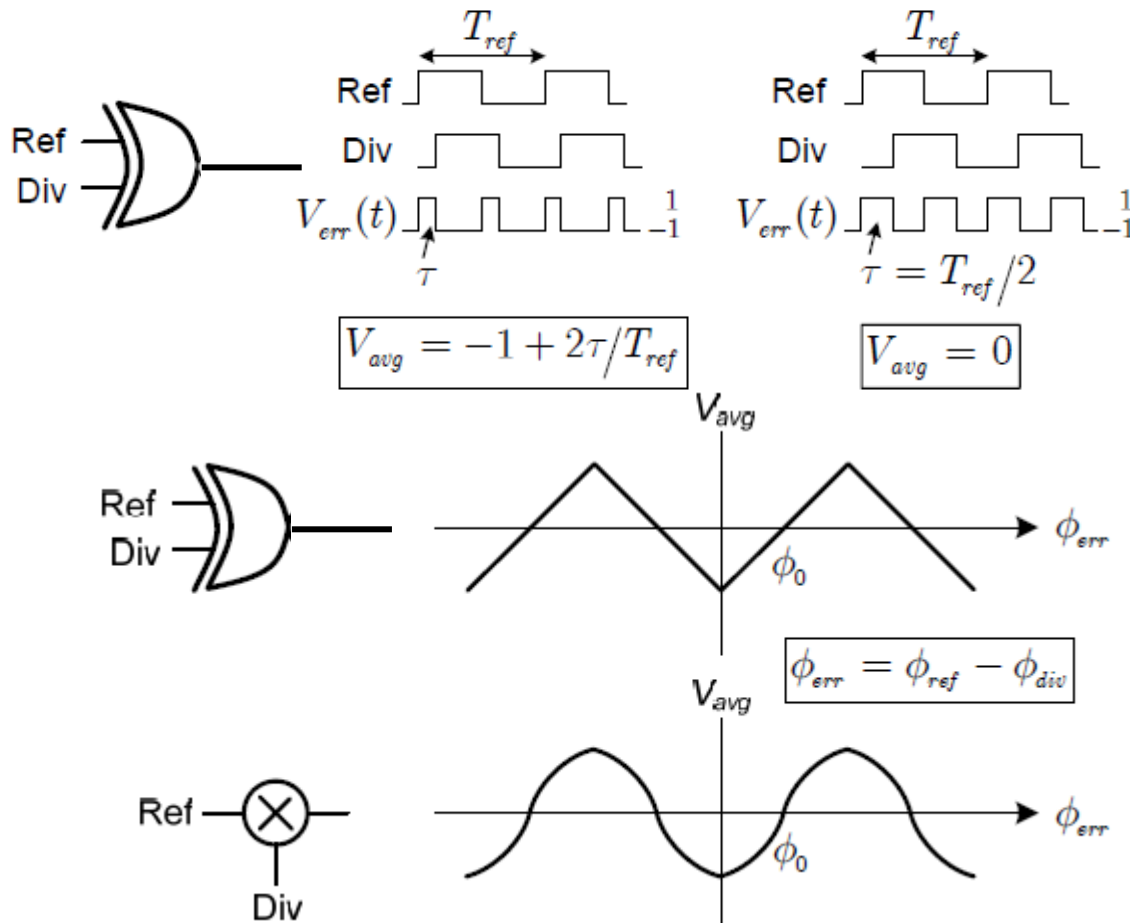

- Can assume that in the linear region, on average,

$$V_{avg}(t) \approx K_{PD} (\phi_{ref}(t) - \phi_{div}(t) - \phi_0)$$



Intuitive PLL Model

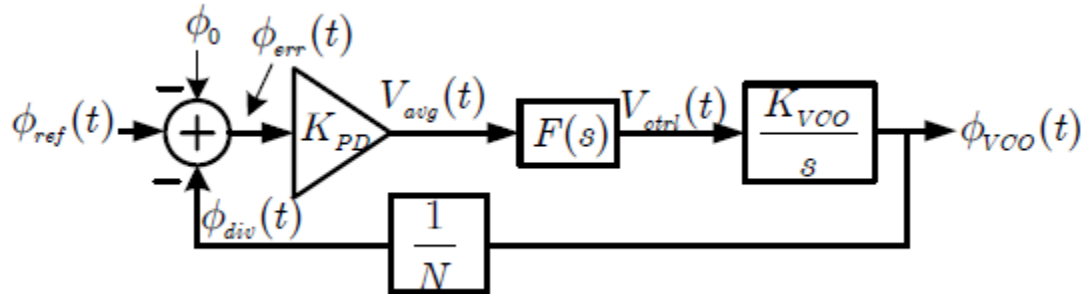


- **Negative feedback loop tries to force $\Phi_{err}(t) = \Phi_0$**
 - In steady state i.e. in “lock” $f_{VCO} = N \cdot f_{ref}$
- **The continuous time, analog model is in general incorrect**
 - Many components have discrete time operation.
 - However, important conclusions can be drawn from it.

Understanding PLL Frequency Response

- Linear “small-signal” analysis is useful for understanding PLL dynamics if
 - PLL is locked (or near lock).
 - Input phase deviation amplitude is small enough to maintain operation in lock range.
- Frequency domain analysis can tell us how well the PLL tracks the input phase as it changes at a certain frequency.
- PLL transfer function is different depending on which point in the loop the output is responding to.

 
 


Phase Frequency Detector

 


- “Up” and “Dn” together contain the phase error information.
 - Their time difference is proportional to the phase error.
- A proportional voltage or current can be generated for $F(s)$.
 - A charge pump is best suited for this purpose.

Charge Pump Integer-N PLLs

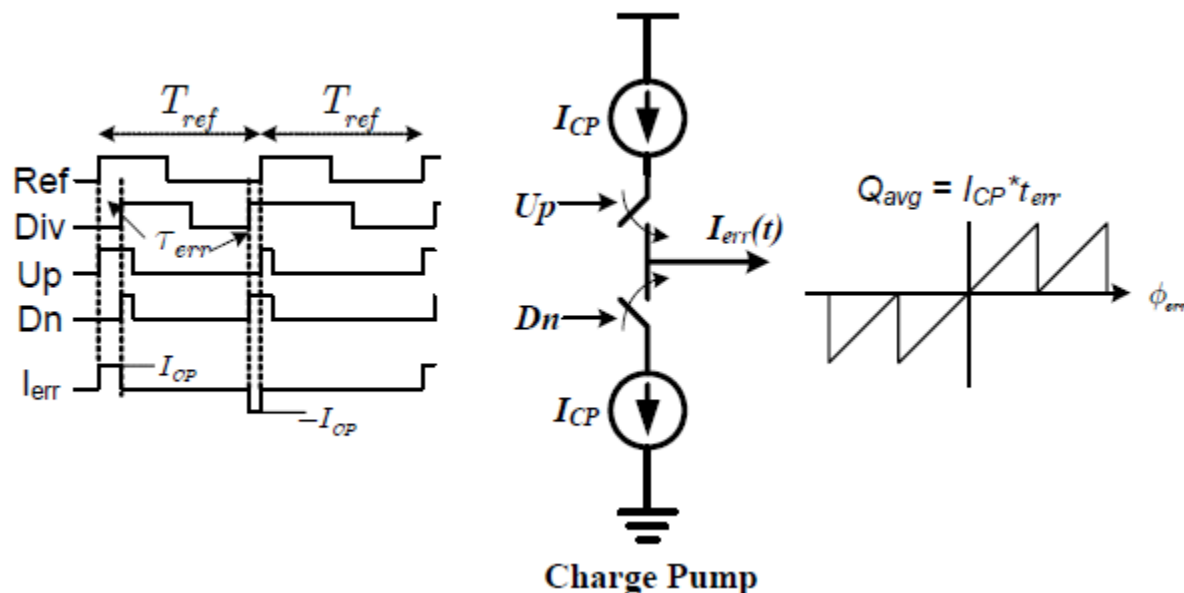 


- PFD + CP together dump charge, Q_{avg} proportional to Φ_{err} into the loop filter, during each reference period.

Charge Pump Integer-N PLLs: LTI Model

 


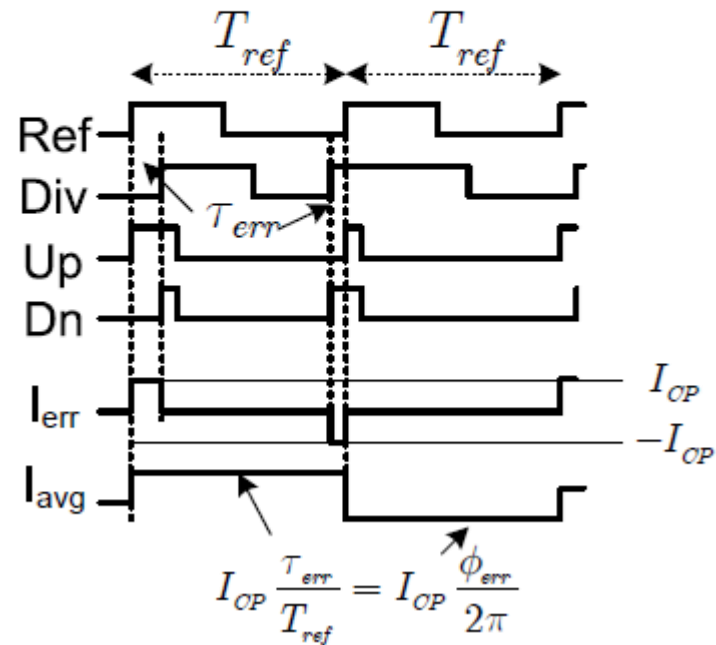Assumption: CP produces an average current during each reference period.




- **Linear, time-invariant model**
 - Ignores the non-linearity of the PFD
 - Ignores position and width of current pulses
 - Reasonable approximation for low bandwidth PLLs

Common Charge Pump Integer-N PLLs

 


- Loop filter is usually of Type II.

 

$$F(s) = R \left(\frac{1 + s\tau_2}{s\tau_2} \right)$$


$$\tau_2 \triangleq RC_2,$$

 

$$F(s) = R \left(\frac{b-1}{b} \right) \left(\frac{1 + s\tau_2}{s\tau_2(1 + s\tau_p)} \right)$$

$$b \triangleq 1 + \frac{C_2}{C_1}, \quad \tau_p \triangleq R \frac{C_1 C_2}{C_1 + C_2} = \frac{\tau_2}{b}$$

Stability (1)

 


$$T(s) = \frac{K(1 + s\tau_2)}{s^2\tau_2(1 + s\tau_p)}$$

$$K = \left(\frac{b-1}{b}\right) \frac{I_{CP}K_{VCO}R}{2\pi N}$$

$$PM \approx \tan^{-1}(K\tau_2) - \tan^{-1}(K\tau_2/b)$$



Stability (2)

 


$$T(s) = \frac{K(1 + s\tau_2)}{s^2\tau_2(1 + s\tau_p)}$$

$$K = \left(\frac{b-1}{b}\right) \frac{I_{CP}K_{VCO}R}{2\pi N}$$

$$PM \approx \tan^{-1}(K\tau_2) - \tan^{-1}(K\tau_2/b)$$

- **Two poles at $s=0$ cause instability**
 - The zero provides phase margin (PM).
 - Large $K\tau_2$ values give better PM.

Stability (3)

 


$$T(s) = \frac{K(1 + s\tau_2)}{s^2\tau_2(1 + s\tau_p)}$$

$$K = \left(\frac{b-1}{b}\right) \frac{I_{CP}K_{VCO}R}{2\pi N}$$

$$PM \approx \tan^{-1}(K\tau_2) - \tan^{-1}(K\tau_2/b)$$

- Large “b” gives better PM: typically, $b > 16$ is used

Closed Loop Response (1)

 


$$A_\phi(s) = \frac{N(1 + s\tau_2)}{1 + s\tau_2 + s^2\tau_2/K + s^3\tau_2\tau_p/K},$$

where $K = \left(\frac{b-1}{b}\right) \frac{I_{CP}K_{VCO}R}{2\pi N},$

- **A pole-zero doublet exists at the zero location.**
 - Magnitude response of $A_\phi(s)$ rises at the doublet.
 - Doublet slows down settling response.

Closed Loop Response (2)

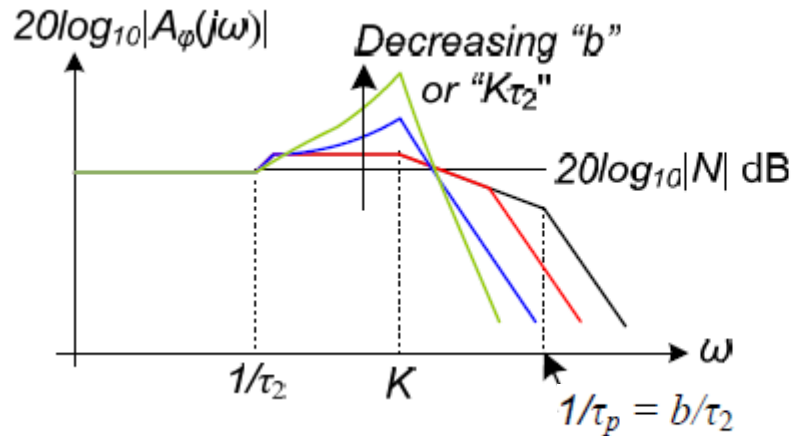

$$A_\phi(s) = \frac{N(1 + s\tau_2)}{1 + s\tau_2 + s^2\tau_2/K + s^3\tau_2\tau_p/K},$$

where $K = \left(\frac{b-1}{b}\right) \frac{I_{CP}K_{VCO}R}{2\pi N},$

- **A pole-zero doublet exists at the zero location.**
 - Magnitude response of $A_\phi(s)$ rises at the doublet.
 - Doublet slows down settling response.
- **Decreasing "b" or " $K\tau_2$ " increases peaking.**
 - Frequency where peaking occurs is not necessarily K.



Simple Design Procedure

- **Given quantities**

- F_{ref} , N , K_{VCO} (Hz/V), minimum phase margin, PM_{required}
- Required closed loop bandwidth, f_{BW} (Hz)

- **Calculate b**

$$PM_{\text{required}} \leq \tan^{-1} \left(\frac{\sqrt{b} - 1/\sqrt{b}}{2} \right)$$

- **Calculate I_{CP} , R , C_2 such that**

$$I_{\text{CP}}R = \left(\frac{b}{b-1} \right) \frac{2\pi N f_{\text{BW}}}{K_{\text{VCO}}} \quad \text{and} \quad RC_2 = \frac{\sqrt{b}}{2\pi f_{\text{BW}}}$$

- **Calculate C_1 such that** $C_1 = \frac{C_2}{b-1}$

- **Note: Multiple choices for (I_{CP}, R, C_2) are possible**

- Thermal noise, power considerations will help in making the choice





Design Issues


- **Sophisticated filter design is possible.**
 - Implementation concerns
 - Not much room to play with
- **Several tools available**
 - Mainly choose the components of a chosen filter structure,
 - Good example: Michael Perrott's PLL Design tool
- **The challenging problems in PLL design are usually elsewhere**
 - Dealing with component variability
 - How much phase margin is enough phase margin ?



2nd Order vs. 3rd Order Type II CP PLL

  

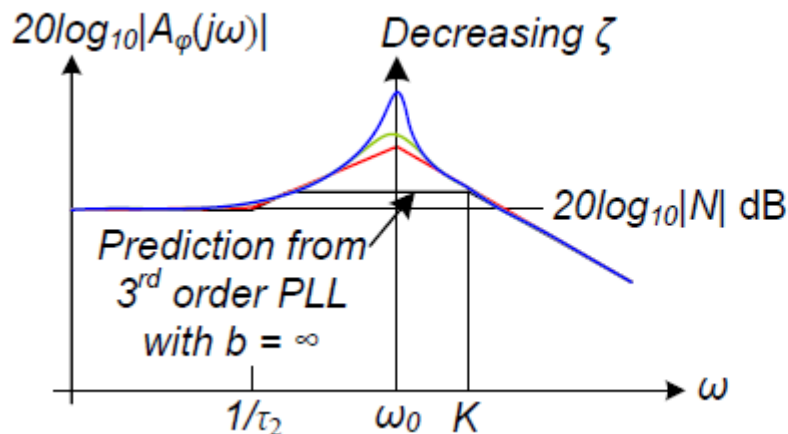- 2nd order PLL is a special case of the 3rd order PLL.
 - $b = \text{infinity}$
- However, analysis has been application specific
 - Digital, wired communication analyses focus on 2nd order PLL




$$PM = \tan^{-1}(K\tau_2)$$

$$A_\phi(s) = \frac{N(1 + 2\zeta s/\omega_0)}{1 + 2\zeta s/\omega_0 + s^2/\omega_0^2}$$


where $\omega_0 = \sqrt{\frac{1}{2\pi N} \frac{I_{OP} K_{VCO}}{C_2}}$, $\zeta = \frac{1}{2} \omega_0 R C_2$

Control Voltage Ripple

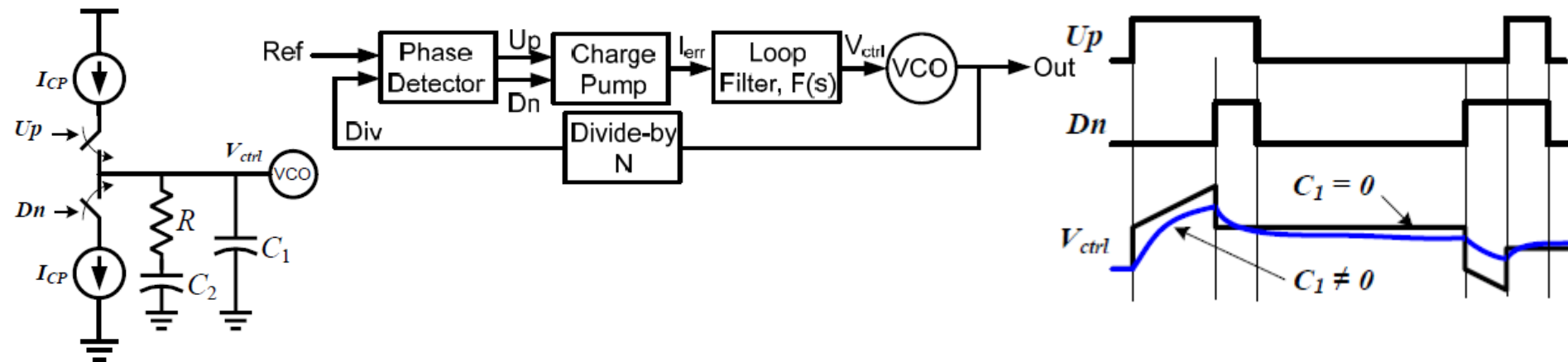

- The “ripple” on V_{ctrl} causes periodic jumps in VCO phase
 - Causes spikes in power spectral density of VCO output
 - Bad for both wireless and wire-line communications
- 3rd pole attenuates the ripple and its effects
 - Small “b” is desired for more attenuation
 - Recall: small “b” reduces phase margin
- Often choose K to be the geometric mean of $1/\tau_2$, and $1/\tau_p$
 - Used this in the design procedure mentioned earlier

Effect of Feedback Delay in PLLs

 


- **Non-zero delay in the feedback is common in PLLs.**
 - E.g., clock distribution in chip-to-chip I/O
- **Feedback delay degrades the phase margin of the PLL.**
- **Can be shown that**

$$PM \approx PM_{t_d=0} - f_{BW} t_d \times 360^\circ$$

- Assuming $K \approx f_{BW}$




Noise in the PLL

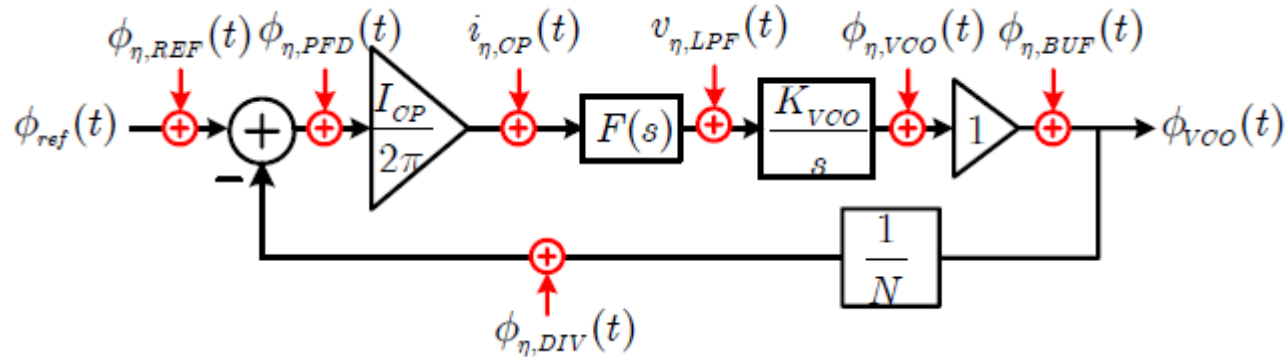

- **Many sources of noise**
 - Charge pump, loop filter, reference, divider, VCO, buffers, PFD
- **Both random and deterministic sources of “noise”**
- **Linear model can be used because noise terms are small.**


Ref./Divider/PFD Noise Contribution (1)

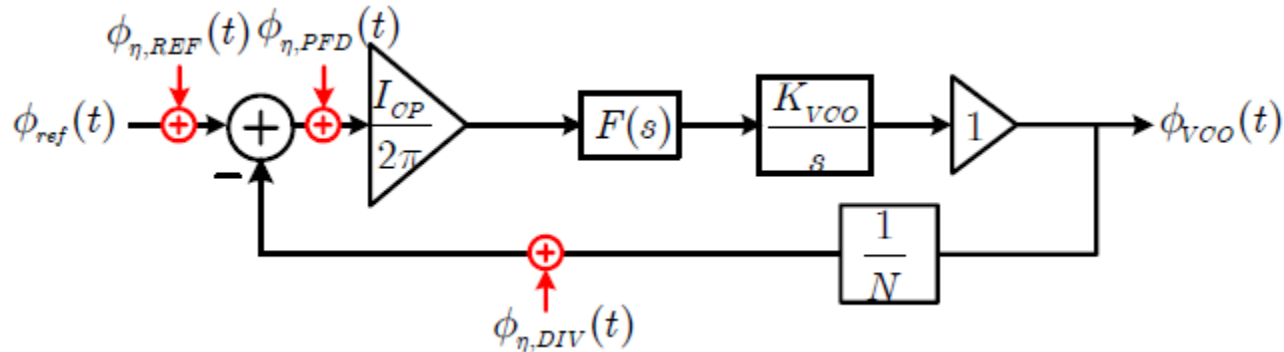

- Reference, divider, and PFD noise are combined into a single equivalent phase error term, $\phi_{\eta,ref}(t)$.
- This noise is effectively low-pass filtered by the PLL.


$$\frac{\phi_{VCO}(s)}{\phi_{\eta,ref}(s)} = \frac{NT(s)}{1 + T(s)}, \quad T(s) \text{ is open-loop transfer}$$
$$= A_{\phi}(s), \text{ "PLL closed loop transfer function".}$$

Ref./Divider/PFD Noise Contribution (2)

 

- **Circuit noise**
 - Usually white, possibly some flicker noise
 - A small “N”, small “K”, and a small “b” are advisable.
- **Noise in the reference itself**
 - Considerable particularly in clock recovery loops
 - “Peaking” in $|A_{\phi}(j\omega)|$ is bad.
 - A small “ $K\tau_2$ ” and a large “b” are advisable.


Charge Pump Noise Contribution (1)

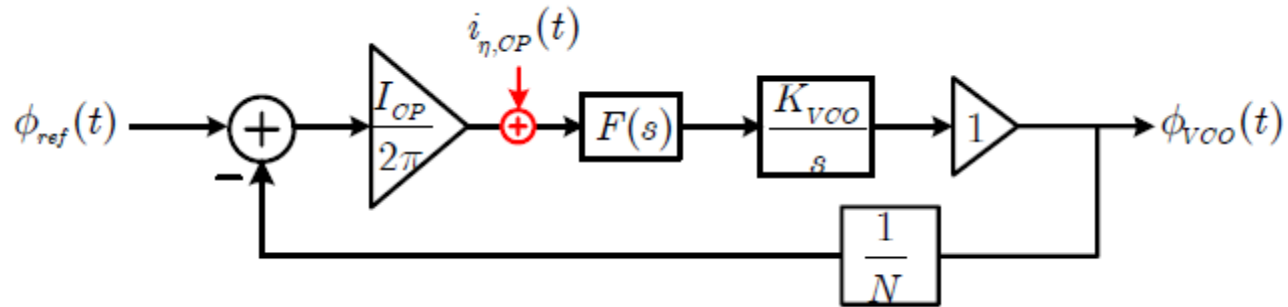

- **Charge pump dumps a net noise charge into the loop filter**
 - Both white noise and flicker noise components are present
- **Charge pump noise charge can be translated into an equivalent phase error at the reference**
 - Charge pump noise is low-pass filtered by the PLL.


$$\frac{\phi_{VCO}(s)}{i_{\eta,CP}(s)} = \left(\frac{2\pi}{I_{CP}} \right) \frac{NT(s)}{1 + T(s)} = \frac{2\pi}{I_{CP}} A_{\phi}(s)$$

Charge Pump Noise Contribution (2)

 

- **Charge pump noise is low-pass filtered by the PLL.**
 - Again, a small “N”, small “K”, and a small “b” are advisable.

Loop Filter Noise Contribution (1)

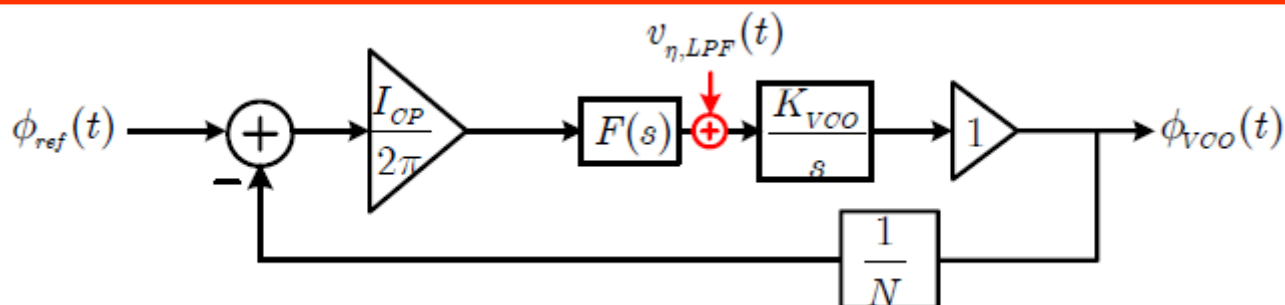


- Noise comes from resistors and transistors in active filters.
- Noise can be referred to the output of the filter.
 - E.g., $v_{\eta,LPF} = v_{\eta}$ for the 2nd order loop filter
 - E.g., for the 3rd order loop filter,
- Refer the voltage noise to the filter output
 - It is band pass filtered by the PLL.

$$v_{\eta,LPF}(s) = \left(\frac{b-1}{b} \right) \left(\frac{1}{1+s\tau_p} \right) v_n(s)$$


$$\frac{\phi_{VCO}(s)}{v_{\eta,LPF}(s)} = \frac{2\pi}{I_{CP}} \left(\frac{1}{F(s)} \right) A_{\phi}(s)$$

Loop Filter Noise Contribution (2)

 


- **For the 3rd order LPF,**
 - Again, a small “N”, a small “K”, and a small “b” are advisable

Oscillator Noise Contribution (1)

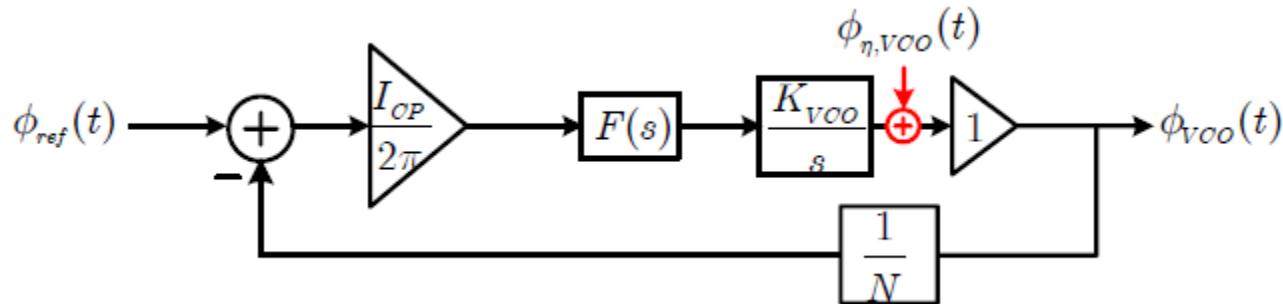

 
- Free running oscillators usually accumulate phase noise.
 - Has a complicated power spectral density.
 - Usually, the $1/f^2$ terms dominates.



- Noise on the VCO supply also causes phase noise.
- VCO noise gets high-pass filtered by the PLL.


$$\frac{\phi_{VCO}(s)}{\phi_{\eta,VCO}(s)} = \frac{1}{1 + T(s)}$$

Oscillator Noise Contribution (2)

 


- VCO noise is suppressed within the PLL bandwidth.
- A wide PLL bandwidth is desired to suppress VCO noise.
 - Typical target for PLLs in chip-to-chip communications

Buffer Noise Contribution

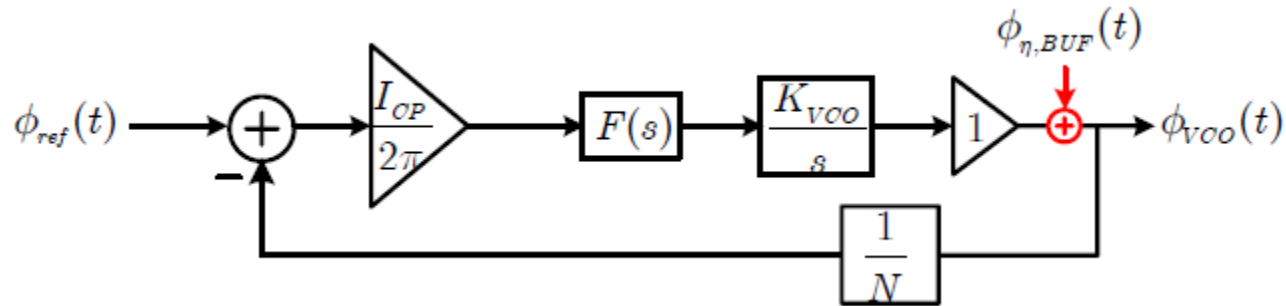


- Phase noise induced by both thermal noise and supply noise.
- Thermal noise
 - Induces timing jitter.
- Supply noise
 - Changes the buffer delay.
- Buffer noise sees the same PLL response as VCO noise.

Overall PLL Noise

 

Noise Transfer Functions

PLL Noise Contributions

 



Outline

- PLL
 - Components
 - Models
 - Noise Transfer Functions
 - Circuits
- **DLL**
 - Types
 - Models
 - Noise Transfer Functions
- **PLL/DLL comparison**




Phase Frequency Detector (PFD)

  - Phase Frequency Detector allows for wide frequency locking range, potentially entire VCO tuning range.
- 3-stage operation with UP and DOWN outputs
- Edge-triggered results in duty cycle insensitivity





PFD Transfer Characteristic

 




- **Constant slope and polarity asymmetry about zero phase allows for wide frequency range operation.**

PFD Deadzone

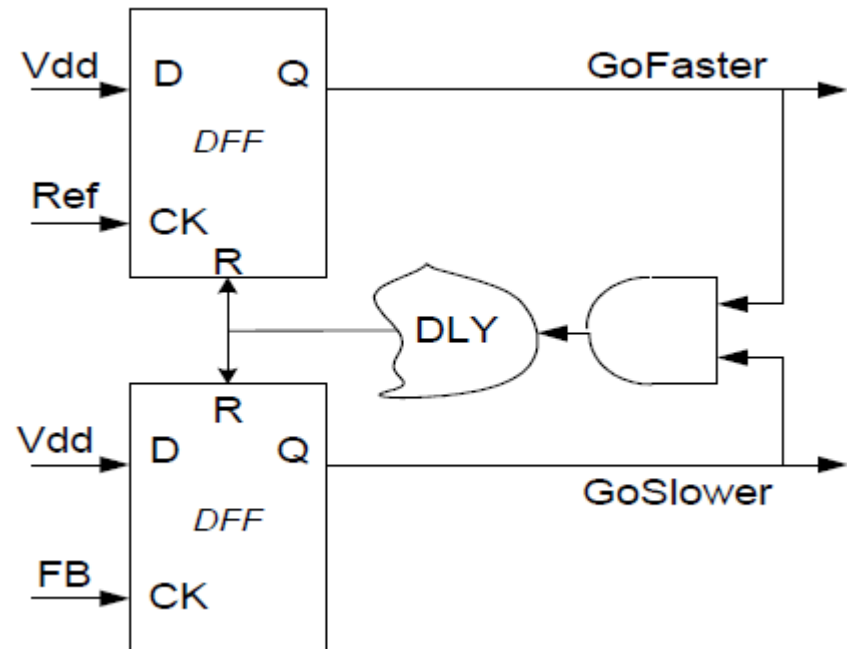 - If phase error is small, then short output pulses are produced by PFD.
- Cannot effectively propagate these pulses to switch charge pump.
- Results in phase detector “dead zone” which causes low loop gain and increased jitter.
- Solution is to add delay in PFD reset path to force a minimum UP and DOWN pulse length.



Charge Pump

   


PFD-CP Gain: $\left(\frac{1}{2\pi} \right) I_{CP}$

- **Design Goals**


- Low noise
- Low power consumption
- Low mismatch between Up and Down currents
- Low switch charge injection
- High speed of switching for wide bandwidth PLLs

Mismatch and Current Injection Problem

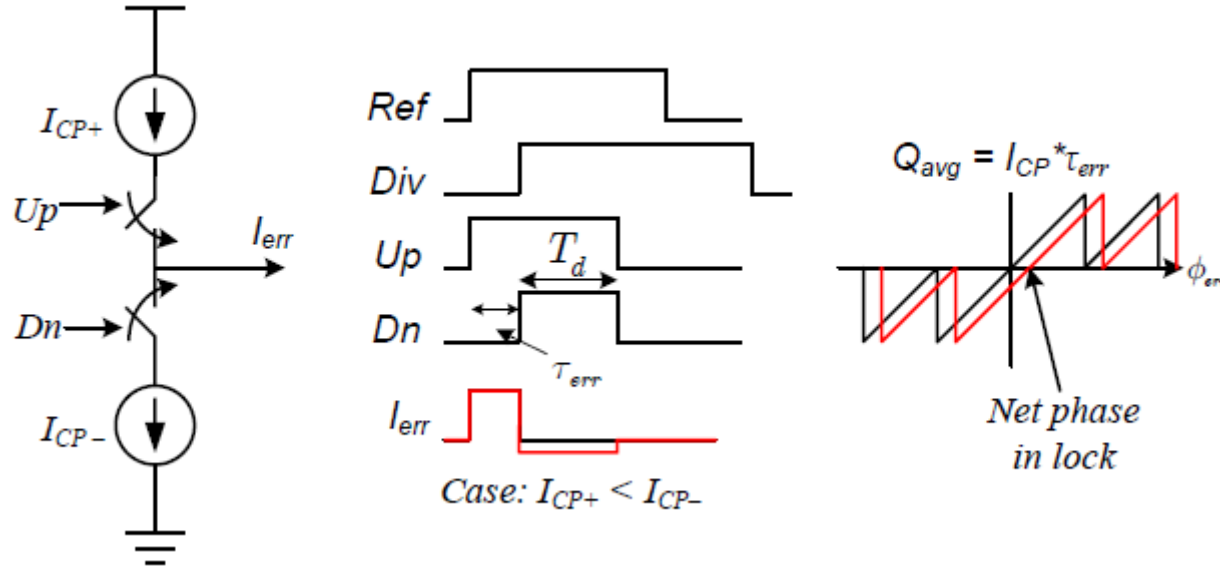

- Mismatch and charge injection add a net charge (+ve or -ve) into the loop every period.
- The PLL locks with a non-zero phase offset between the reference and the divider output.
 - Undesirable, mainly in chip-to-chip communications


Reducing Charge Injection (1)

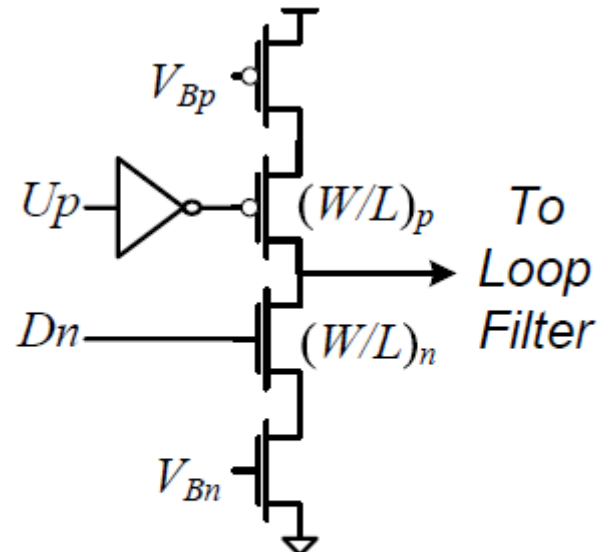

$$C_{ox}(W/L)_n(V_{DD} - V_{Tn}) = C_{ox}(W/L)_p(V_{DD} - |V_{Tp}|)$$


- Choose the switch sizes to match charge injection from nMOS and pMOS switches.
 - Not reliable, just an estimate

Reducing Charge Injection (2)

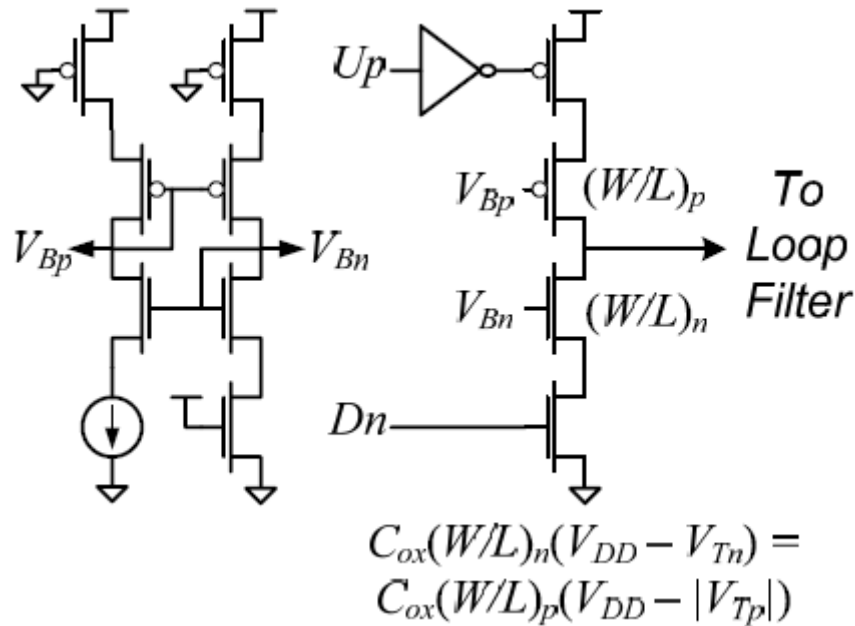


- **Move the switches close to the supply and ground rails.**
 - Channel charge goes into the parasitic cap instead of the loop filter
- **Bias generation is somewhat complicated.**

Reducing Charge Injection (3)

 

- **Equal sized dummy devices cancel charge injection.**
 - They also cancel clock feed through.
- **The amplifier keeps V_A at the same voltage as V_{CTRL} to cancel charge injection from dummy devices.**



Reducing Charge Pump Mismatch

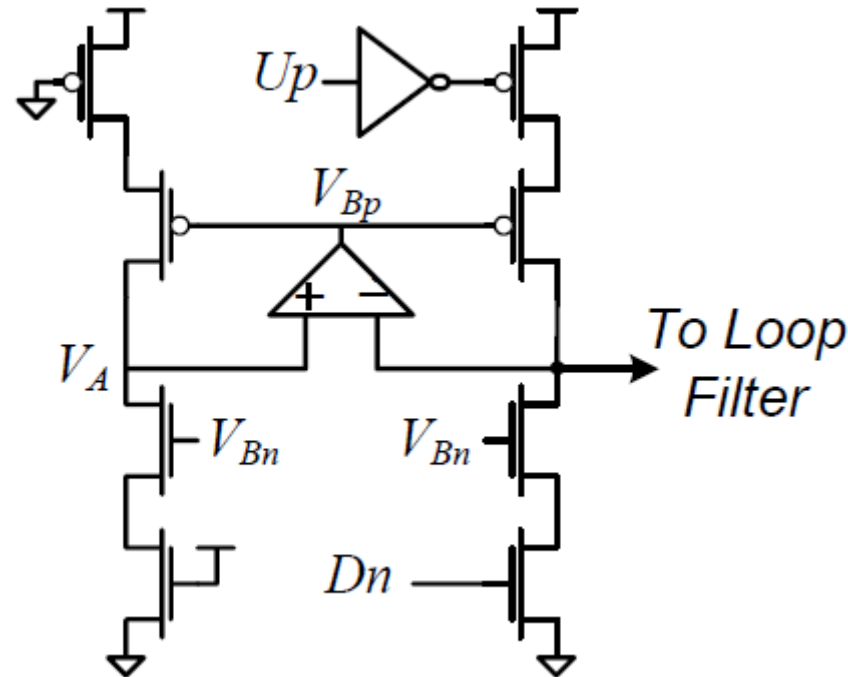

- **Very slow feedback loop to match Up current to Down current**
 - Mitigates current mismatches due to finite R_{out} of current sources.
 - Loop picks appropriate V_{BP} to make V_A match the loop filter voltage.

Design of Fast Switching Charge Pumps

  - Turning the current sources off makes switching them back on slow.
 - This is particularly so when the switches are close to the rails.
 - Use a large capacitor on the bias lines
- Redirecting the current (instead of switching it off) is much faster.
 - E.g., differential structure shown below
 - Too much power consumption



Loop Filter Design



- **Design Goals**

- Low ripple on the control voltage
 - Important concern in chip-to-chip communications
- Low die area
 - Important concern in chip-to-chip communications
- Adaptability and re-configurability
 - Component variability over process, voltage, and temperature (PVT)


Loop Filter Passive Components

- **Resistors**


- Poly, n-well, non-silicided diffusion
- MOS triode resistors
 - Limited operating range
 - Very sensitive to PVT variations

- **Capacitors**

 - Typically MOS capacitors, 5 – 15 fF/μm²
- Occupy a large die area
- Miller multiplication can decrease die area




Active Zero for Reduced Cap Area

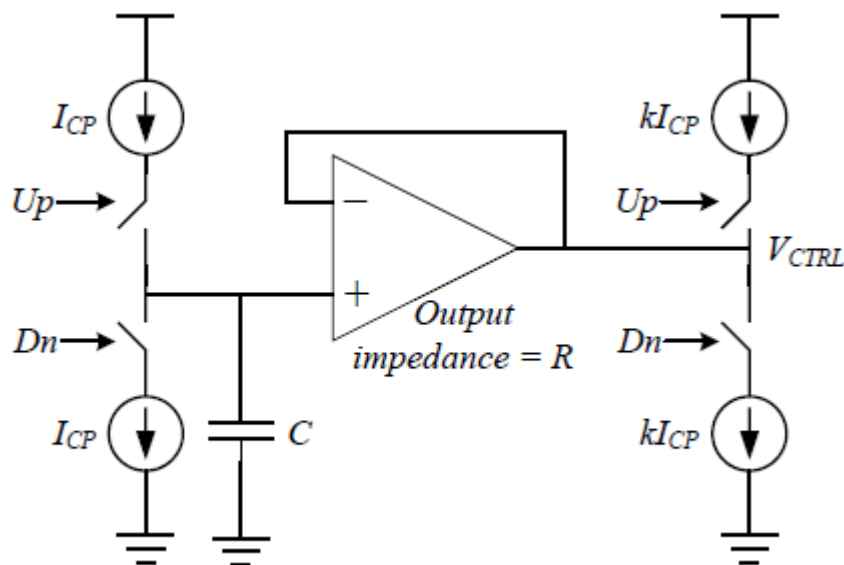

$$V_{CTRL}(s) = \frac{I_{CP}}{sC} + kI_{CP}R$$
$$\Rightarrow F(s) = R_{eq} \frac{(1 + sCR_{eq})}{sCR_{eq}},$$
$$R_{eq} = kR$$

- A large cap is required for a low zero frequency.
- A second, scaled, charge pump places the zero at $1/kCR$ rad/s.
- The resistance, R , is the output impedance of an amplifier.
- Helps in loop BW adaptability.

Switched-Capacitor Loop Filters

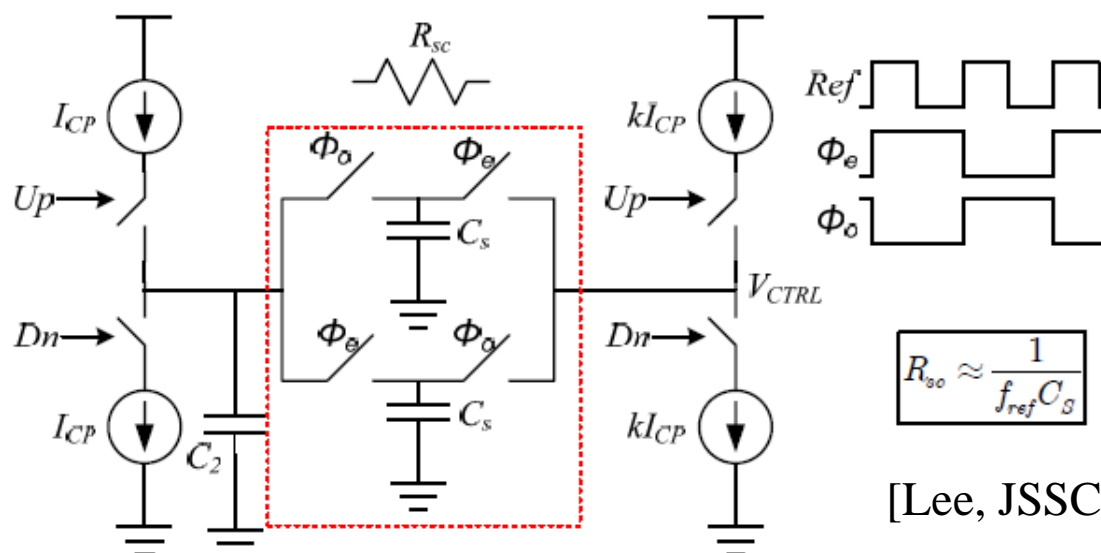

- Realizes the filter zero using a switched capacitor circuit.
- V_{CTRL} is changed only as much as needed
 - Can reduce ripple significantly.
- Charge injection and clock feed-through are serious problems.

$$V_{CTRL}(s) = \frac{I_{CP}}{sC_2} + kI_{CP}R_{sc} \Rightarrow F(s) = R_{eq} \frac{(1 + sCR_{eq})}{sCR_{eq}}, R_{eq} = kR_{sc}$$

VCO

- **Ring Oscillator**



- Easy to integrate
- Wide tuning range (5x)
- Higher phase noise

- **LC Oscillator**


- Large area
- Narrow tuning range (20-30%)
- Lower phase noise

- **Matters of Interest**

  - Frequency range, K_{vco}
- Phase noise and/or jitter
- Thermal noise and power supply noise
- Power consumption and die area




LC VCOs

 

- **Multiple oscillator structures**
 - Negative-gm, Colpitts, Clapp etc.
- **Frequency control is achieved using varactors.**



Ring Oscillators

 


- N-stage ring oscillator will have a period:

$$T_{period} = 2N \times t_{inv}$$

- N should be odd.
 - Differential inverter stages enable even number of stages.
- The delay of each inverter stage depends on V_{CTRL} .




Current Starved Inverter Stage

 


$$t_{inv} \propto \frac{V_{DD}}{(V_{CTRL} - V_T)} \text{ or } t_{inv} \propto \frac{V_{DD}}{(V_{CTRL} - V_T)^2}$$

- Very wide tuning range
- Terrible supply sensitivity
 - 1% change in V_{DD} causes a 1% change in t_{inv} .


Differential Inverter Stages

 

$$t_{inv} \propto \frac{C_L}{(V_{DD} - V_{CTRL} - |V_T|)}$$

 


$$t_{inv} \propto \frac{C_L}{g_{m,p}}$$

 

- Differential nature reduces supply noise only slightly.
- Bias current has to be adjusted to maintain swing.
- Third circuit is a full swing VCO.



Supply-Regulated VCOs

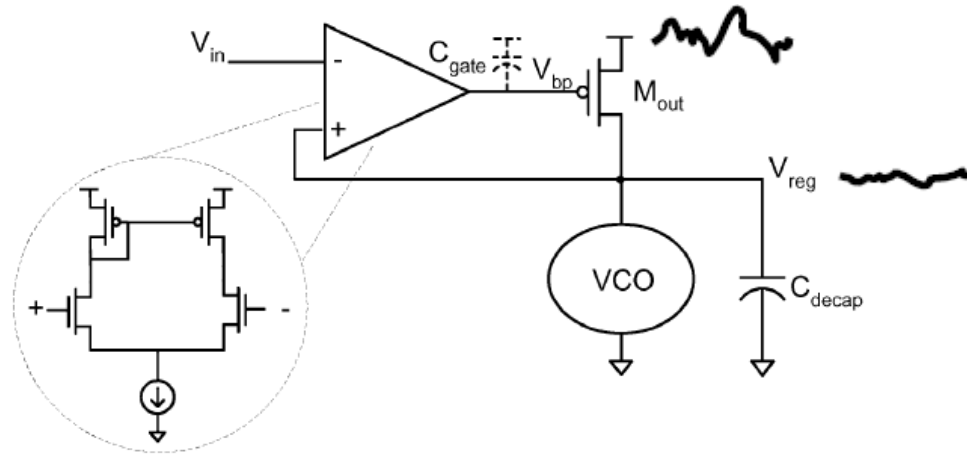

- **The amplifier adjusts V_{bp}**
 - So, V_{reg} is relatively free of V_{DD} variations
- **Desirable features**
 - Large regulation range i.e. low dropout regulation
 - Low amplifier power consumption
 - Small area
 - Wide bandwidth suppression of V_{DD} variations




Basic Divide-by-2

 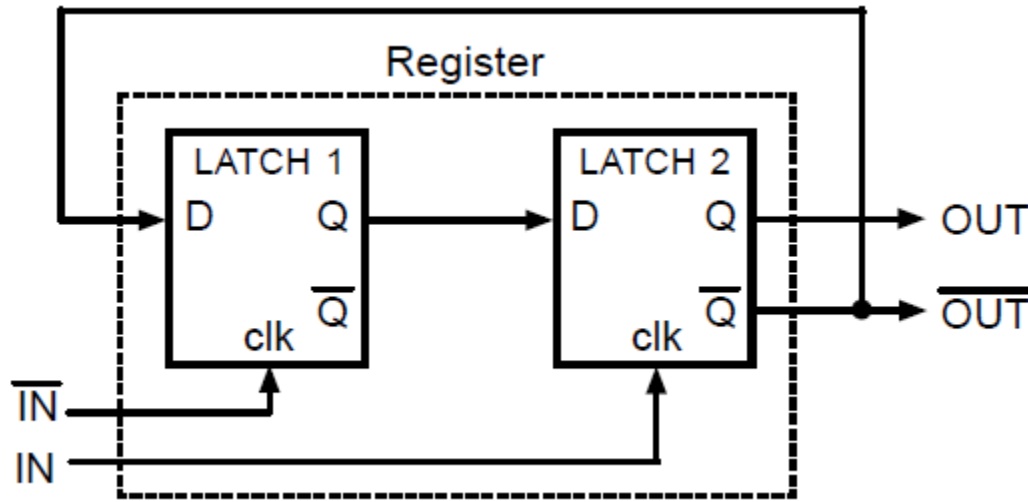

- Divide-by-2 can be realized by a flip-flop in “negative feedback”.
- Divider should operate correctly up to the maximum output clock frequency of interest PLUS some margin.

Divide-by-2 with TSPC FF

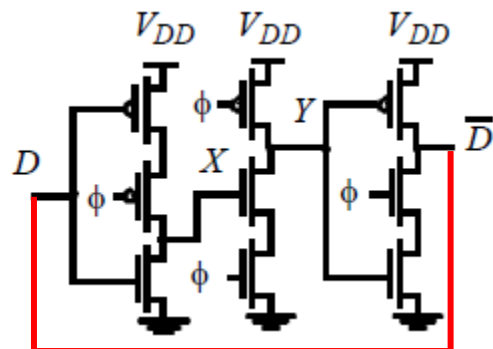

- **Advantages**



- Reasonably fast, compact size, and no static power
- Requires only one phase of the clock.

- **Disadvantages**

- Signal needs to propagate through three gates per input cycle.
- Need full swing CMOS inputs.
- Dynamic flip-flop may have issues at very low frequency operation (test mode) depending on process leakage.



Divide-by-2 with CML FF

  

- **Advantages**

- Signal only propagates through two CML gates per input cycle.
- Accepts CML input levels.


- **Disadvantages**

- Larger size and dissipates static power.
- Requires differential input.
- Additional speedup (>50%) can be achieved with shunt peaking inductors.



Binary Dividers

Asynchronous Divider

 


- **Advantages**

- Each stage runs at lower frequency, resulting in reduced power
- Reduced high frequency clock loading

- **Disadvantage**

- Jitter accumulation

Synchronous Divider

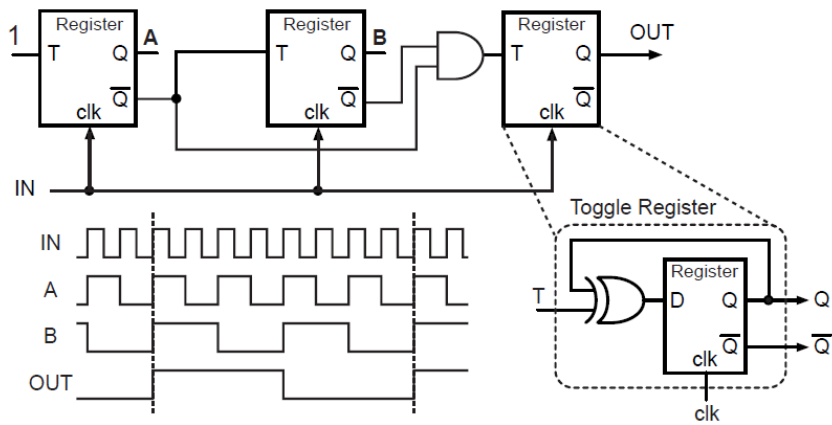


- **Advantage**

- Reduced jitter

- **Disadvantage**

- All flip-flops work at maximum frequency, resulting in high power
- Large loading on high frequency clock

Dual Modulus Prescalers

 


- **For /15, first prescaler circuit divides by 3 once and 4 three times during the 15 cycles.**

Outline

- PLL
 - Components
 - Models
 - Noise Transfer Functions
 - Circuits
- **DLL**
 - Types
 - Models
 - Noise Transfer Functions
- **PLL/DLL comparison**



DLL VCDL

 



- Just a chain of inverter stages (similar to ring oscillators)
- Delay is controlled by V_{CTRL} .

$$\Delta T(t) = K_{VCDL} V_{CTRL}(t) \text{ or } \phi(t) = K_{DL} V_{CTRL}(t)$$

seconds/volts


radians/volts, $K_{DL} = \frac{2\pi}{T_{ref}} K_{VCDL}$

Delay Locked Loop –Types I and II

  

- Closed loop response is different between Type I and II DLLs
- Type I
 - More popular type of DLL
 - Used in multi-phase clock generation
 - High frequency reference noise shows up in the output
- Type II
 - Used in clock and data recovery (CDR) loops

Type II Continuous-Time Model

 


- Just as in the PLL, the continuous time model is accurate for bandwidths $\ll f_{ref}/10$.
- Negative feedback loop tries to force $\phi_{err}(t) = \phi_0$
- Loop transfer function is

$$T(s) = K_{PD}K_{DL}F(s)$$



- Closed loop response is

$$A_\phi(s) = \frac{K_{PD}K_{DL}F(s)}{1 + K_{PD}K_{DL}F(s)}$$


Type II Charge Pump DLL

 

  - $F(s)$ is typically just an integrator.
- Sometimes, an additional pole is added



1st Order Type II CP DLL

 

- Loop transfer function is

$$T(s) = \frac{K}{s}, \quad K = \frac{I_{CP} K_{DL}}{2\pi C}$$


Unconditionally stable !

- Closed loop response is

$$A_{\phi}(s) = \frac{1}{1 + s/K}$$


1st order response, no peaking !

Noise Transfer Functions

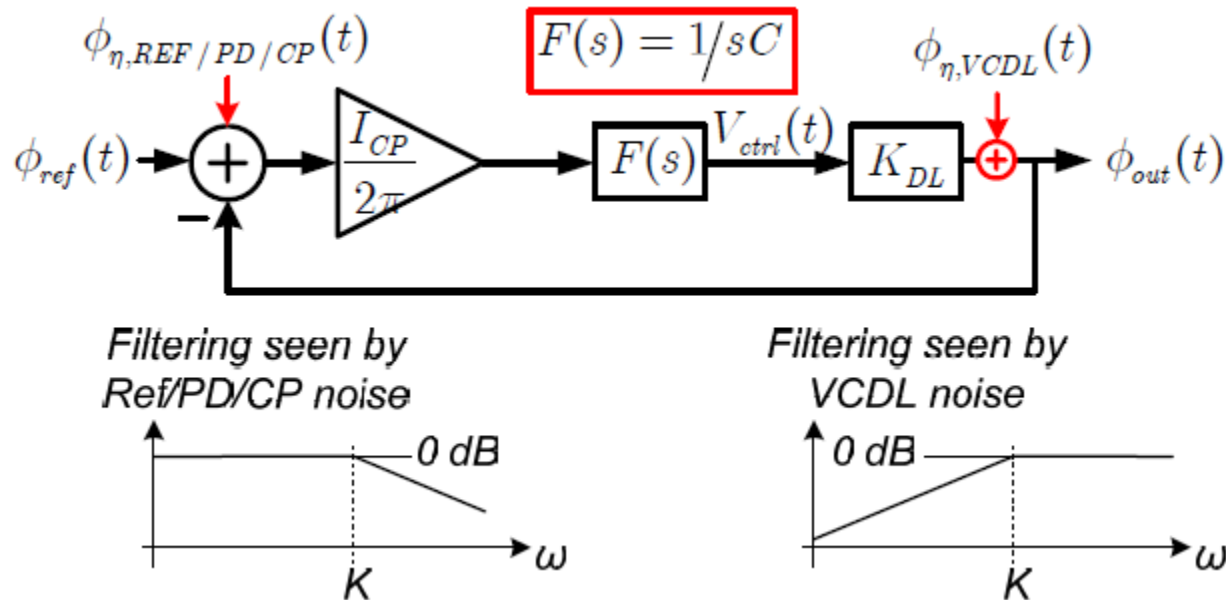

- **VCDL noise is suppressed by a high-pass filter.**
 - Wide bandwidth can be easily achieved because stability is not a problem.
- **Ref/PD/CP noise is suppressed by a low-pass filter.**
 - There is no jitter peaking.

2nd Order Type II CP DLL

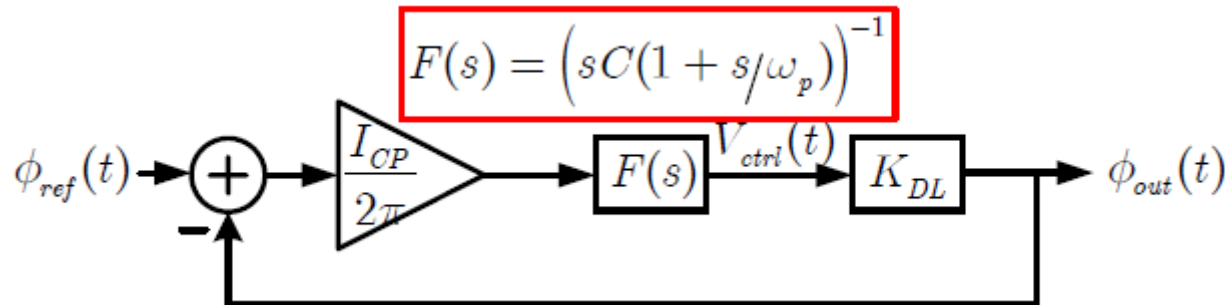

- Loop transfer function is

$$T(s) = \frac{K}{s(1 + s/\omega_p)}, \quad K = \frac{I_{CP}K_{DL}}{2\pi C}$$


Not unconditionally stable, anymore !

- Closed loop response is

$$A_\phi(s) = \frac{1}{1 + s/K + s^2/K\omega_p}$$






Noise Transfer Functions

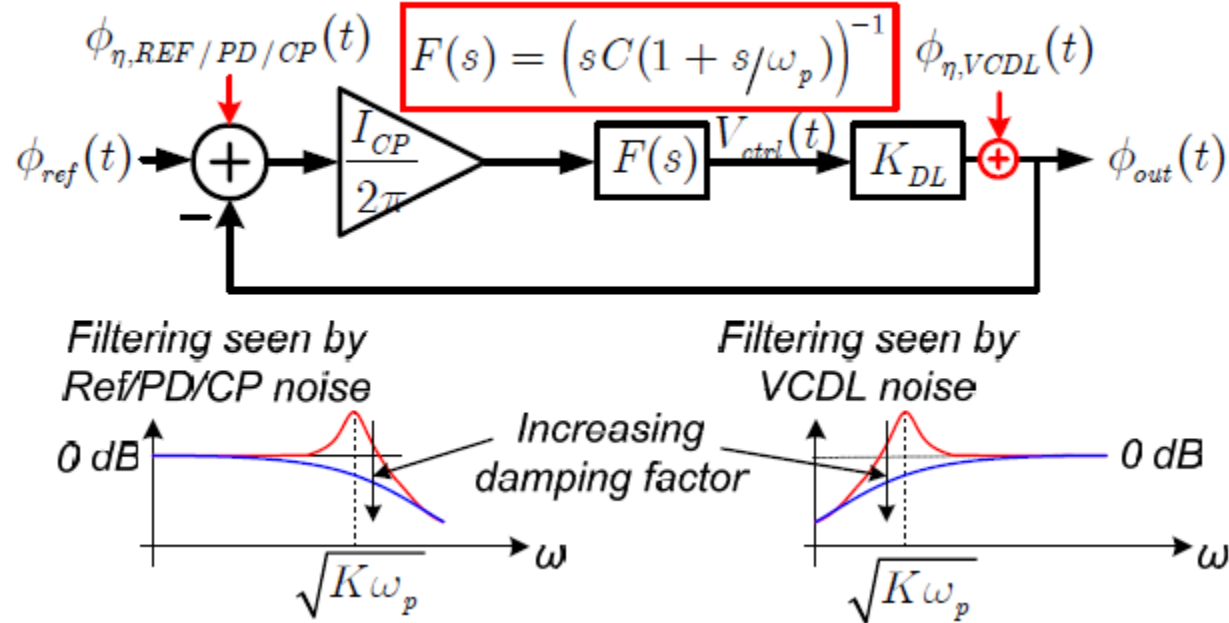


- **Additional pole has multiple effects.**
 - Increases jitter peaking.
 - Attenuates high frequency Ref/PD/CP noise a lot more.
 - Could increase VCDL noise contribution.

Type I CP DLL

 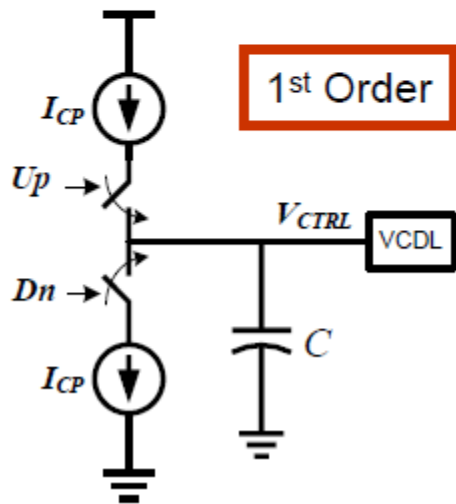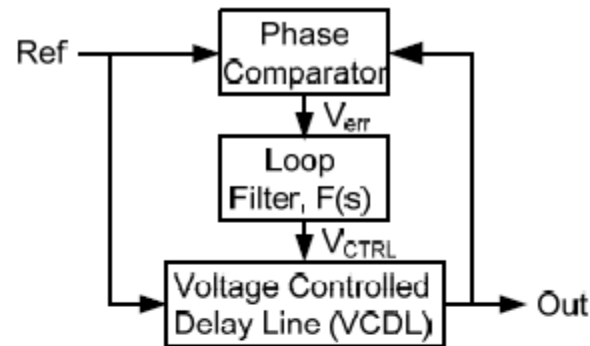

Type I DLL Discrete-Time Model

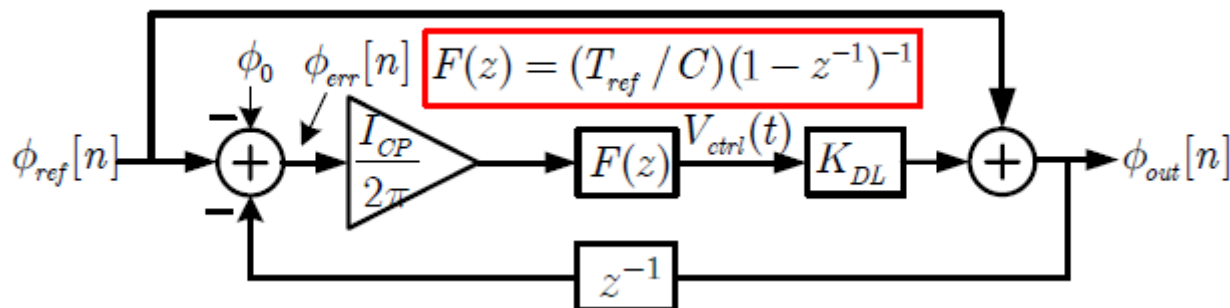

- A continuous time mode can be derived, but a discrete time model is simpler and more appropriate.
- Loop transfer function is

$$T(z) = z^{-1} \frac{I_{CP} K_{DL} F(z)}{2\pi}$$


$$T(z) = \frac{K T_{ref} z^{-1}}{1 - z^{-1}}, \quad K = \frac{I_{CP} K_{DL}}{2\pi C}$$

- Closed loop response is

$$A_{\phi}(z) = \frac{1 + zT(z)}{1 + T(z)}$$


$$A_{\phi}(z) = \frac{1 - z^{-1} + K T_{ref}}{1 - z^{-1} + K T_{ref} z^{-1}} = \frac{(1 + \alpha) - z^{-1}}{1 - (1 - \alpha)z^{-1}}$$

Jitter Peaking

 


- **Noise on the reference does NOT see a low-pass filter.**
- **The reference noise is actually, significantly, amplified**
 - The Type I DLL thinks a sudden +ve jump in the Reference phase is actually a sudden –ve jump on the VCDL output phase
 - So, it increases the VCDL delay → jitter amplification


Other Noise Transfer Functions

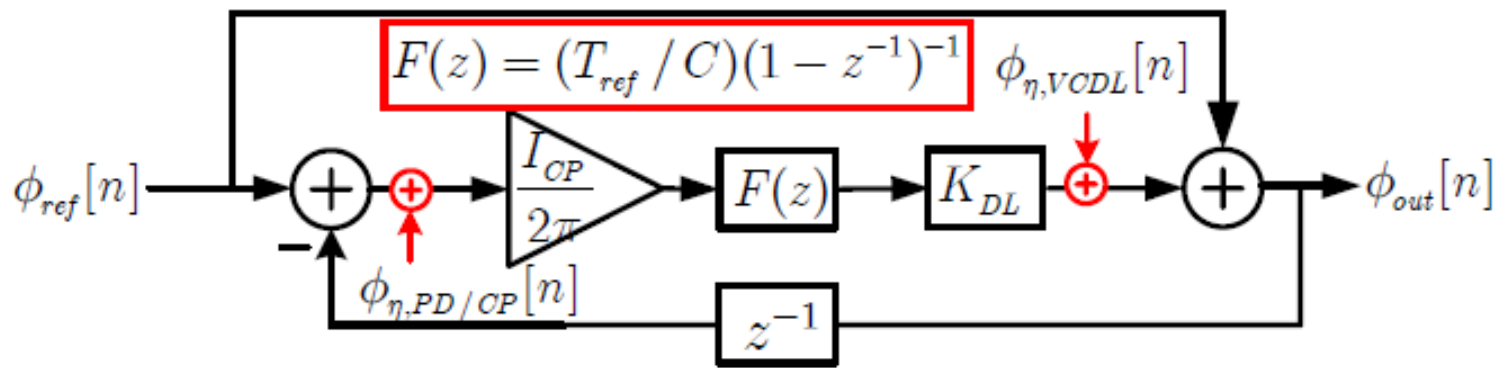

Filtering seen by
PD/CP noise

 

Filtering seen by
VCDL noise

 


$$\frac{\phi_{out}(z)}{\phi_{\eta,PD/CP}(z)} = \frac{\alpha z^{-1}}{1 - (1 - \alpha)z^{-1}}$$

$$\frac{\phi_{out}(z)}{\phi_{\eta,VCDL}(z)} = \frac{1 - z^{-1}}{1 - (1 - \alpha)z^{-1}}$$

PLL vs. DLL (1)

 - **Stability**
 - DLLs are more stable, and hence easier to design.
- **Supply noise**
 - DLLs can be designed with higher bandwidths.
 - So, supply noise is better attenuated.



PLL vs. DLL (2)

- **Circuit noise**

- The VCDL does not accumulate jitter unlike the VCO.
 - The VCDL actually accumulates noise within a period.
 - But, at the end of the period, the noise is cleaned up.
- So, DLLs have lower phase noise and/or jitter due to circuit noise.

- **Reference noise**

- DLLs (particularly Type I) have higher jitter peaking.

