

Wireline Transceiver Circuits

Dr. Mohamed Salah Mobarak

Email: mohamedmobarak@eng.cu.edu.eg

Department of Electronics and Electrical
Communications Engineering
Cairo University

Course Outline


- Introduction to phase locked loops
- Phase locked loop top level analysis
- Phase locked loop building blocks
 - Phase detectors
 - Voltage controlled oscillators
 - Frequency dividers
- Phase locked loop noise analysis
- Crystal oscillator circuit

Introduction to Phase Locked Loops

- Phase locked loops (PLL) are used in many applications such as wireless and wireline transceivers
 - In radio/TV transceivers there are multiple channels
 - Phase locked loop is used to generate the required frequency for a certain channel
 - High accuracy and low noise is required
- PLLs are also used to generate clocks for digital processors, wireline communication systems




Introduction to Phase Locked Loops

 - PLL is used to generate a certain output frequency
- Feedback is used to generate precise output frequency
- An example of feedback system is air condition (A/C) systems where a desired output temperature is needed




Introduction to Phase Locked Loops

  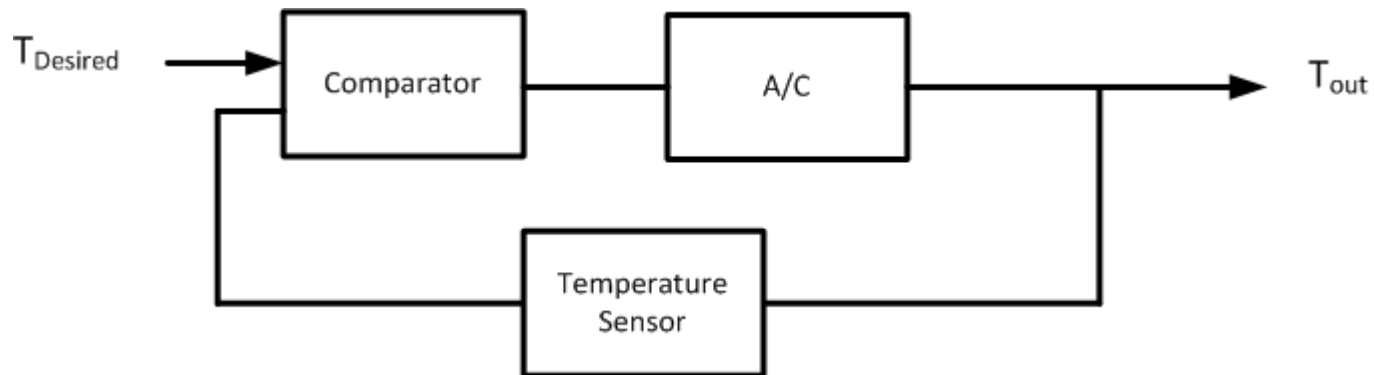
- Feedback system need to be stable
 - If comparator output is slow, the output temperature will oscillate




Basic PLL Block Diagram

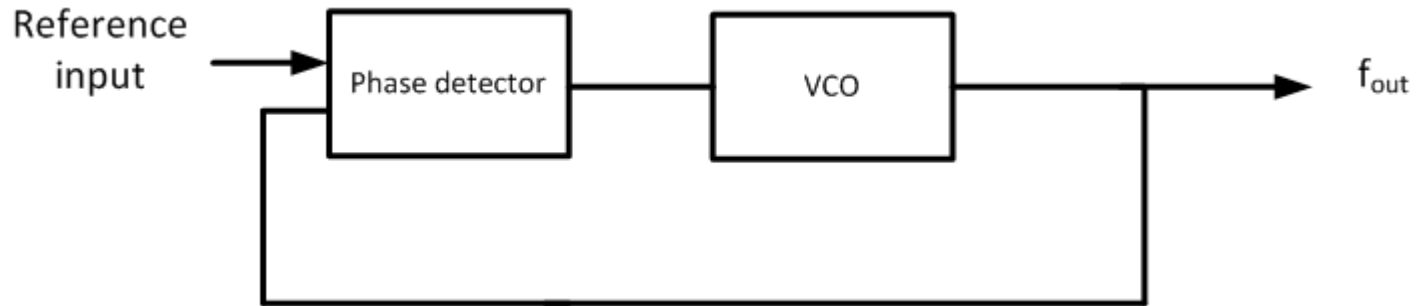

 - Main building blocks of PLL are
 - Voltage controlled oscillator (VCO)
 - Phase Detector (PD)
- Simplest frequency detector is XOR gate




Basic PLL Block Diagram

 

- Note that phase detector output is voltage while VCO output is frequency or phase
- XOR output is a pulse proportional to the phase difference
 - Low pass filter is added to extract the average voltage which is proportional to the phase difference

XOR Phase Detector


Case 1: $-\pi < \phi_1 - \phi_2 < 0$

 

- Assume that supply of XOR gate is V_{CC} and $-V_{CC}$
- 1 period duration is T , which is also 2π
 - $\Delta T/T = -\Delta\phi/2\pi$
- The output $X_{out}(t)$ can be represented by a DC component and a summation of sinusoidal waves
 - Sinusoidal waves will be filtered by LPF and only DC component will pass
 - DC component of $X_{out} = \frac{1}{T} \int_0^T X_{out}(t) dt = \frac{1}{T} (V_{CC} 2\Delta T - V_{CC} (T - 2\Delta T))$
 $= 2V_{CC} \left(\frac{\Delta T}{T} \right) - V_{CC} = 4V_{CC} \left(\frac{-\Delta\phi}{2\pi} \right) - V_{CC}$

XOR Phase Detector


Case 2: $0 < \phi_1 - \phi_2 < \pi$

 

- Assume that supply of XOR gate is V_{CC} and $-V_{CC}$
- 1 period duration is T , which is also 2π
 - $\Delta T/T = \Delta\phi/2\pi$
- The output $X_{out}(t)$ can be represented by a DC component and a summation of sinusoidal waves
 - Sinusoidal waves will be filtered by LPF and only DC component will pass
 - DC component of $X_{out} = \frac{1}{T} \int_0^T X_{out}(t) dt = \frac{1}{T} (V_{CC} 2\Delta T - V_{CC} (T - 2\Delta T))$


$$= 2V_{CC} \left(\frac{\Delta T}{T} \right) - V_{CC} = 4V_{CC} \left(\frac{\Delta\phi}{2\pi} \right) - V_{CC}$$

XOR Phase Detector

 


- One region will be stable while the other one will be unstable

Frequency Locked Loop

 


- Can we use frequency locked loop instead of phase locked loop?
 - Frequency is the differentiation of phase
 - Finite phase error exist in PLL

Frequency Locked Loop

 

- For an op-amp with infinite gain, $V_{out} = V_{in}$
- Due to finite op-amp gain
 - $V_{in} - V_{out} = V_{out}/A$
- For PLL due to finite loop gain, there is a finite phase difference
 - $\phi_{out} - \phi_{in} \neq 0$




Frequency Locked Loop

 

- For PLL with finite gain
 - $\phi_{out} - \phi_{in} = \text{Constant}$, then $f_{out} = d\phi_{out}/dt = f_{in} = d\phi_{in}/dt$
- For frequency locked loop, there will be a finite difference between input and output frequencies



VCO Model

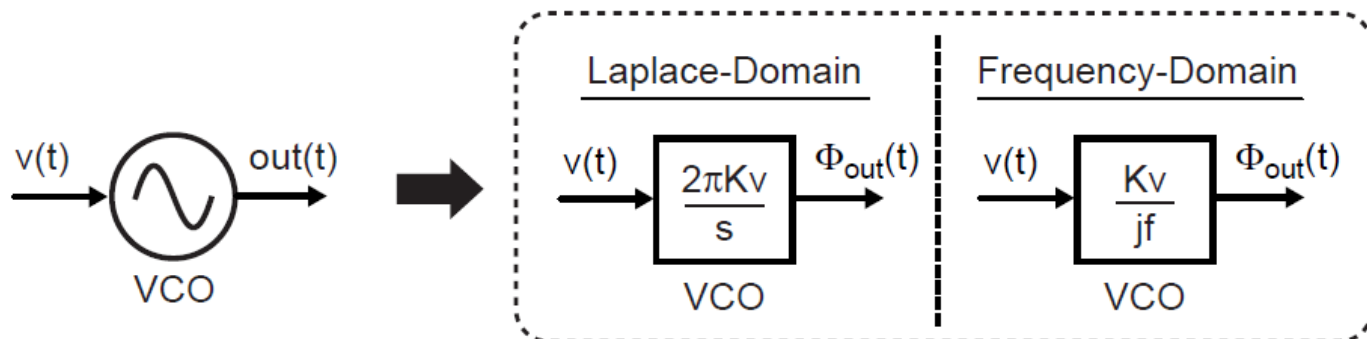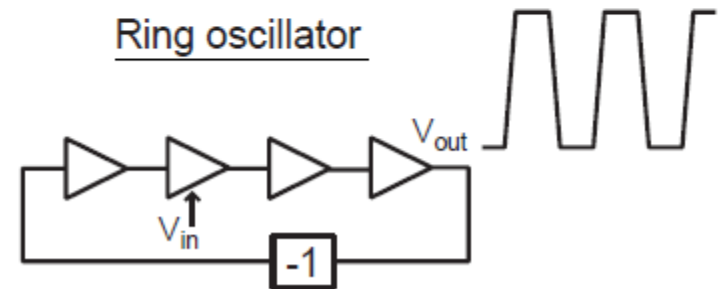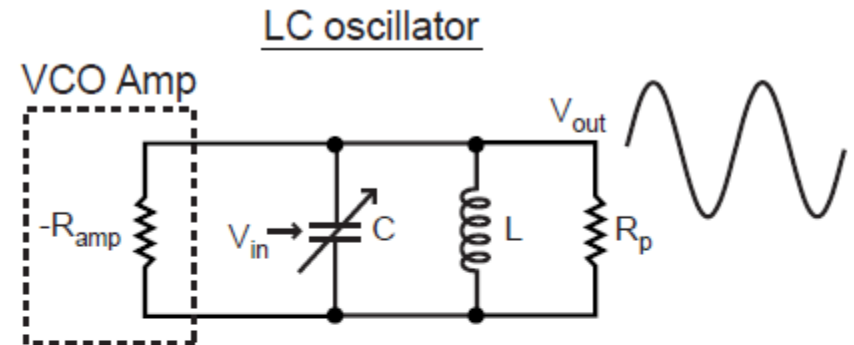- $f_{out} = Kv_c$
- $\phi_{out} = \int 2\pi f_{out} dt$




Phase Detector Model

  - For $0 < \phi_1 - \phi_2 < \pi$
 - Phase detector output is given by $4V_{CC} \left(\frac{\Delta\phi}{2\pi} \right) - V_{CC}$
 - Phase detector can be modeled as a constant gain block




Loop Dynamics of PLL

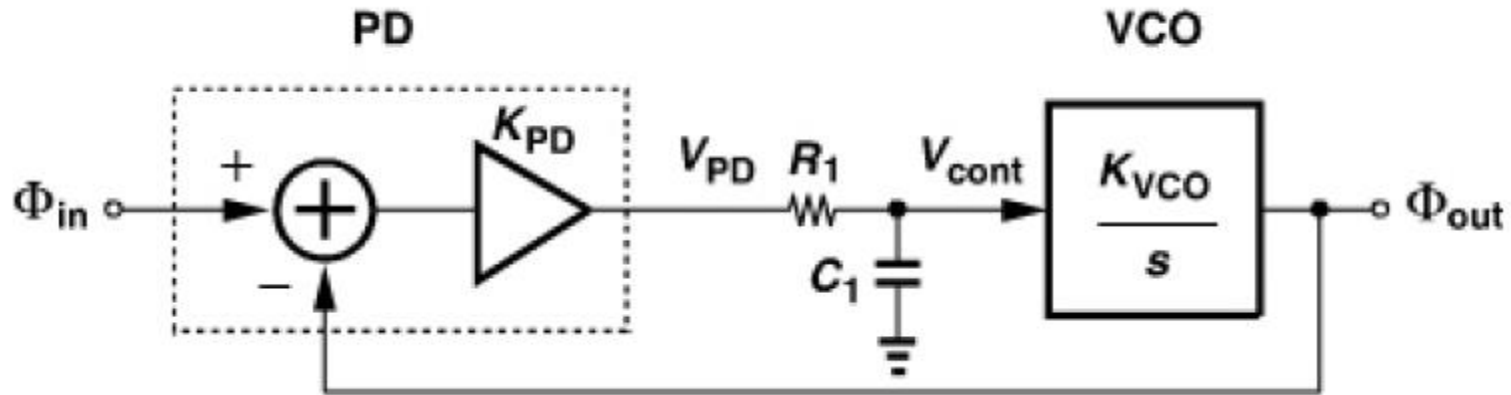

- Phase domain is used to model the PLL
 - VCO act as an integrator
 - $f_{out} = K_{VCO} V_{in}$, or $\phi_{out} = K_{VCO} \int V_{in} dt$

$$\frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD} K_{VCO}}{R_1 C_1 s^2 + s + K_{PD} K_{VCO}}$$

Loop Dynamics of PLL

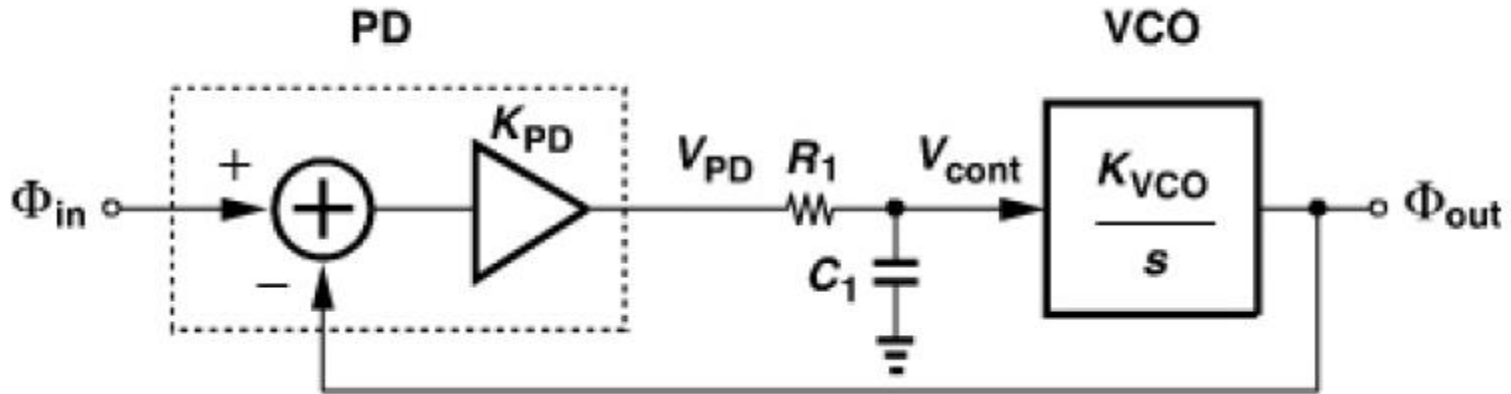

$$\frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}}$$


$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$

$$\frac{\phi_{out}}{\phi_{in}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_ns + \omega_n^2}$$

$$\omega = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$


- PLL has a second order transfer function and it can have under-damped, critically damped, or over-damped response

Loop Dynamics of PLL

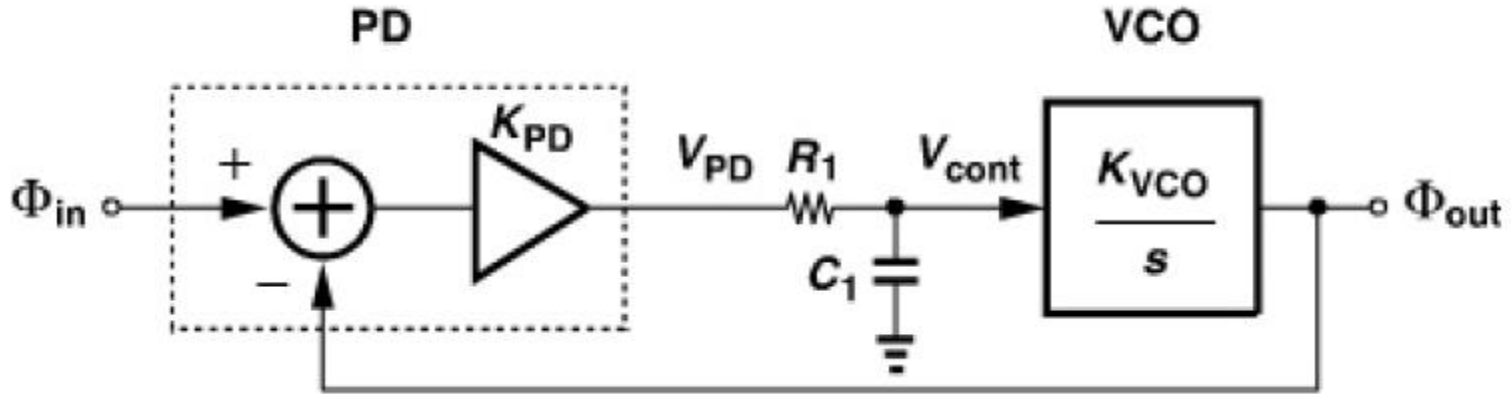


$$\frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}}$$

 
- The output frequency of VCO is given by: $\omega = \omega_0 + K_{vco}\Delta v_c$
- ω_0 is the steady state output frequency
- $K_{vco} = \Delta\omega / \Delta v_c$



XOR Phase Detector

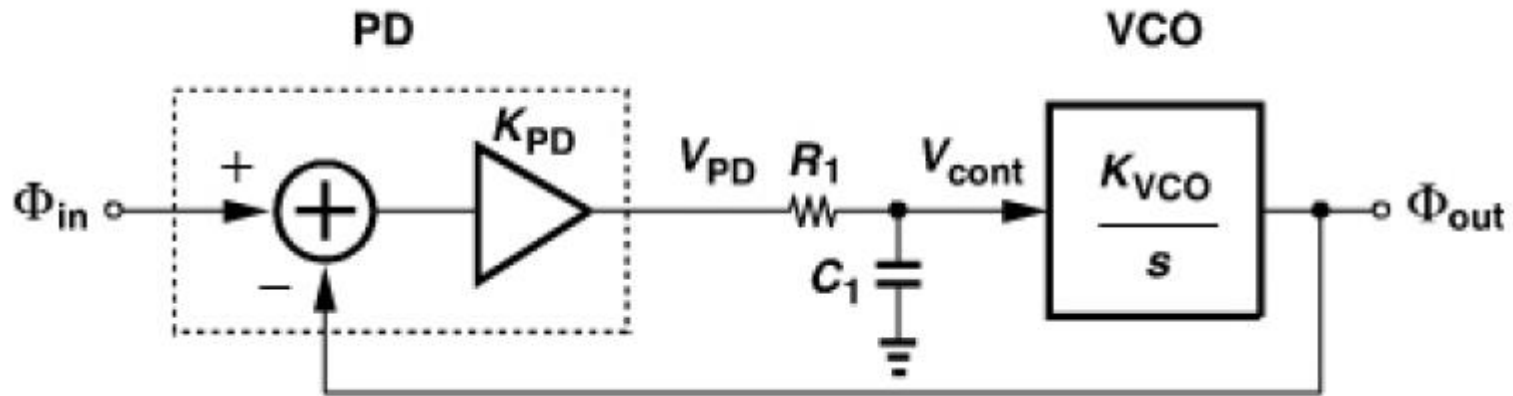

 - Assume $\omega_{vco} = \omega_0 + K_{vco}V_{cont}$
- If $\omega_0 = \omega_{ref}$, then $V_{cont} = 0$ and $\phi_1 - \phi_2 = \pi/2$
- In general $V_{cont} = (\omega_{ref} - \omega_0)/K_{vco}$, $\phi_1 - \phi_2 = \frac{\pi}{2} + V_{cont}\pi/2V_{cc}$





Voltage Multiplication

- For ideal buffer $V_{out} = V_{in}$
- With voltage division network $V_{out} = 16V_{in}$


$$A(s) = \frac{A_0}{1 + s/p}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{1}{A_0} + \frac{1}{N}} \rightarrow \frac{V_{out}}{V_{in}} = N$$
  
$$\frac{V_{\varepsilon}}{V_{in}} = \frac{1}{1 + \frac{A_0}{N}} \rightarrow \frac{V_{\varepsilon}}{V_{in}} = 0$$




Frequency Multiplication

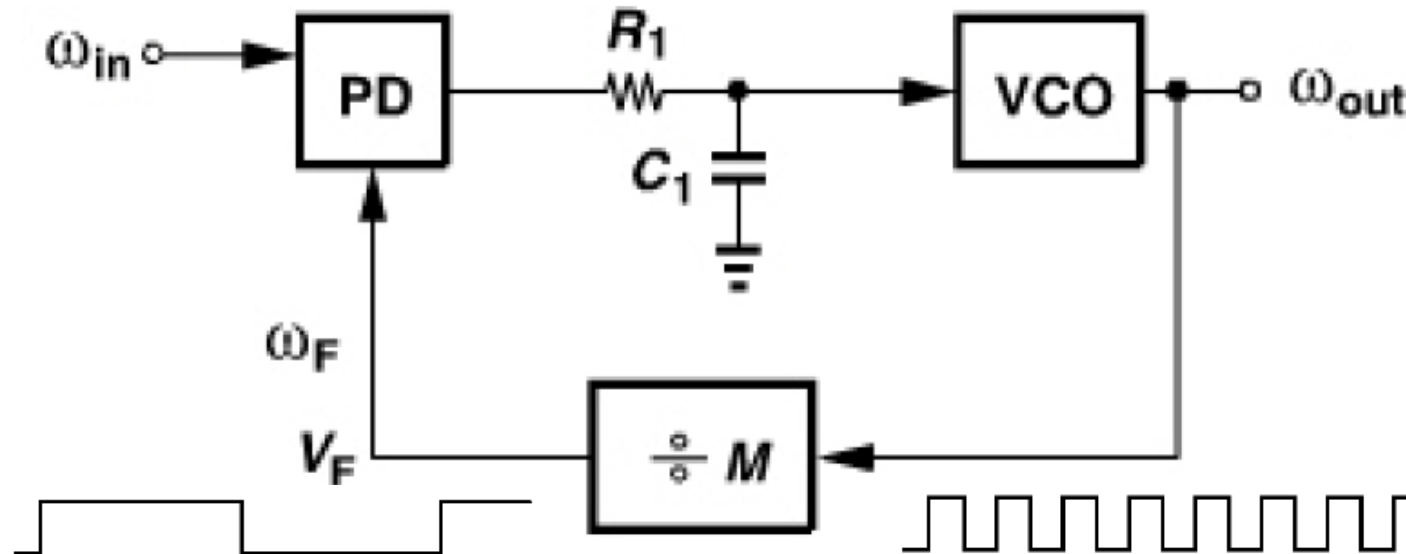

- $f_{out} = M \times f_{in}$
- As M changes, the output frequency also changes
 - Multiple frequencies can be generated from one reference

Frequency Multiplication

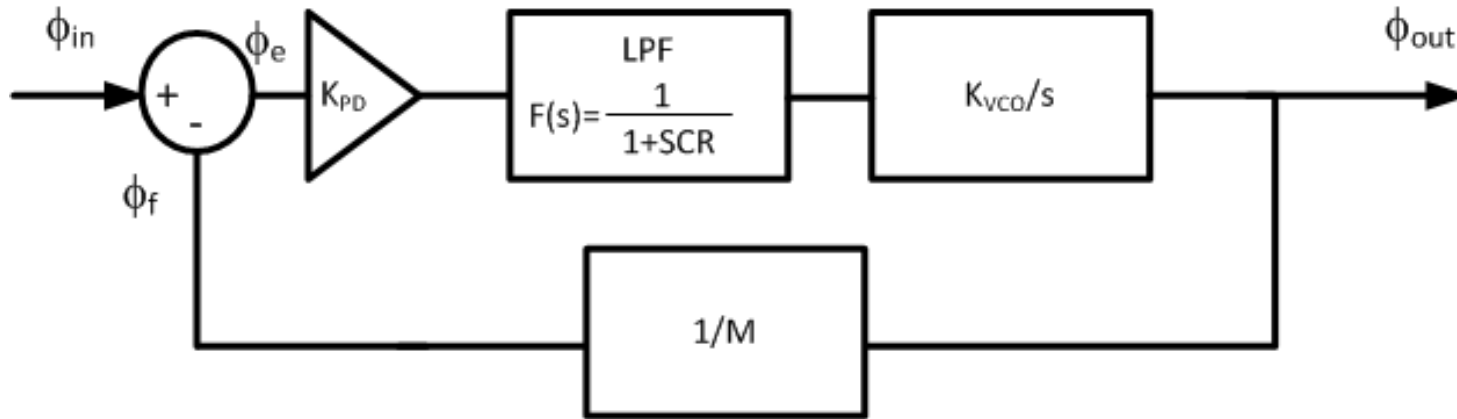

$$G(s) = \frac{K_{PD}K_{VCO}}{s + R_1C_1s^2} \quad H(s) = \frac{1}{M}$$

$$\frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}/M}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}M}{K_{PD}K_{VCO}}}$$


$$\frac{\phi_{out}}{\phi_{in}} = \frac{M\omega_n^2}{s^2 + 2\zeta\omega_ns + \omega_n^2}$$

$$\omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}/M}$$

- What is the transfer function ω_{out}/ω_{in} ?




Phase Step

 - *Frequency is the same, the phase take a step at $t=0$*
- $\phi(t) = \Delta\phi u(t)$
- $v(t) = \sin(\omega t + \Delta\phi u(t))$






Frequency Step

   - $\omega(t) = \omega_0 + \Delta\omega u(t)$
- $v(t) = \sin(\omega_0 t + \Delta\omega t u(t))$
 $= \sin(\omega_0 t + \phi(t)u(t))$
- $\phi(t) = \Delta\omega t$



Frequency Ramp

   - $\omega(t) = \omega_0 + \Delta\omega t u(t)$
- $v(t) = \sin(\omega_0 t + \phi(t)u(t))$
- $\phi(t) = \int_0^t \Delta\omega \tau = \frac{\Delta\omega t^2}{2}$
- $v(t) = \sin(\omega_0 t + \frac{\Delta\omega t^2}{2} u(t))$




Order and Type

- Order of PLL system is the number of poles in the closed loop transfer function
- Type of PLL is the number of integrators that exists in the loop
- Order should be greater than or equal Type
- Since VCO is an integrator, PLL has to be at least type 1.
- Type 2 is the most common PLL type

Phase Error and Frequency Error

- The steady state error can be calculated from S domain $\lim_{t \rightarrow \infty} y(t) = \lim_{s \rightarrow 0} sY(s)$
- The phase error transfer function ($\phi_e = \phi_{in} - \phi_f$)
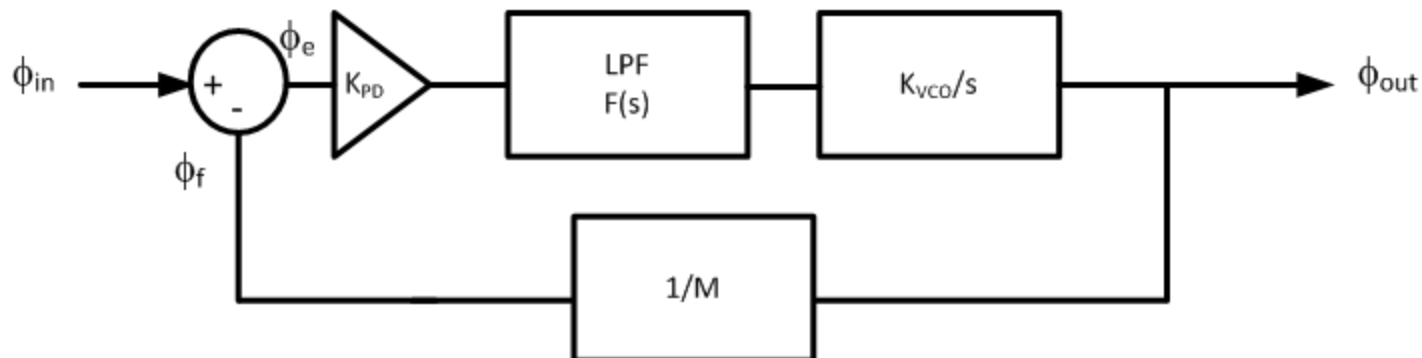
$$\frac{\phi_e}{\phi_{in}} = \frac{s}{s + K_{PD}K_{VCO}F(s)/M}$$



Phase Error and Frequency Error

$$\phi_e(s) = \frac{s\phi_{in}(s)}{s + K_{PD}K_{VCO}F(s)/M}$$

$$\lim_{t \rightarrow \infty} \phi_e(t) = \lim_{s \rightarrow 0} s\phi_e(s) = \lim_{s \rightarrow 0} \frac{s^2\phi_{in}(s)}{s + K_{PD}K_{VCO}F(s)/M}$$

- For a phase step $\phi_{in}(s) = \Delta\phi/s$


$$\lim_{t \rightarrow \infty} \phi_e(t) = \lim_{s \rightarrow 0} \frac{s\Delta\phi}{s + K_{PD}K_{VCO}F(s)/M} = 0 \quad (\text{for } F(0) \neq 0)$$

- For a frequency step $\omega(s) = \Delta\omega/s$ or $\phi_{in}(s) = \Delta\omega/s^2$

$$\lim_{t \rightarrow \infty} \phi_e(t) = \lim_{s \rightarrow 0} \frac{\Delta\omega}{s + K_{PD}K_{VCO}F(s)/M} = \frac{M\Delta\omega}{K_{PD}K_{VCO}F(0)}$$

Phase Error and Frequency Error

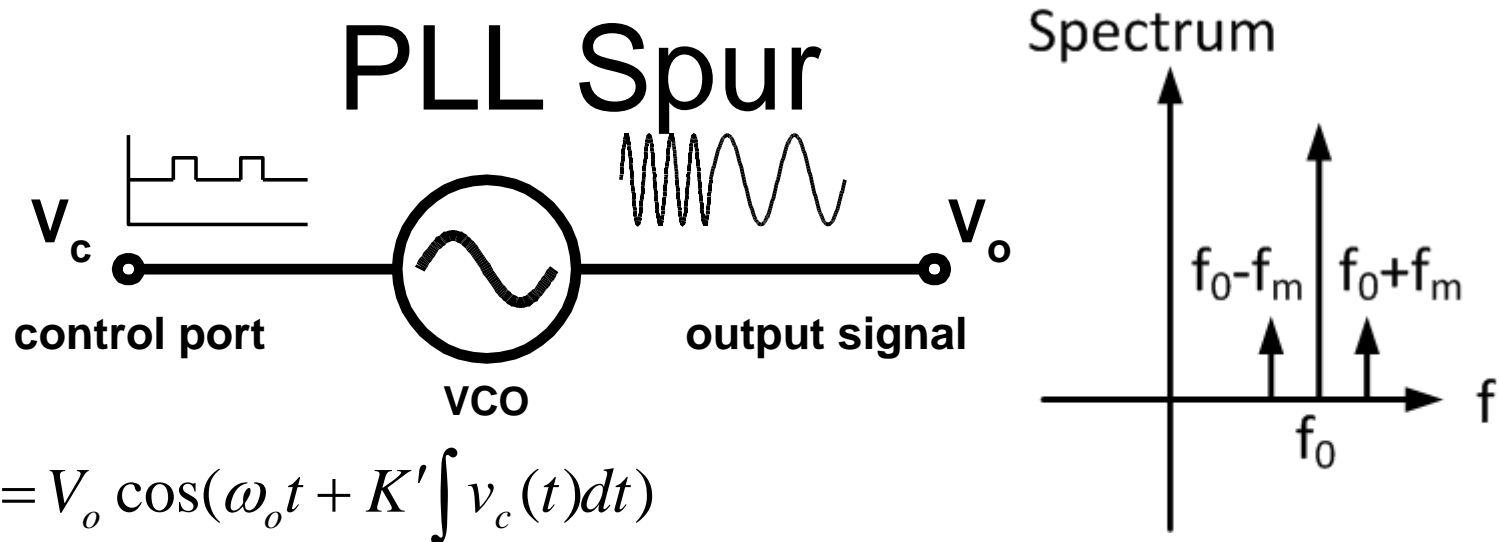- For frequency step, the phase error is zero if $F(0)=\infty$, or there is $1/s$ term in the filter response
- Type II PLL is commonly used since there are two poles at the origin and hence no static phase error for frequency step



$$v_o(t) = V_o \cos(\omega_o t + K' \int v_c(t) dt)$$


$$= V_o \cos(\omega_o t + K \sin \omega_m t)$$

$$\approx V_o (\cos \omega_o t - \sin \omega_o t \cdot K \sin \omega_m t)$$

$$= V_o \left(\cos \omega_o t - \frac{K}{2} \cos(\omega_o - \omega_m) t + \frac{K}{2} \cos(\omega_o + \omega_m) t \right)$$

- VCO output is modulated by coupled signal on control port.
- Two sideband tones at $\pm \omega_m$ away from the center frequency


Type II PLL

 

Active loop filter:

$$F(s) = -\frac{1 + sCR_2}{sCR_1}$$

additional pole
at 0
□ Type II PLL

 

- Closed loop transfer function is given by

$$T(s) = \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\zeta = \frac{R_2}{2R_1} \sqrt{K_{PD}K_{VCO}R_1C/N} \quad \omega_n = \sqrt{K_{PD}K_{VCO}/R_1CN}$$

Settling time

DEFINITION: The time required for the PLL to change its output frequency from $f_{out}(0)$ to $f_{out}(\infty)$ within a frequency error smaller or equal to ε

The closed loop transfer function is:

$$T(s) = \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\varepsilon \geq |f_{out}(t) - f_{out}(\infty)|$$

Changing the division ratio from N to $N + \Delta N$ is equivalent to a frequency step from f_{ref} to $(1 + \Delta N/N)f_{ref}$

The output frequency of the VCO

$$f_{out} = (N + \Delta N)f_{ref} = N \left\{ \left(1 + \frac{\Delta N}{N} \right) f_{ref} \right\}$$

Settling time

The PLL responds to the input frequency step as

$$\Delta f_{out}(s) = f_{out}(s) - Nf_{ref} = \frac{\Delta Nf_{ref}}{N \cdot s} T(s)$$

$$\Delta f_{out}(s) = \Delta Nf_{ref} \frac{(2\zeta\omega_n s + \omega_n^2)}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$$

The steady state frequency can be found using the final value theorem

$$\Delta f_{out}(\infty) = f_{out}(\infty) - Nf_{ref} = \lim_{s \rightarrow 0} s \left[\frac{\Delta Nf_{ref}}{N \cdot s} T(s) \right] = \Delta Nf_{ref}$$

and the lock time can be calculated as:

$$t_{lock} = \left| L^{-1} \{ \Delta f_{out}(s) \} - \Delta f_{out}(\infty) \right| < \varepsilon$$

$$t_{lock} = \left| L^{-1} \{ \phi_e(s) \} \right| < \varepsilon$$

Settling time

$$\phi_e(s) = \frac{s^2 \phi_{in}(s)}{s^2 + 2\zeta\omega_n s + \omega_n^2} = \frac{\Delta\omega}{s^2 + 2\zeta\omega_n s + \omega_n^2} \text{ for frequency step } \phi_{in}(s) = \Delta\omega / s^2$$

Depending on the value of the damping factor ξ , there are three different cases

$0 < \xi < 1$ Underdamped
 $\xi = 1$ Critically Damped
 $\xi > 1$ Overdamped

The poles of the transfer function for each case are


$$\omega_{1,2} = \begin{cases} -\omega_n(\zeta \pm j\sqrt{1-\zeta^2}) & \zeta < 1 \\ -\zeta\omega_n & \zeta = 1 \\ -\omega_n(\zeta \pm \sqrt{\zeta^2-1}) & \zeta > 1 \end{cases}$$

$$\begin{aligned} \Delta\omega_{out}(t) &= \Delta\omega_{in}u(t) - \Delta\omega_{in} \left[\cos\left(\sqrt{1-\zeta^2}\omega_n t\right) \right. \\ &\quad \left. - \frac{\zeta}{\sqrt{1-\zeta^2}} \sin\left(\sqrt{1-\zeta^2}\omega_n t\right) \right] e^{-\zeta\omega_n t} u(t) \quad \zeta < 1 \\ &= \Delta\omega_{in}u(t) - \Delta\omega_{in}(1 - \omega_n t)e^{-\zeta\omega_n t} u(t) \quad \zeta = 1 \\ &= \Delta\omega_{in}u(t) - \Delta\omega_{in} \left[\cosh\left(\sqrt{\zeta^2-1}\omega_n t\right) \right. \\ &\quad \left. - \frac{\zeta}{\sqrt{\zeta^2-1}} \sinh\left(\sqrt{\zeta^2-1}\omega_n t\right) \right] e^{-\zeta\omega_n t} u(t) \quad \zeta > 1. \end{aligned}$$

Fastest settling around $\xi=1$


Phase Frequency Detector

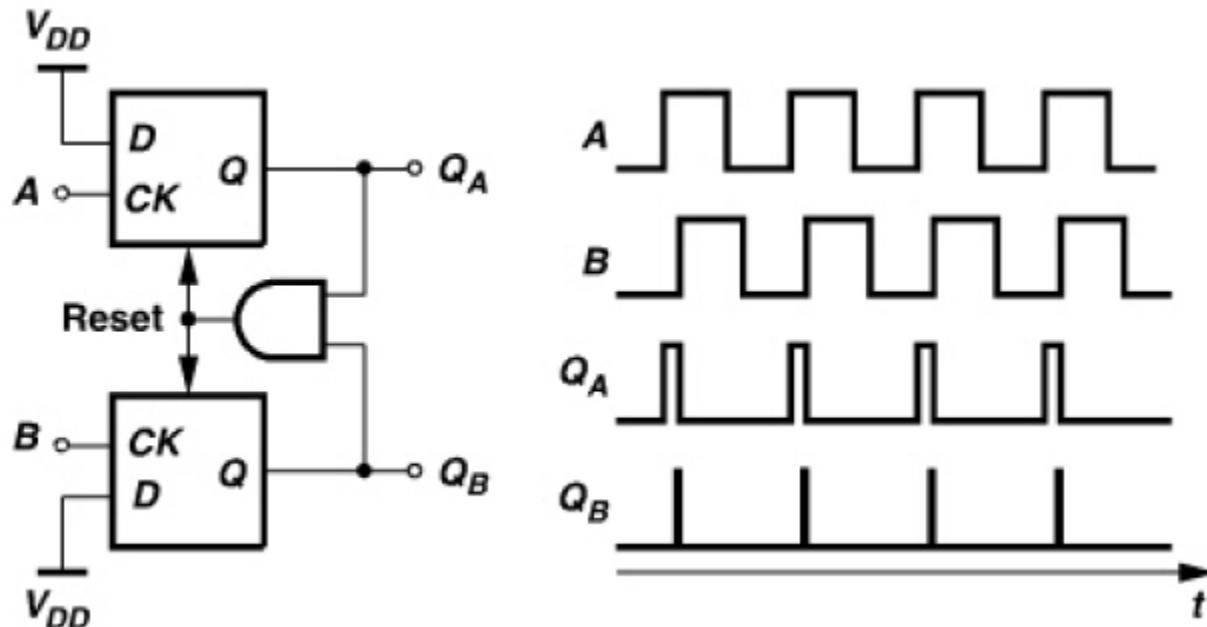- If input and output frequencies are far from each other, phase detection is not enough
- Phase frequency detector (PFD) work with signal edges




Phase Frequency Detector

 - If input and output frequencies are far from each other, phase detection is not enough
- Phase frequency detector (PFD) work with signal edges




Charge Pump PLL

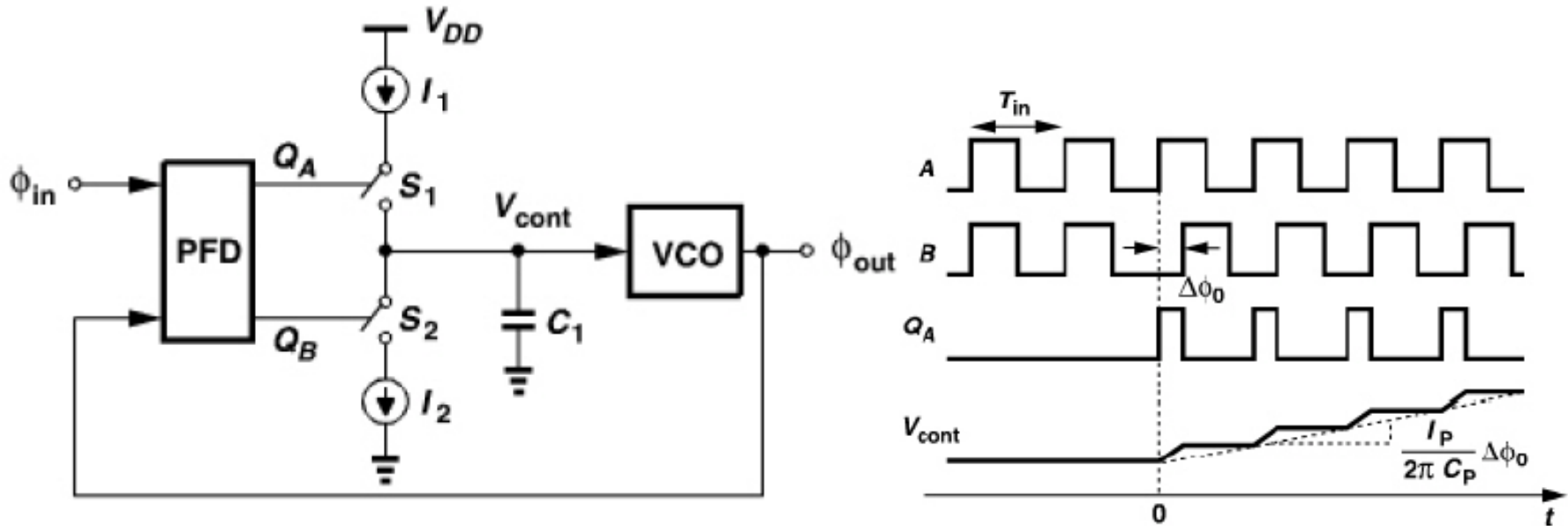

- Note that the current consists of pulses
 - Continuous time approximation will be used ($BW \ll F_{ref}$)

Charge Pump PLL


 


- If the phase difference between two signals is $\Delta\phi_0$, then time difference is $\Delta t = \Delta\phi \times T/2\pi$
 - I_{out} of CP = $I_{cp}\Delta t/T = I_{cp}\Delta\phi/2\pi$
 - Gain of PFD+CP = $I_{out}/\Delta\phi = I_{cp}/2\pi$

Charge Pump PLL

- $G(s) = \frac{I_{cp}}{2\pi} \frac{1}{sC_1} \frac{K_{VCO}}{s}$
- $T(s) = \frac{G(s)}{1+G(s)} = \frac{I_{cp}K_{VCO}}{2\pi C_1 s^2 + I_{cp}K_{VCO}}$
- Two poles at origin lead to unstable response

Charge Pump PLL

 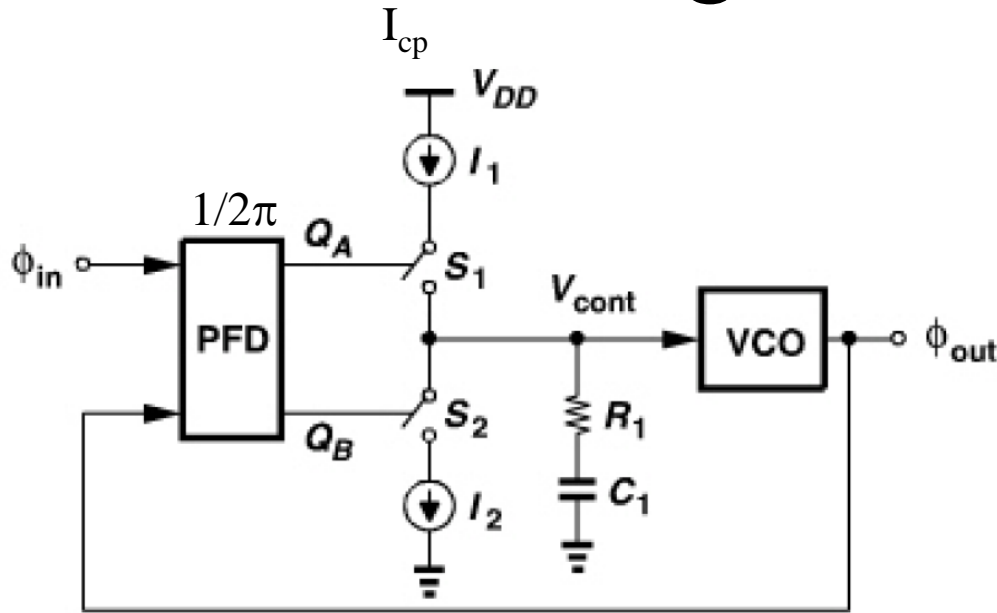




- Zero is added to stabilize response

$$G(s) = \frac{I_{cp}}{2\pi} \frac{1}{sC_1} \frac{K_{VCO}(1+sR_1C_1)}{s}$$


$$T(s) = \frac{G(s)}{1+G(s)} = \frac{(I_{cp}K_{VCO}/2\pi C_1)(1+sR_1C_1)}{s^2 + \left(\frac{I_{cp}K_{VCO}R_1}{2\pi}\right)s + \frac{I_{cp}K_{VCO}}{2\pi C_1}}$$

Charge Pump PLL

- Ripples exist due to R_1

   

Charge Pump PLL

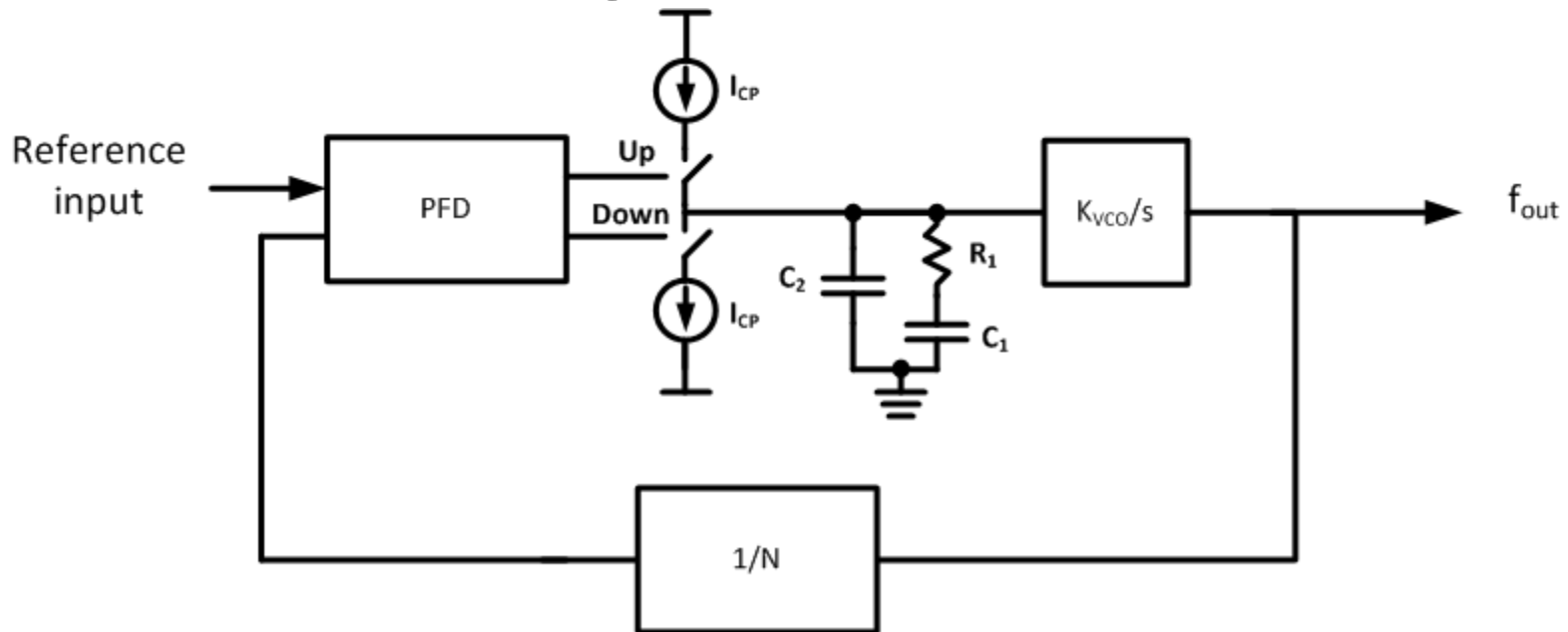


- Addition of R_1 will cause ripples on VCO control line
- Addition of C_2 will help to smooth ripples

$$F(s) = \frac{1}{s(C_1 + C_2)} \cdot \frac{1 + s/\omega_z}{(1 + s/\omega_p)} \quad \omega_z = \frac{1}{R_1 C_1} \quad \omega_p = \frac{1}{R_1(C_1 C_2)/(C_1 + C_2)} \approx \frac{1}{R_1 C_2}$$

Charge Pump PLL

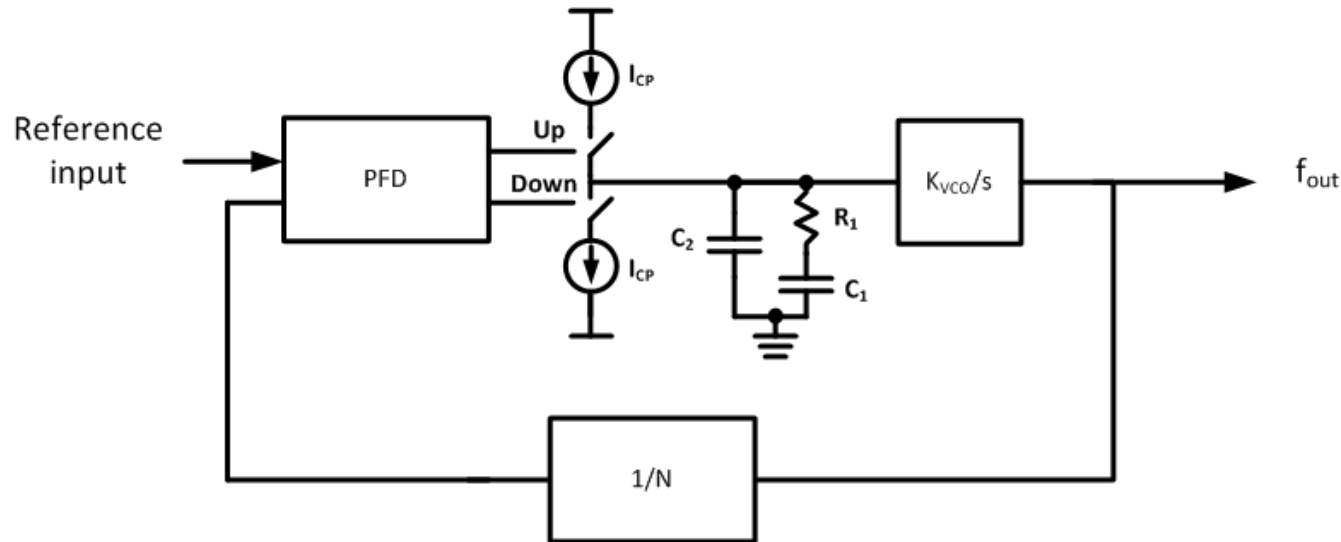- C_2 is added to minimize ripples ($C_2 \ll C_1$)
- T_{OL} is the open loop gain $G(s) \cdot H(s)$



$$T_{ol}(s) = \frac{IK_{VCO}}{2\pi \cdot N \cdot s} \cdot \frac{1}{C_1 + C_2} \cdot \frac{1 + s/\omega_z}{s(1 + s/\omega_p)} = \frac{K_D K_{VCO} (1 + s/\omega_z)}{s^2 (1 + s/\omega_p)} \quad \text{where } K_D = \frac{I}{2\pi \cdot N \cdot (C_1 + C_2)} \approx \frac{I}{2\pi \cdot N \cdot C_1}$$

$$\phi_m = \tan^{-1}\left(\frac{\omega_c}{\omega_z}\right) - \tan^{-1}\left(\frac{\omega_c}{\omega_p}\right)$$


$$\omega_c = K_D K_{VCO} / \omega_z$$

- Max phase margin at $\omega_c = \sqrt{\omega_p \omega_z} = \sqrt{b} \omega_z$, $b = \omega_p / \omega_z$


Charge Pump PLL

$$T_{ol}(s) = G(s)H(s) \approx K_D K_{VCO} \frac{(1 + s/\omega_z)}{s^2(1 + s/\omega_p)} = \omega_n^2 \frac{(1 + s/\omega_z)}{s^2(1 + s/\omega_p)}$$

- Magnitude

 

- Phase

 

- Natural frequency

$$\omega_n = \sqrt{K_D K_{VCO}} = \sqrt{\frac{IK_{vco}}{2\pi C_1 N}}$$

- Crossover frequency

$$\omega_c \approx \frac{\omega_n^2}{\omega_z}$$


- Zero frequency

$$\omega_z = \frac{1}{R_1 C_1}$$

- Pole frequency

$$\omega_p \approx \frac{1}{R_1 C_2}$$

Charge Pump PLL

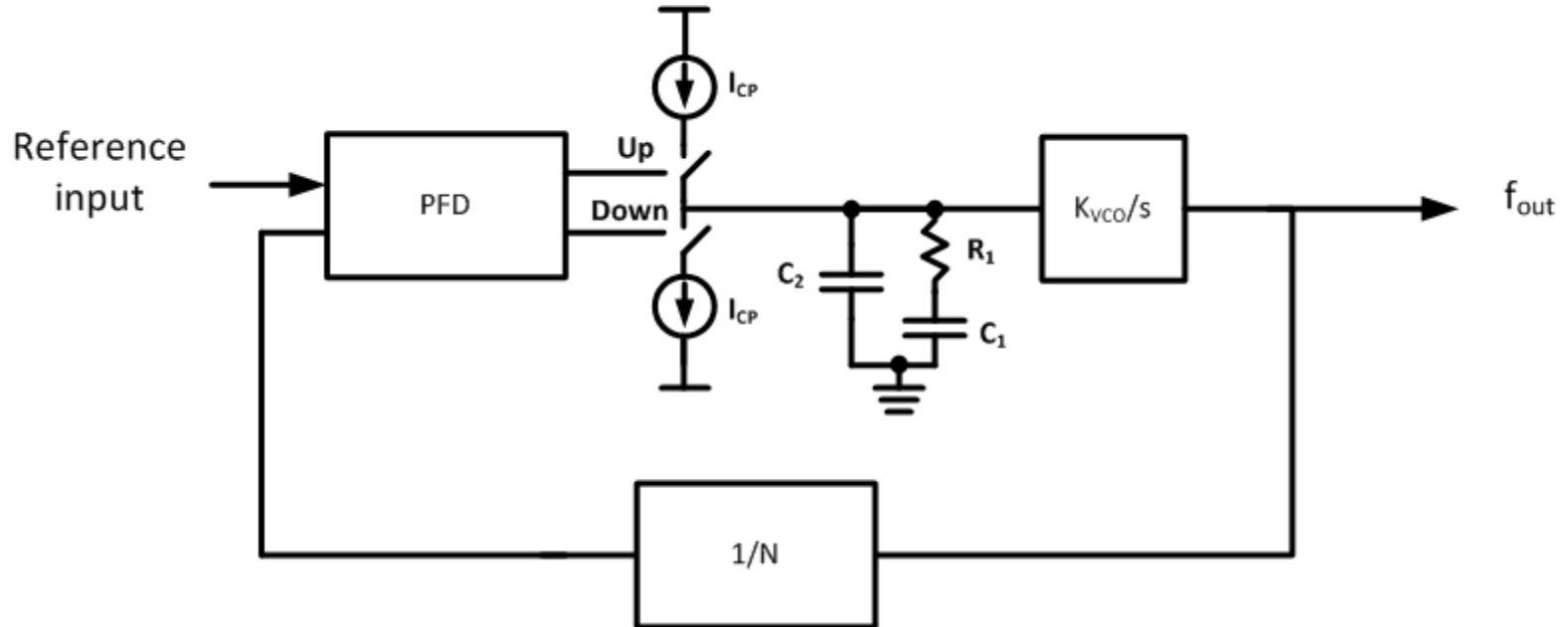




$$G(s) = N\omega_n^2 \frac{(1 + s/\omega_z)}{s^2(1 + s/\omega_p)}, H(s) = 1/N$$

$$T_{cl}(s) = N \frac{(1 + s/\omega_z)}{1 + s/\omega_z + s^2/K_D K_{VCO} + s^3/\omega_p K_D K_{VCO}} \approx N \frac{(1 + s/\omega_z)}{1 + s/\omega_z + s^2/\omega_n^2} \quad (\omega_p \gg \omega_n)$$

$$T_{cl}(s) = N \frac{(\omega_n^2 + s(\omega_n^2/\omega_z))}{s^2 + s(\omega_n^2/\omega_z) + \omega_n^2}, \quad \omega_n = \sqrt{K_D K_{VCO}}, \quad 2\zeta\omega_n = \omega_n^2/\omega_z = \omega_c \Rightarrow \zeta = \omega_c/2\omega_n$$



PFD Dead Zone

   - When phase error approaches zero output of PFD is very narrow pulses
- Due to finite time needed for switches, charge pump doesn't respond and loop is open
 - Loop lose accuracy and will have higher noise
- Delay should be added to ensure minimum pulse out of PFD



Charge Pump Circuit

  - When PLL is in lock condition up and down pulses are the same
 - For a small period of time both current sources are switched ON
- Due to mismatch between up and down current, I_{out} will have a finite value $\neq 0$
- In steady state V_{cont} should be periodic, i.e.
 $V_{cont}(nT) = V_{cont}((n+1)T)$





Charge Pump Circuit Design

- Current sources should have high output resistance
 - Cascode current source are commonly used
- Charge injection and charge sharing could be a problem

Charge Pump Circuit Design

  - Charge sharing when devices turn ON or OFF
 - Charges on NMOS and PMOS gets to V_{cont} node
 - At different values of V_{cont} , Charges on PMOS and NMOS are different




$$\Delta V = \frac{C_{GD2} - C_{GD1}}{C_{GD1} + C_{GD2} + C_2}$$

After charge sharing between C_1 and C_2


$$\Delta V' = \frac{C_{GD2} - C_{GD1}}{C_{GD1} + C_{GD2} + C_2 + C_1}$$

Charge Pump Circuit Design


- Solutions to charge injection issue

 

1- Move switch away from V_{cont}

 


2- Use dummy switch
 $W_5 = 0.5 W_1$

 

3- Use differential pair



Charge Pump Circuit Design

 - Matching between up and down currents is very important
 - Output impedance should be very high
 - Regulated cascode current sources can be used
 - BW of amplifiers A1 and A2 should be very high



Charge Pump Circuit Design

  
- $V_{D6}=V_{D4}$, $V_{D5}=V_{D3}$
 - Effect of channel length modulation is eliminated



Lower Headroom required

Charge Pump Circuit Design

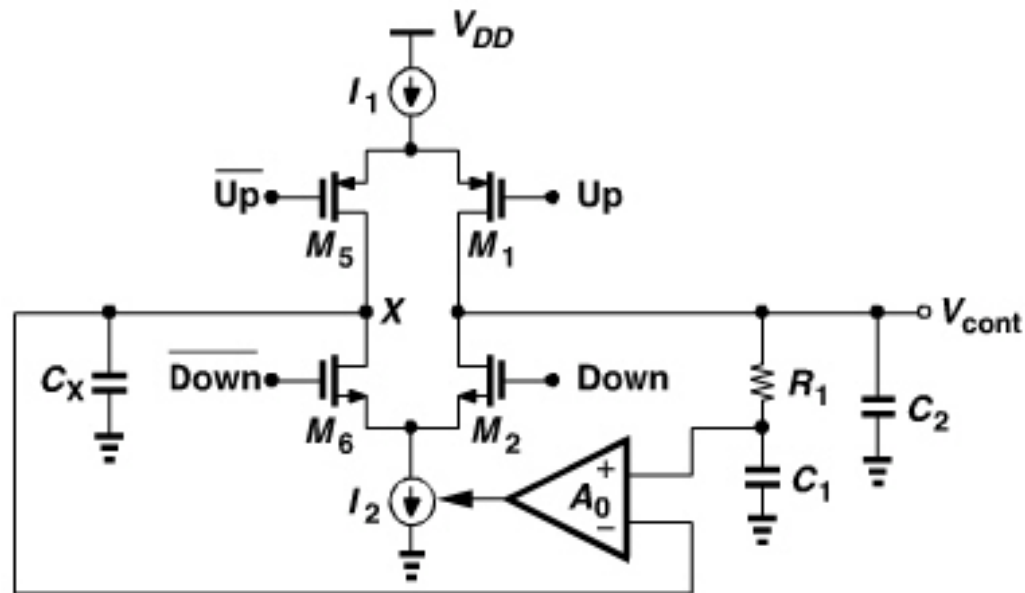- In steady state $I_1 = I_2$ and $V_x = V_{\text{cont}}$



Design Procedure

- How to choose f_{ref}
- If we need to generate 10MHz, 14MHz, 18MHz
 - Note that $f_{\text{out}} = N * f_{\text{ref}}$
 - $F_{\text{ref}} = 2\text{MHz}$
 - For 10 MHz, $N=5$ for 14 MHz, $N=7$ and so on
- $f_{\text{REF}} = \text{GCD}(f_{\text{Carrier}}, f_{\text{Spacing}})$

Design Procedure

$$T_{ol}(s) = \omega_n^2 \frac{(1 + s/\omega_z)}{s^2(1 + s/\omega_p)} \approx \frac{(2\zeta\omega_n s + \omega_n^2)}{s^2} \quad T_{cl}(s) \approx N \frac{(\omega_n^2 + s(\omega_n^2/\omega_z))}{s^2 + s(\omega_n^2/\omega_z) + \omega_n^2}, \quad (\omega_p \gg)$$

$$\zeta = \frac{\omega_n}{2\omega_z} = \frac{\omega_c}{2\omega_n} \quad \omega_c = \frac{\omega_n^2}{\omega_z}$$

- 3 Unknowns ($\omega_n, \omega_z, \omega_p$) note that ζ is a function of ω_n, ω_z
- 3 Equations $\zeta=1, \omega_n^2 = \omega_z \omega_p, \omega_c < \omega_{REF}/10$

1. Determine the loop bandwidth

$$\omega_c = \omega_{REF}/10$$

2. Choose damping factor $\zeta=1$

3. Calculate natural frequency

$$\omega_n = \omega_c/2\zeta$$

4. Calculate $\omega_z = \omega_n/2\zeta = \omega_c/4\zeta^2$

5. Calculate $\omega_p = \omega_c \times 4\zeta^2$ (Remember that $\omega_c = \sqrt{\omega_p \omega_z}$)

Design Procedure

- Now we have ω_n , ω_z , ω_p

$$\omega_n = \sqrt{K_D K_{VCO}} = \sqrt{\frac{IK_{vco}}{2\pi C_1 N}} \quad \omega_z = \frac{1}{R_1 C_1} \quad \omega_p \approx \frac{1}{R_1 C_2}$$

- 5 unknowns and 3 Equations (I , K_{vco} , R_1 , C_1 , C_2)
 - Choose any 2 variables and calculate the rest
 - Use average value of N

Example

- Design PLL that generate frequencies from 2.45GHz to 2.55 GHz with 0.5 MHz channel spacing
 - $F_{\text{ref}}=0.5\text{MHz}$, $\omega_{\text{ref}}=3.14 \text{ Mrad/s}$ ($N=4900$ to 5100)
 - $\omega_c=\omega_{\text{ref}}/10=0.314 \text{ Mrad/s}$
 - $\zeta=1$
 - $\omega_n = \omega_c/2\zeta=0.157 \text{ Mrad/s}$
 - $\omega_z = \omega_n/2\zeta = \omega_c/4\zeta^2=0.0785 \text{ Mrad/s}$
 - $\omega_p = \omega_c \times 4\zeta^2=1.256 \text{ Mrad/s}$ (*Remember that $\omega_c = \sqrt{\omega_p \omega_z}$*)
 - Choose $I=100\mu\text{A}$, $K_{\text{vco}}=1\text{Grad/V}$

$$\omega_n = \sqrt{\frac{IK_{\text{vco}}}{2\pi C_1 N}} \Rightarrow C_1 = 129\text{PF} \quad \omega_z = \frac{1}{R_1 C_1} \Rightarrow R_1 = 100\text{k}\Omega \quad \omega_p \approx \frac{1}{R_1 C_2} \Rightarrow C_2 = 8\text{PF}$$