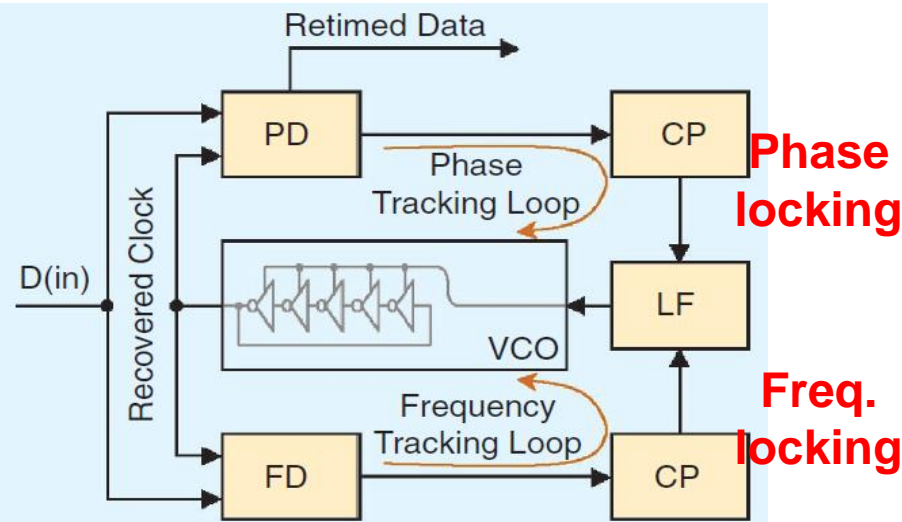


# **Clock and Data Recovery: Architectures**

*Lecture 10*


# Reference-less PLL-based CDRs



- The freq. detector (FD) provides an output proportional to the frequency error between  $D_{in}$  & VCO output  $\rightarrow$  no need for external clock frequency
- At start-up, the FD drives the VCO frequency close to  $D_{in}$  then PD takes over to lock on  $D_{in}$  phase:
- **Aided Acquisition** allows increasing loop locking range without sacrificing the VCO ripple (or increasing  $f_{BB}$ )
- The PD & FD may interfere during transferring over to the PD mode, also FD might be confused with long CIDs  $\rightarrow$  control voltage ripple or failure/false lock


[Ref]: "Architectures for Multi-Gigabit Wire-Linked Clock and Data Recovery," *IEEE Circ. & Sys. Magazine*, 2008
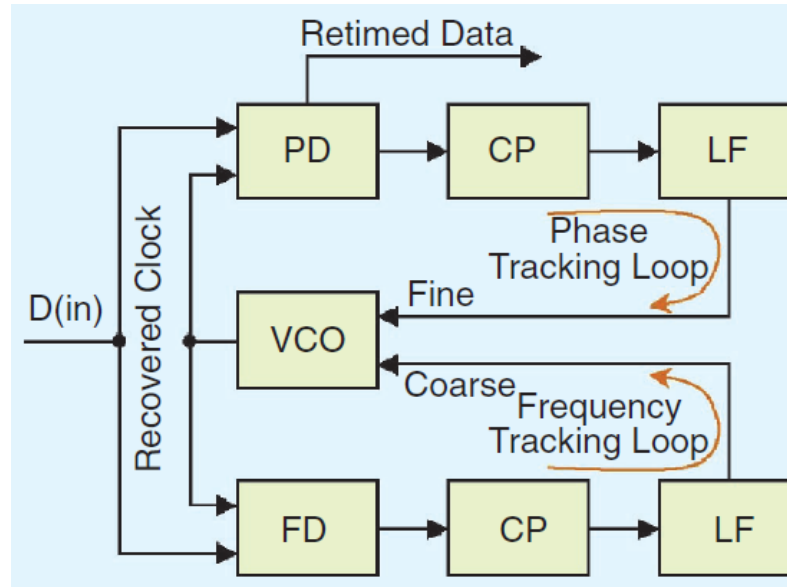
## Reference-less PLL-based CDRs (Cont'd)




- Each loop can drive its own CP & loop filter
- Frequency tracking is typically necessary at power up or to track slow temperature drift  $\rightarrow$  speed is not important
- Loop BW of frequency tracking loop should be  $\ll$  BW of phase tracking loop
- Large BW of phase tracking loop improves CDR jitter tolerance
- Disadvantage: large area  $\rightarrow$  Could combine using analog & digital loop filters
 
# Frequency Detectors (Quadri-correlator)



$$X_A(t) = \frac{A_1 A_2}{2} \cos(\omega_1 - \omega_2)t$$

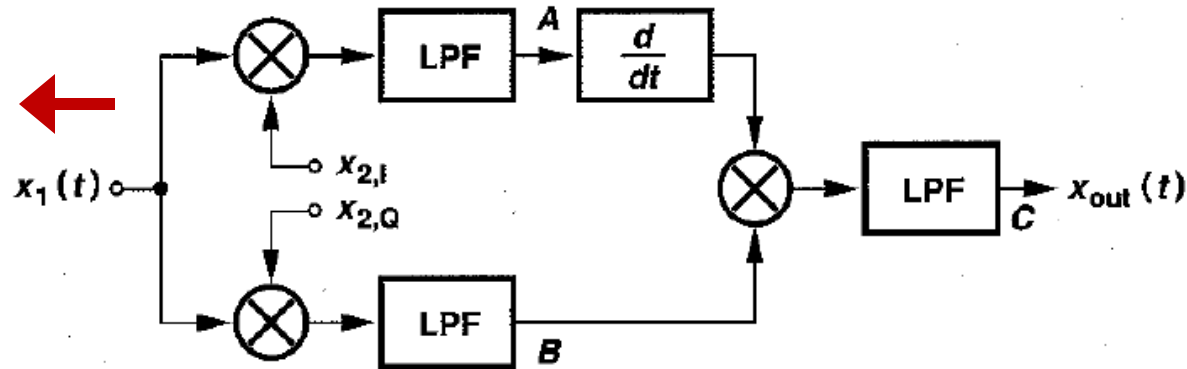
$$X_B(t) = \frac{A_1 A_2}{2} \sin(\omega_1 - \omega_2)t$$



$$X_{out}(t) = LPF \left\{ - \left( \frac{A_1 A_2}{2} \right)^2 (\omega_1 - \omega_2) \times \left( \frac{1}{2} - \frac{\cos 2(\omega_1 - \omega_2)t}{2} \right) \right\}$$

- $X_1(t)$  has to have a spectral line at  $f_b \rightarrow$  Edge detector
- Close to lock, the component at  $2(\omega_1 - \omega_2)$  may cause a large ripple at the output

# Random Data Balanced Quadri-correlator

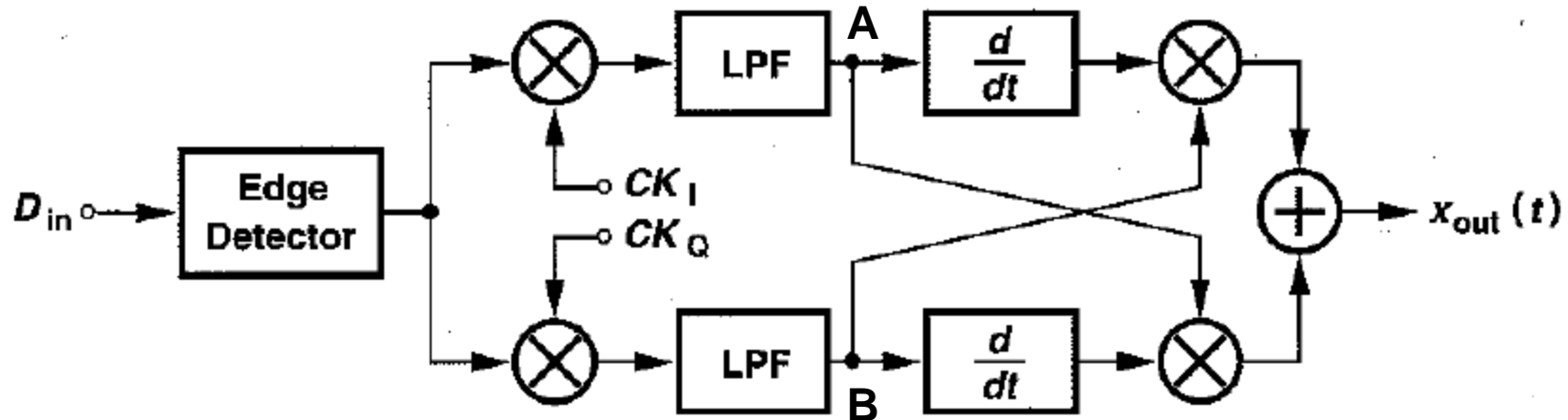

$$X_A(t) = \frac{A_1 A_2}{2} \cos(\omega_1 - \omega_2)t$$


$$X_B(t) = \frac{A_1 A_2}{2} \sin(\omega_1 - \omega_2)t$$





$$X_{out}(t) = -\left(\frac{A_1 A_2}{2}\right)^2 (\omega_1 - \omega_2) \times \sin^2(\omega_1 - \omega_2)t \\ - \left(\frac{A_1 A_2}{2}\right)^2 (\omega_1 - \omega_2) \times \cos^2(\omega_1 - \omega_2)t$$

- The balanced quadri-correlator suppresses the component at  $2(\omega_1 - \omega_2)$  improving the lock behavior
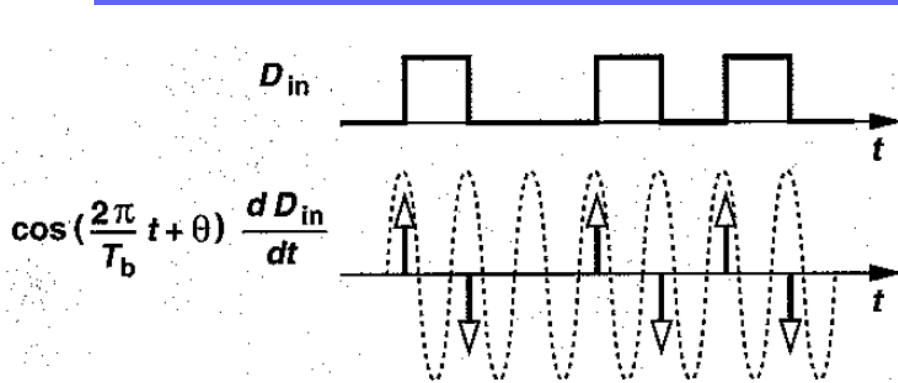
# Creating a Spectral line at $f_b$ (Edge Detection )




  Differentiation is a linear operation:  
will not create a spectral line




- Random data  $D_{in}$  doesn't include a spectral line at  $f_b$
- Differentiating  $D_{in}$  still produces 0 when correlated with  $\cos(\omega_b t + \theta) \rightarrow$  No Edge detection
- If the  $-ve$  impulses are converted to  $+ve$  impulses the correlation will yield a non-zero value
- Differentiation & Rectification produces a spectral line at  $f_b \rightarrow$  Edge detection

# Digital Quadri-correlator

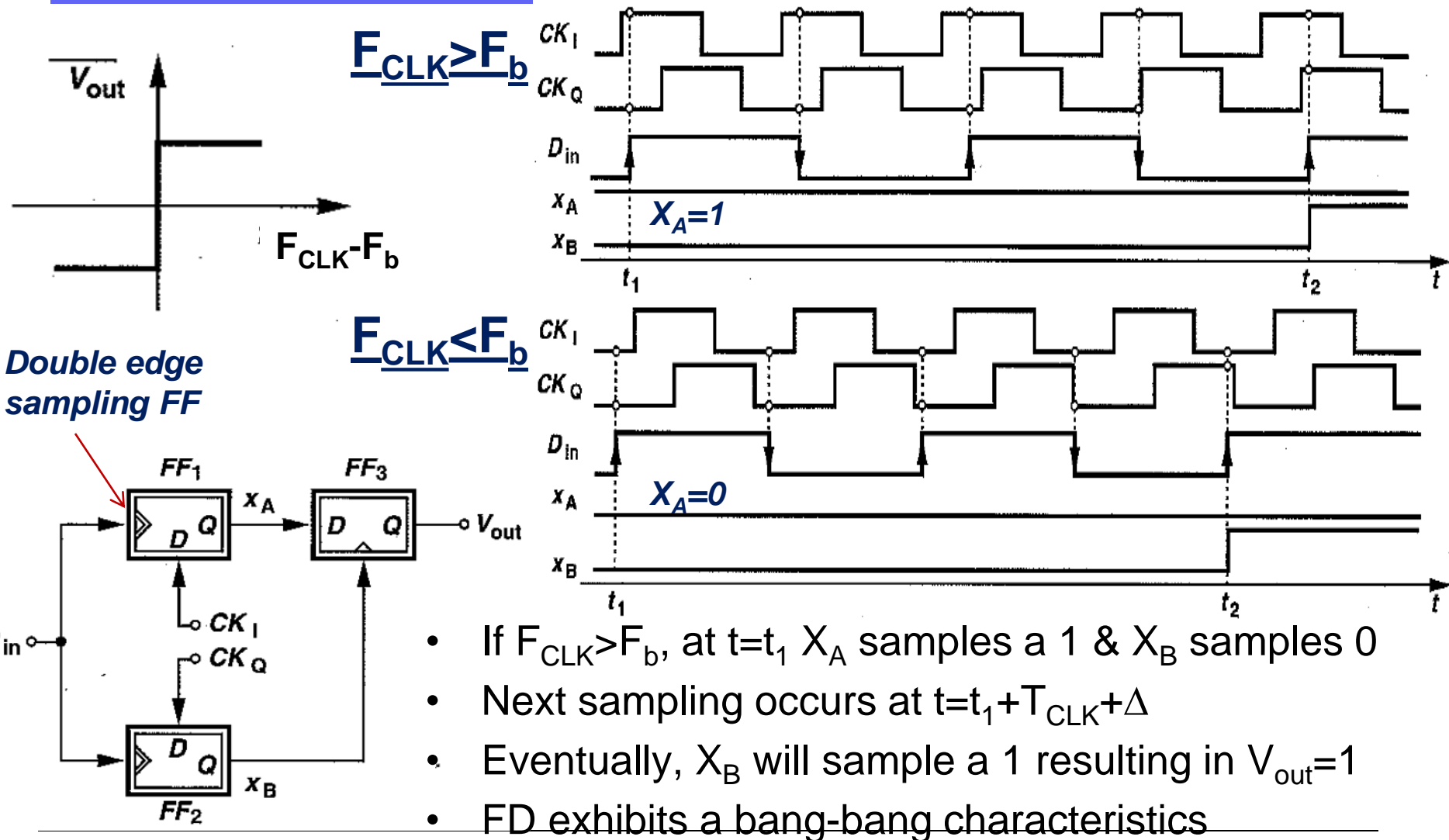

- If  $F_{CLK} > F_b$ , at  $t=t_1$   $X_A$  samples a 1 &  $X_B$  samples 0
- Next sampling occurs at  $t=t_1 + T_{CLK} + \Delta$
- Eventually,  $X_B$  will sample a 1 resulting in  $V_{out}=1$
- FD exhibits a bang-bang characteristics
 
## PLL-based CDRs with External Reference Clock




- *Advantages:*
  - ✓ *Availability of separate  $VCO_2$  control  $\rightarrow$  faster acquisition time for phase locking*
- *Disadvantages:*
  - X *Sensitive to mismatches between  $VCO_1$  &  $VCO_2$  ( $f_1 \neq f_2$ )*
  - X *If the Tx has finite frequency offset the 2 VCOs will be running at different frequencies  $\rightarrow$  frequency pulling*

- Freq. tracking loop locks  $VCO_2$  output to  $F_{ref} * M$
- $VCO_2$  control voltage is applied to  $VCO_1$  ( $VCO_2$  is a replica of  $VCO_1$ )
- This centers  $VCO_1$  around the input data rate & allows the phase tracking loop to lock the phase of  $VCO_1$  to  $D_{in}$
- The gain of the phase tracking loop must be (fine step)  $\ll$  the gain of the frequency tracking loop (coarse step)



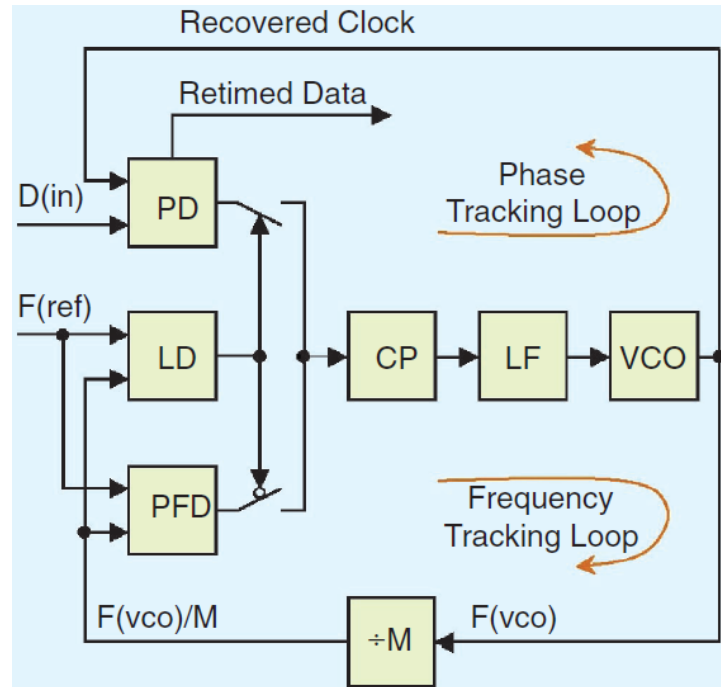
# PLL-based CDRs with External Reference Clock



- *Advantages:*
  - ✓ *Eliminates the extra CP, LF, & VCO  $\rightarrow$  no mismatch issues*
- *Disadvantages:*
  - X *Transition from freq. to phase tracking loops might cause disruption to VCO control causing freq. shift  $\rightarrow$  failure to lock or ripple on VCO control*

- A lock detector (LD) can be used to sequentially switch between the freq. & phase tracking loops
- When the LD senses that the difference between  $F_{ref}$  and  $F_{vco}/M$  is small it switches to the phase tracking loop


# Delay Lock Loop (DLL)-based CDR

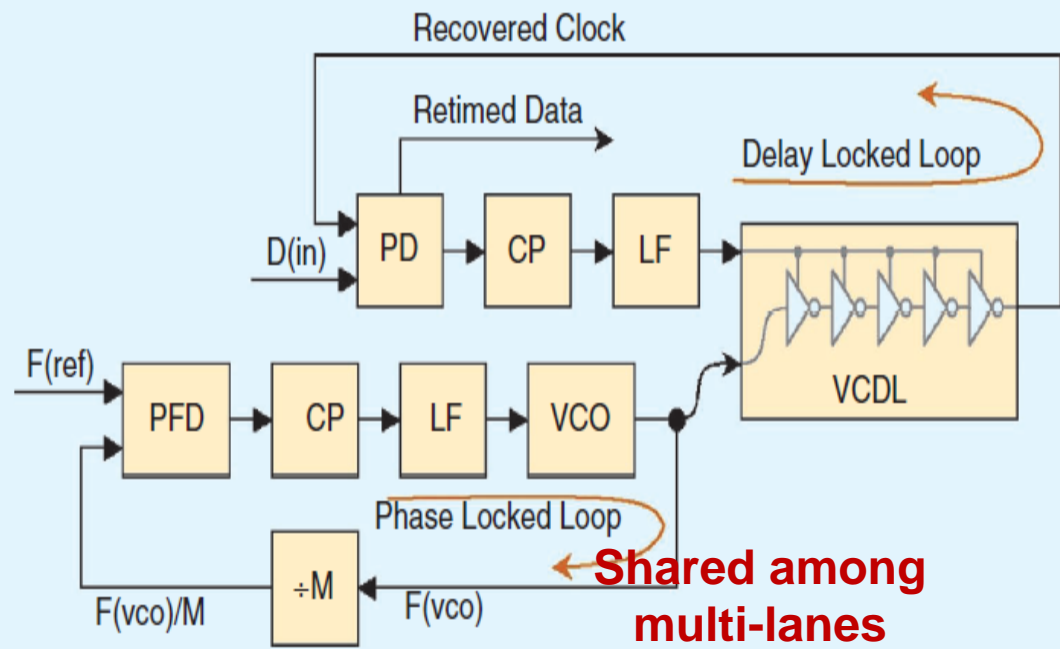

- **Advantages:**
  - ✓ VCDL directly alters the clk phase  $\rightarrow$  no freq. to phase integration (1 less pole): more stable
  - ✓ Faster locking
  - ✓ No jitter accumulation
- **Disadvantages:**
  - X Limited capture range

- Freq. tracking loop provides a high speed clk instead of a voltage
- Phase tracking loop uses a voltage-controlled delay line (VCDL) to lock to the phase of  $D_{in}$
- $F_{ref} * M$  must be the same as the input data rate, suitable for source-synchronous applications (chip-to-chip)

# Phase Interpolator (PI)-based CDR

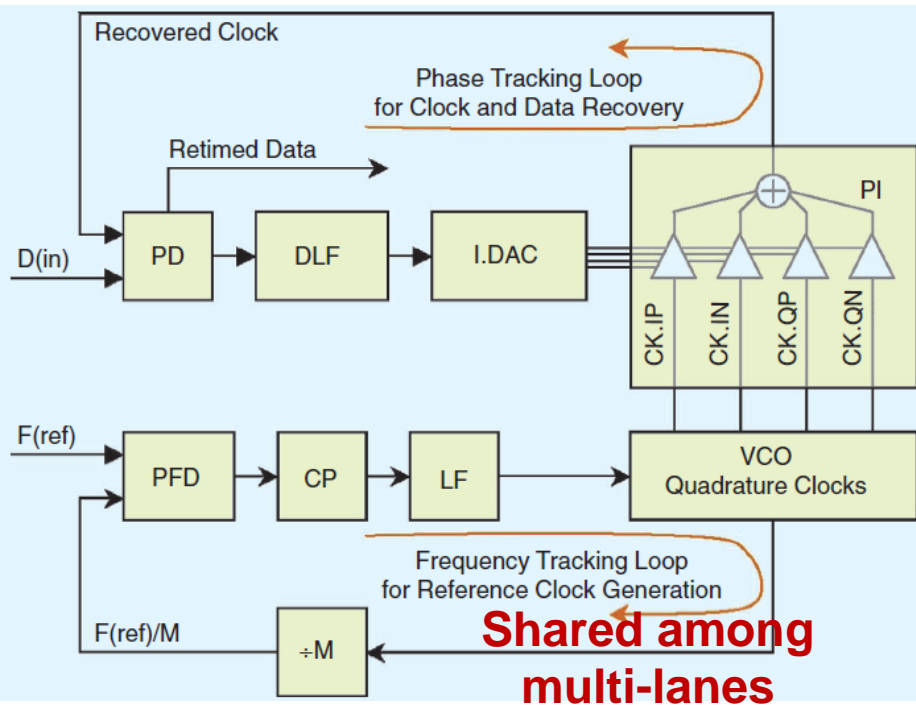

- *Advantages:*
  - ✓ *Increases system stability*
  - ✓ *Faster locking*
  - ✓ *No jitter accumulation*
  - ✓ *No jitter peaking (if loop latency is small)*
  - ✓ *Can operate over limited range of frequency offset*
- *Disadvantages:*
  - X *Need to deliver quadrature clks across the chip*

- Similar to the DLL, but uses a digital loop filter DLF, current DAC, PI
- Output of the I-DAC is a current  $\propto$  to DLF output  $\rightarrow$  controls how much gain is assigned to the I-clk & Q-clk to control the recovered clk phase

# Ideal Phase Interpolation

Starting with 2 quadrature clocks, with amplitude A:

$$CK_I = A \cos(\omega t)$$

$$CK_Q = A \cos(\omega t - 90) = A \sin(\omega t)$$

For any desired angle  $\varphi$ , with fixed amplitude A:

$$CK = A \sin(\omega t - \varphi)$$


$$CK = A \sin(\omega t) \cos(\varphi) - A \cos(\omega t) \sin(\varphi)$$

$$CK = A_I CK_Q + A_Q CK_I \text{ (phase interpolation)}$$

$$A_I = \cos(\varphi) \text{ \& } A_Q = \sin(\varphi) \rightarrow A_I^2 + A_Q^2 = 1 \text{ for constant amplitude (circle)}$$

$$\varphi = \tan^{-1} \left( \frac{A_Q}{A_I} \right)$$

 In practice, most designs use a simpler implementation which results in  $A_I + A_Q = 1 \rightarrow$  diamond shape



# Jitter of Digital PI-based CDRs

- In CDRs with digital loop filters dithering jitter is proportional to the feedback loop delay and phase resolution of the PI
- Dithering jitter is the main source of the deterministic jitter in PI CDRs
- A decimation filter that counts early or late decisions of the phase detector is employed to reduce the dithering jitter

$$\theta_{\text{dither}} = 2 \cdot m \cdot K_{\text{DLL}} \cdot K_{\text{PI}}$$

$m$  is the loop latency in the control loop (in UI),  $K_{\text{PI}}$  is the phase step (or resolution) of the PI, and  $K_{\text{DLL}}$  is the decimation filtering factor

- Slew rate SR (maximum rate at which the loop updates the PI phase) defines its tracking capability

$$\text{SR} = \frac{\text{Phase step}}{\text{Phase update period}} = K_{\text{PI}} \cdot f_{\text{update}} \cdot K_{\text{DLL}}$$


where  $f_{\text{update}}$  is the clock frequency of the digital CDR control blocks

- SR should be  $>$  the phase changing rate caused by input sinusoidal jitter  $A_{\text{mod}}$


$$A_{\text{mod}} < \frac{\text{SR}}{2\pi \cdot f_{\text{jitter}}} = \frac{K_{\text{PI}}}{2\pi} \cdot \frac{f_{\text{update}} \cdot K_{\text{DLL}}}{f_{\text{jitter}}}$$

where  $f_{\text{jitter}}$  is the frequency of the jitter modulated on the incoming data

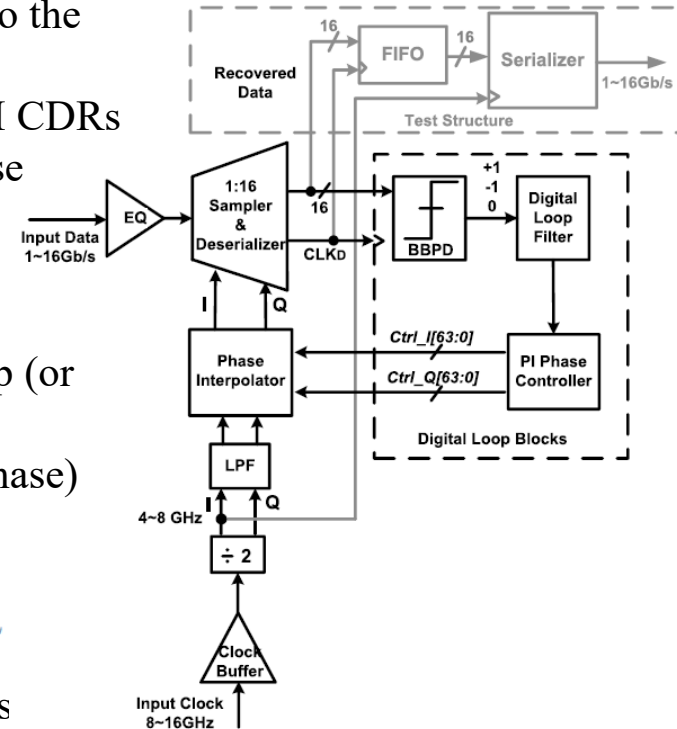
G. Wu et al., "A 1–16 Gb/s All-Digital Clock and Data Recovery With a Wideband High-Linearity Phase Interpolator," in IEEE Transactions on Very Large Scale Integration (VLSI) Systems, vol. 24, no. 7, pp. 2511-2520, July 2016.


 
# JSSC 2006: A 10-Gb/s 5-Tap DFE/4-Tap FFE Transceiver in 90-nm CMOS Technology



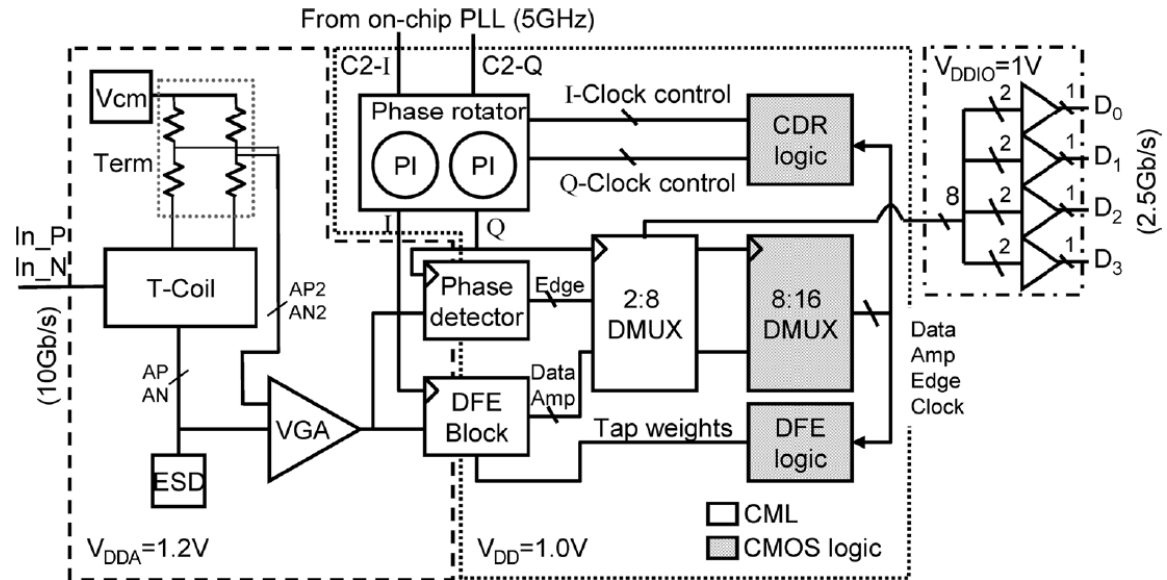Proper choice of T-coil parameters provides  $BW \sim 2.2 / R_L C_L$





- Phase interpolation (PI) by phase rotators controlled by a digital CDR loop generates the I & Q and clocks used to sample the centers and edges of the data bits
- Half-rate CDR logic converts the data and edge samples into early and late signals which are digitally filtered to generate INC/DEC signals that control the PI
- Digital PI must be precise not to degrade the timing of the recovered clock

J. F. Bulzacchelli et al., "A 10-Gb/s 5-Tap DFE/4-Tap FFE Transceiver in 90-nm CMOS Technology," in IEEE Journal of Solid-State Circuits, vol. 41, no. 12, pp. 2885-2900, Dec. 2006.
 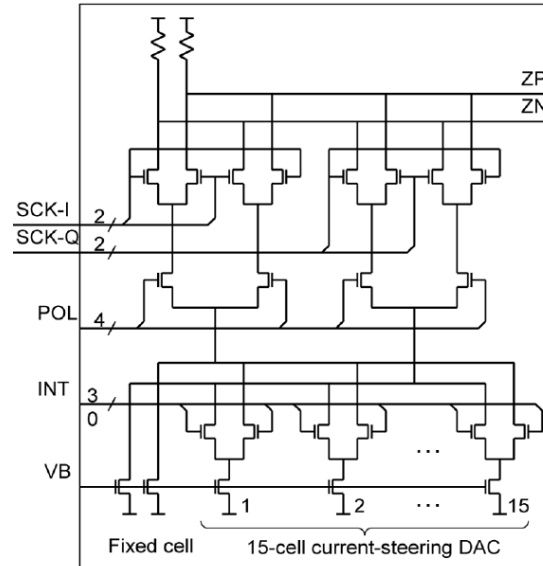
# JSSC 2006: A 10-Gb/s 5-Tap DFE/4-Tap FFE Transceiver in 90-nm CMOS Technology



- The phase rotator is driven by two differential quadrature clock phases
- The circuit selects the quadrant then interpolates to generate 16 phases per quadrant for a total of 64 on a  $360^\circ$  (2 UI) circle




- The interpolator uses a current-steering DAC as tail currents
- Rotator has a diamond-shaped, due to constant total interpolator tail current  $\rightarrow$  non uniform angles close to quadrant edges
- The current-steering DAC has 2 fixed cells of half-size  $\rightarrow$  0.5:15.5 to 15.5:0.5
- Fixed cells improve rotator settling time
- 15 steering DAC cells are not uniform; the largest cells are switched near the quadrant boundaries



 
 
# A 10-Gb/s 5-Tap DFE/4-Tap FFE Transceiver in 90-nm CMOS Technology: JSSC 2006



6 GHz

 


2 GHz

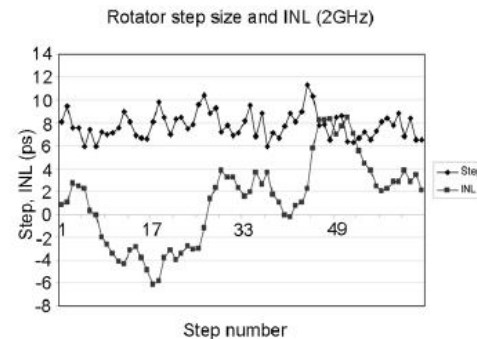 

- Slew-rate-control buffers are required to ensure the signals going to the PI are sinusoidal for proper interpolation
- PI step scales with data rate since it is  $360/\text{no. of states}$ :
  - At 2GHz step = 2.7ps
  - At 6 GHz step = 8ps
- Amplitude variation is periodic, CDR samplers not sensitive to amplitude variation



# Phase Interpolator (PI)-based CDR

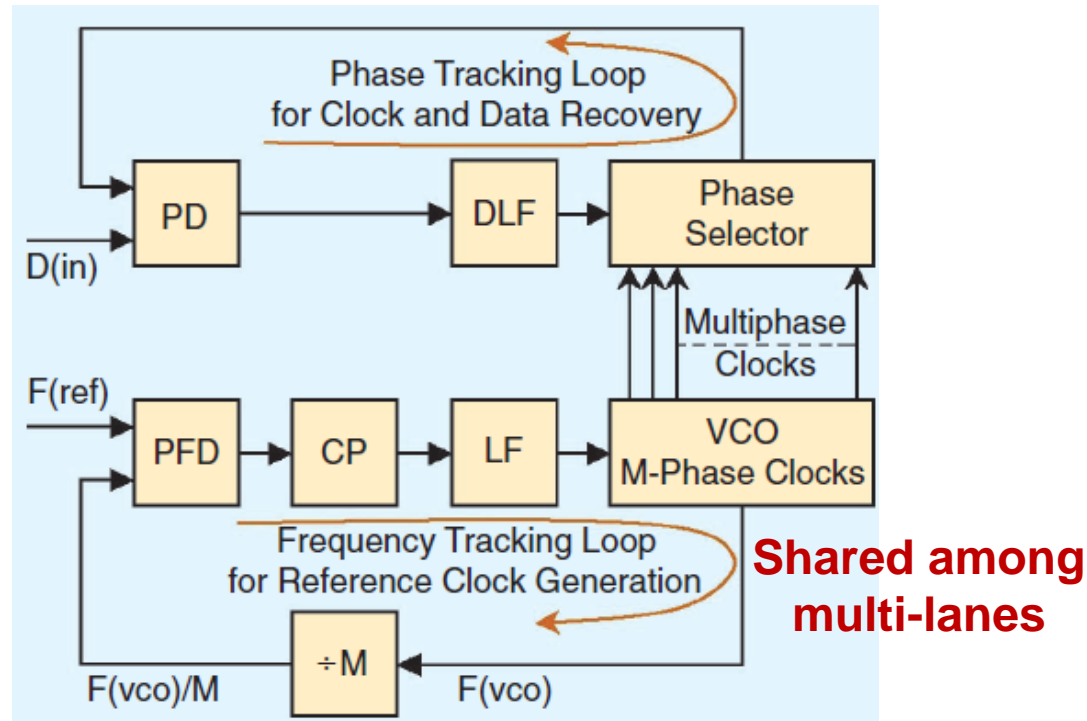

- I-DAC and PI replaced with a phase selector → All digital implementation (more robust to PVT variations)
- Discrete phase steps
- Independent phase & frequency tracking loops → simplifies loop BW/stability Requirements


# All Digital PLL-based CDRs

---

- In deep submicron technologies Analog CDRs suffer from :
  - Insufficient voltage headroom
  - Large area occupied by integral loop capacitor
    - Design sensitive to leakage currents
- All digital CDRs:
  - Easy porting between process nodes
  - Offers easy method to program loop behavior  $K_{\text{prop}}$  &  $K_{\text{int}}$   
→ settling, bandwidth, stability, jitter tolerance...
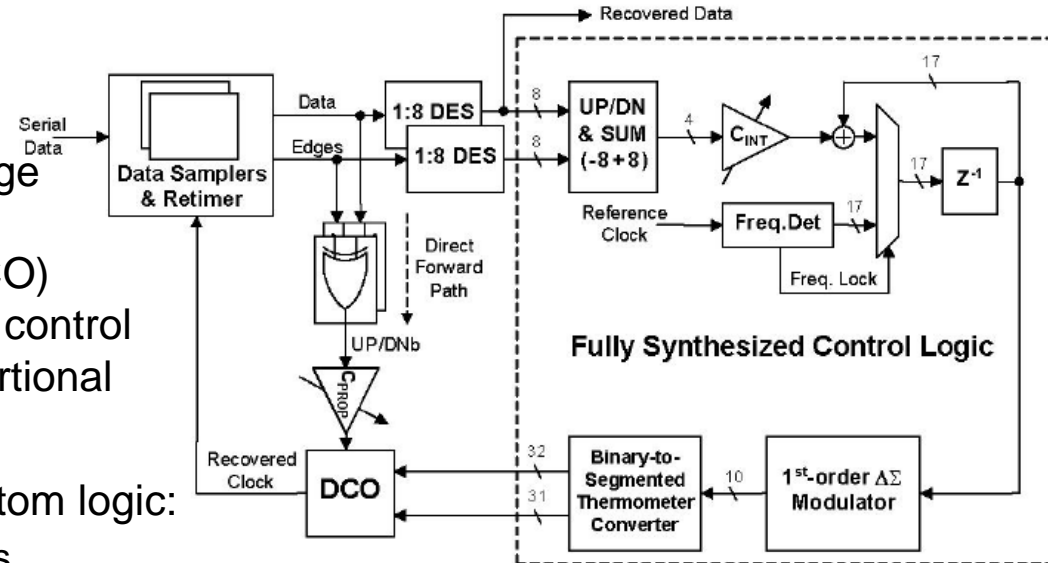
# ISSCC 2007: All-Digital CDR with a 10-bit Monotonic DCO


- The CDR consists of:
  - Bang-band phase detector
  - 1:8 de-serialiers for data and edge samples
  - Digitally controlled oscillator (DCO)
- High speed UP/Down signals directly control the DCO frequency to form the proportional path
- The integral path is formed by the custom logic:
  - Generates low speed UP/Down signals
  - 17 bit Loop integrator synthesized using a digital IIR filter
  - A digital 1<sup>st</sup> order delta-sigma modulator converts the 17 bit frequency code to a dithered 10 bit DCO code
  - To guarantee the monotonicity of the DCO the 10 bits control code is converter to a segmented thero-mometer code (32 + 31) bits.
- Frequency detection is also done by the custom logic block
- DSM (delta-sigma modulator) improves the resolution by dithering (17→10 bits)




D. -H. Oh, D. -S. Kim, S. Kim, D. -K. Jeong and W. Kim, "A 2.8Gb/s All-Digital CDR with a 10b Monotonic DCO," 2007 IEEE International Solid-State Circuits Conference. Digest of Technical Papers, 2007, pp. 222-598
 
# ISSCC 2007: All-Digital CDR with a 10-bit Monotonic DCO

- DCO is a ring oscillator with the supply connected through a digitally controlled resistor
- Resistor is made up of 1024 PMOS transistor switches that control the DCO frequency
- A segmented thermometer (32 rows & 32 columns) control is used for switching to prevent glitches during the code transitions
  - Full thermometer would require 1024 control line
- The DCO tuning steps ( $f_{\text{step}} = f_{n+1}/f_n$ ) should be constant to maintain the same loop stability, bandwidth across different data rates
- Equally spaced tuning steps mean that the frequency increases exponentially → not easy to achieve
- PMOS transistors are inserted between the rows to produce an overall resistance change close to an exponential, frequency can be tuned exponentially



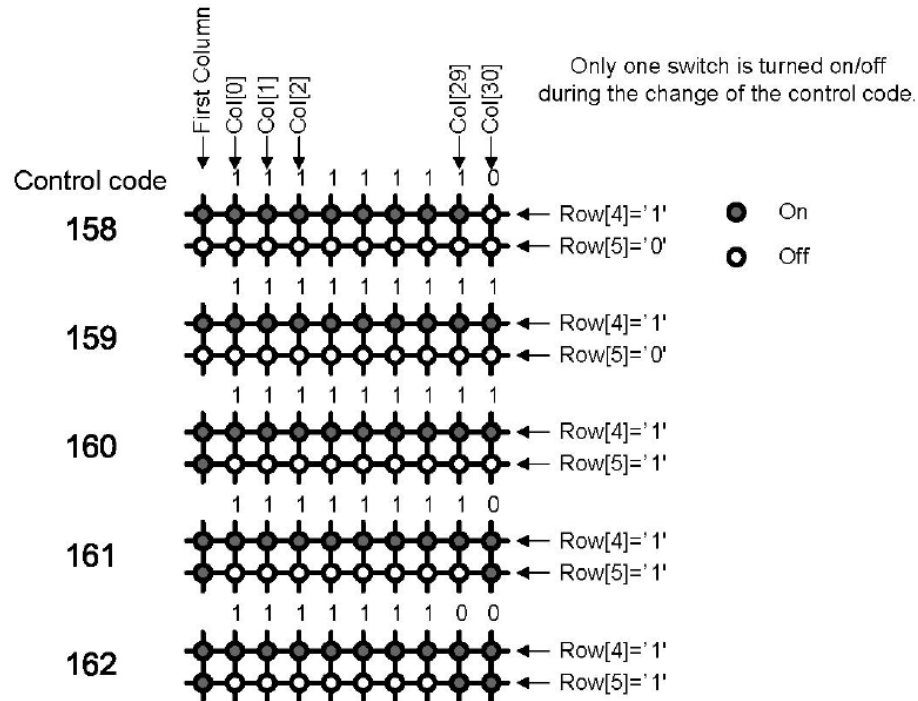
# ISSCC 2007: All-Digital CDR with a 10-bit Monotonic DCO



- A cell in an **even** row is turned on when the corresponding column **code is 1** and a cell in an **odd** row is turned on when the corresponding column **code is 0**
- A cell in the **first column** is turned on when the corresponding row **code is 1**
- DCO has 16 tuning cells for the 2-b forward path that receive the proportional path UP/DN signal

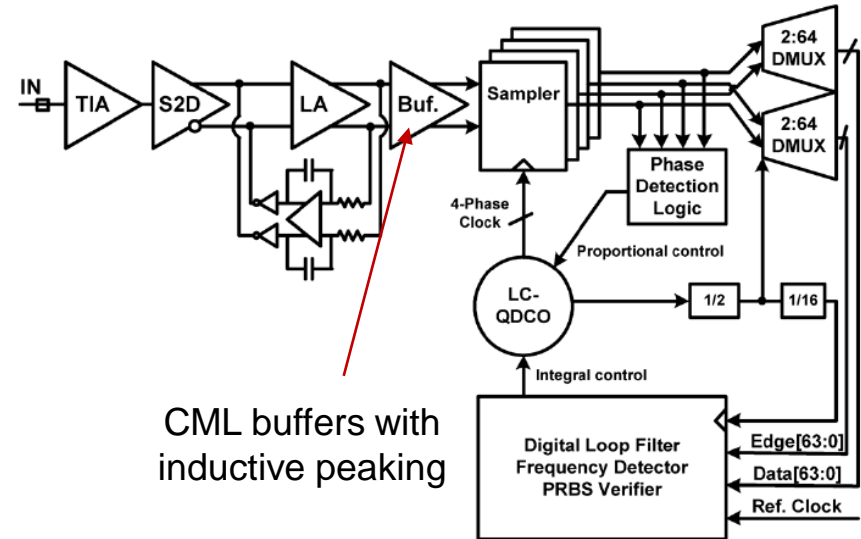
# JSSC 2015: 26.5 Gb/s Optical Receiver With All-Digital Clock and Data Recovery

- Optical front-end consists of TIA, a single-to-differential converter (S2D), an limiting amplifier (LA) with DC offset cancellation
- Output buffers are necessary to drive the large capacitive load of the samplers
- CDR employs a half rate architecture with 2 data and 2 edge samplers (4-phase clock) for phase detection
- This is followed by a 2 to 64 bit de-multiplexers that generate the 64-bit parallel data and edge information Data[63:0] & Edge[63:0]
- The proportional high speed pulses are feed directly to the LC-QDCO (quadrature digitally controlled oscillator)
- The integral path is implemented using a low speed ( $F_b/64$ ) 64-bit parallel digital phase detector & loop filter
- Frequency detection is also done in the digital




S. -H. Chu et al., "A 22 to 26.5 Gb/s Optical Receiver With All-Digital Clock and Data Recovery in a 65 nm CMOS Process," in IEEE Journal of Solid-State Circuits, vol. 50, no. 11, pp. 2603-2612, Nov. 2015.
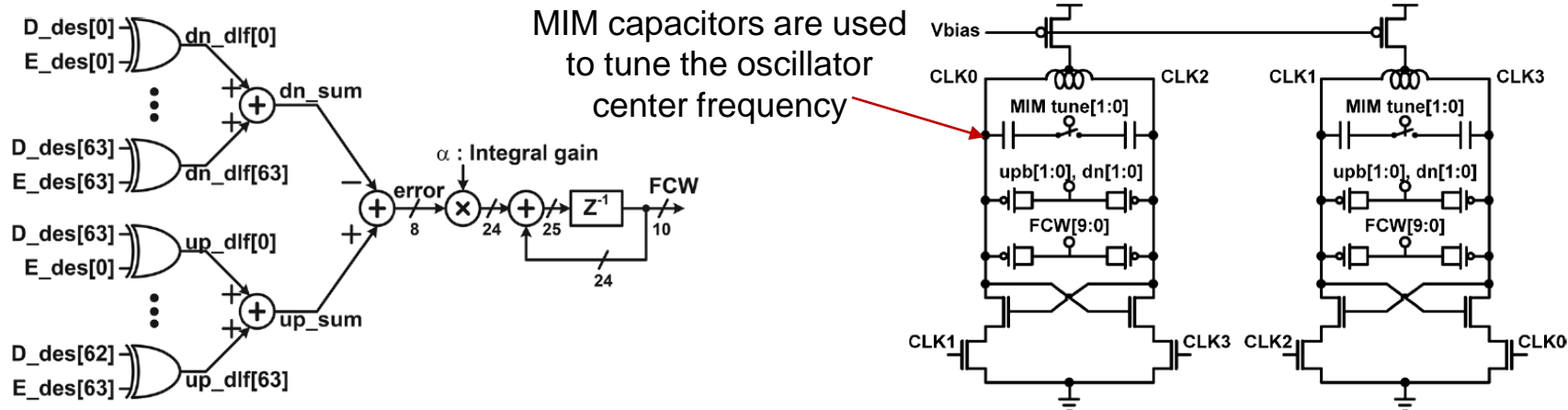
# JSSC 2015: 26.5 Gb/s Optical Receiver With All-Digital Clock and Data Recovery



- The DLF XOR incoming demultiplexed data and edge samples to generate the up/down signals
- The integral path control is generated by a 24 bit integrator (which replaces the large analog loop filter) → Integral path gain is determined digitally by the integral gain  $\alpha$
- Upper 10 bit of the 24 bit integrated error are used for the frequency control word  $FCW[9:0]$
- 2 coupled symmetrical LC oscillators are used to generate the quadrature half-rate clocks with proportional/integral varactor banks to tune the DCO frequency
- To eliminate glitches 8 MSBs of the 10 bit  $FCW$  as 4 bit row and 4 bit column codes and these are converted to two 15 bit thermometer codes, which represent a 30 bit coarse-tuning code
- The two LSBs of the  $FCW$  are for fine-tuning the LC-QDCO code
- The proportional varactor bank consists of binary weighted PMOS capacitors (selectively activated for the proportional gain control)
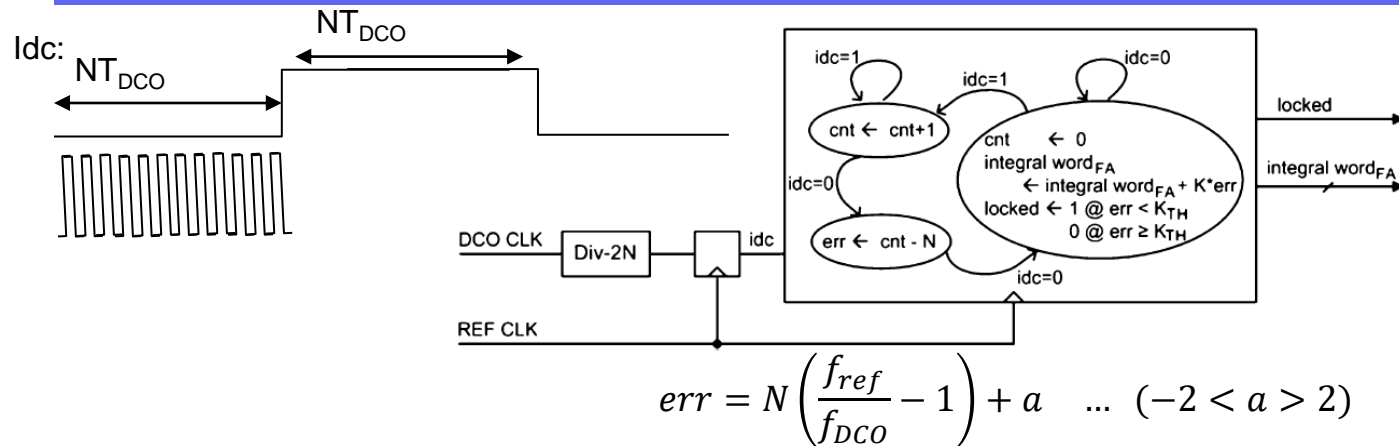
# JSSC 2011: All-Digital CDR With 1.0-ps Period Resolution DCO and Adaptive Proportional Gain



- Frequency acquisition can be performed using a FSM with a digital frequency comparator
- The number of rising reference clock edges are counted during “N” DCO output clocks and subtracting this value from N
- The FSM runs using  $f_{ref}$ , and the enable/disable signal is generated via  $f_{DCO}$
- The result is equal to the product of the frequency error and N
- The integral word is changed by an amount proportional to the measured frequency error
- Once the measured frequency error has declined below a predetermined value, the integral word is then controlled by the DLF
- of the main phase-locking loop

H. Song, D. -S. Kim, D. -H. Oh, S. Kim and D. -K. Jeong, "A 1.0–4.0-Gb/s All-Digital CDR With 1.0-ps Period Resolution DCO and Adaptive Proportional Gain Control," in *IEEE Journal of Solid-State Circuits*, vol. 46, no. 2, pp. 424-434, Feb. 2011.




---

# **CDR SIMULINK DESIGN**


## **EXAMPLE:**

**FULL RATE ALEXANDER PD BASED CDR  
WITH ANALOG CP/LOOP FILTER**
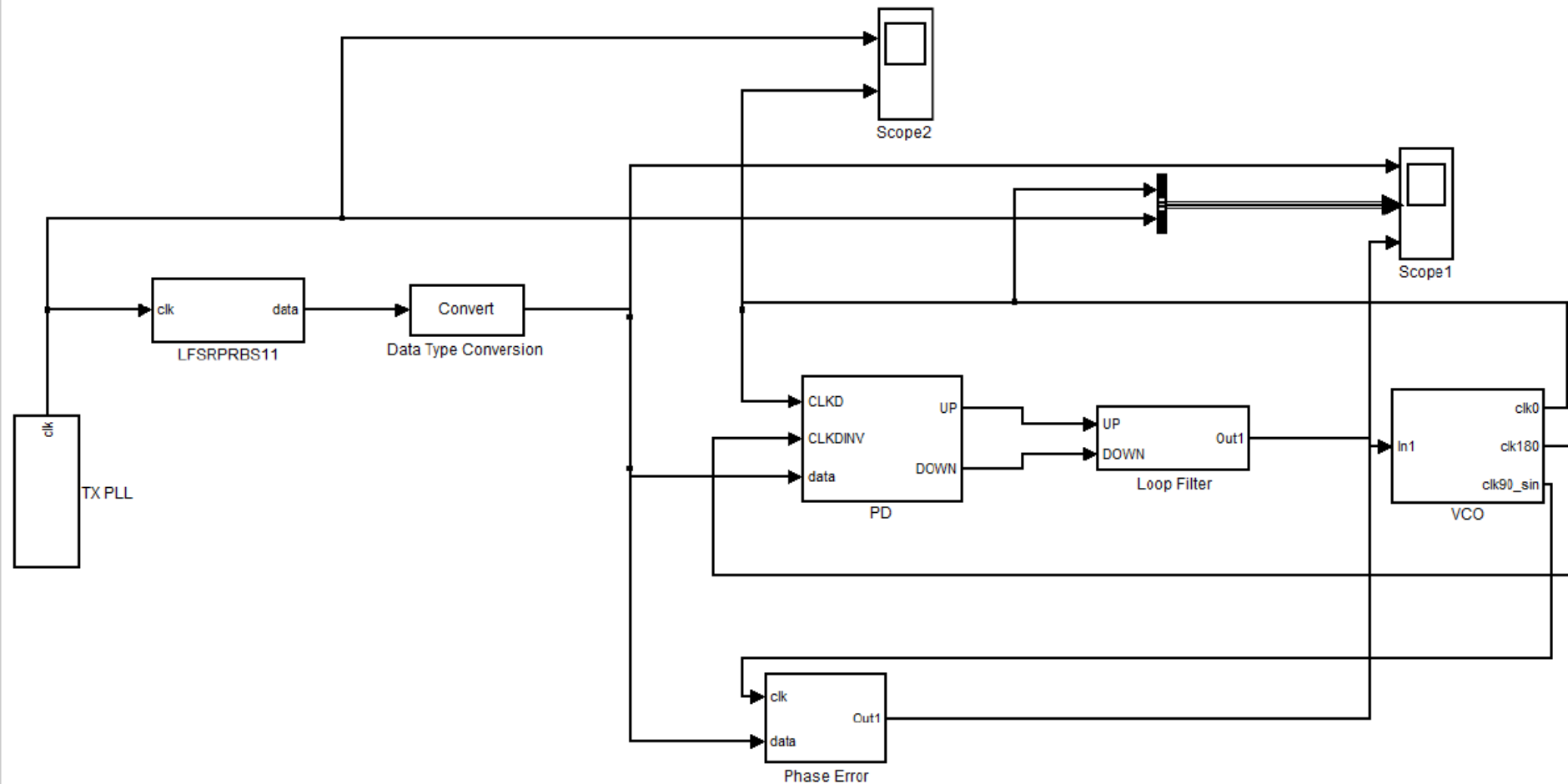
# Block Diagram of CDR with PRBS Generator




# Tx CLK Model with Sinusoidal Jitter

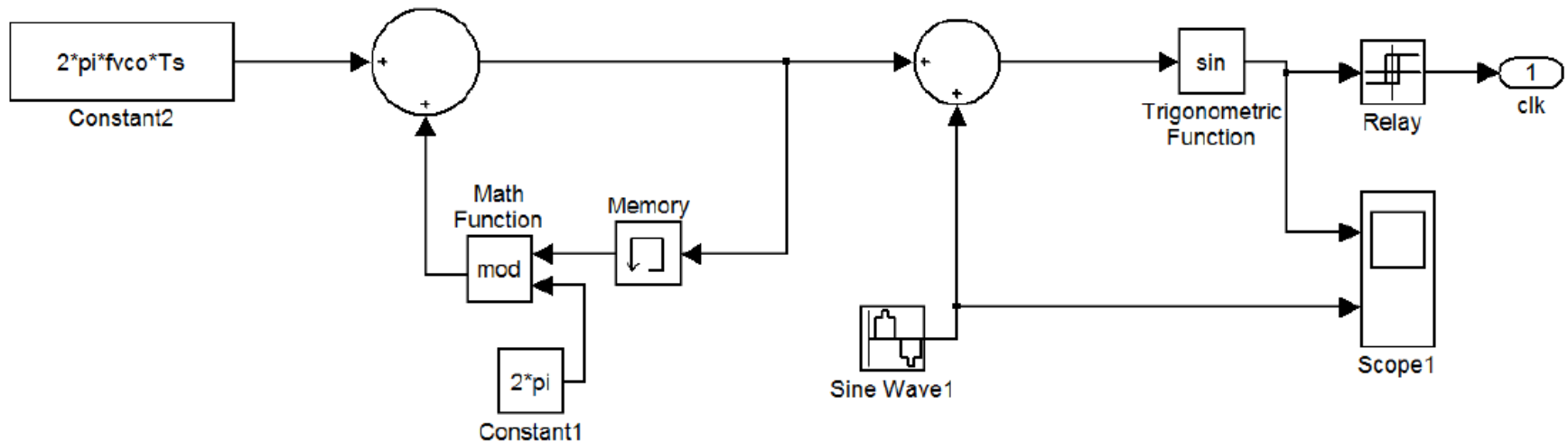





# Phase Detector

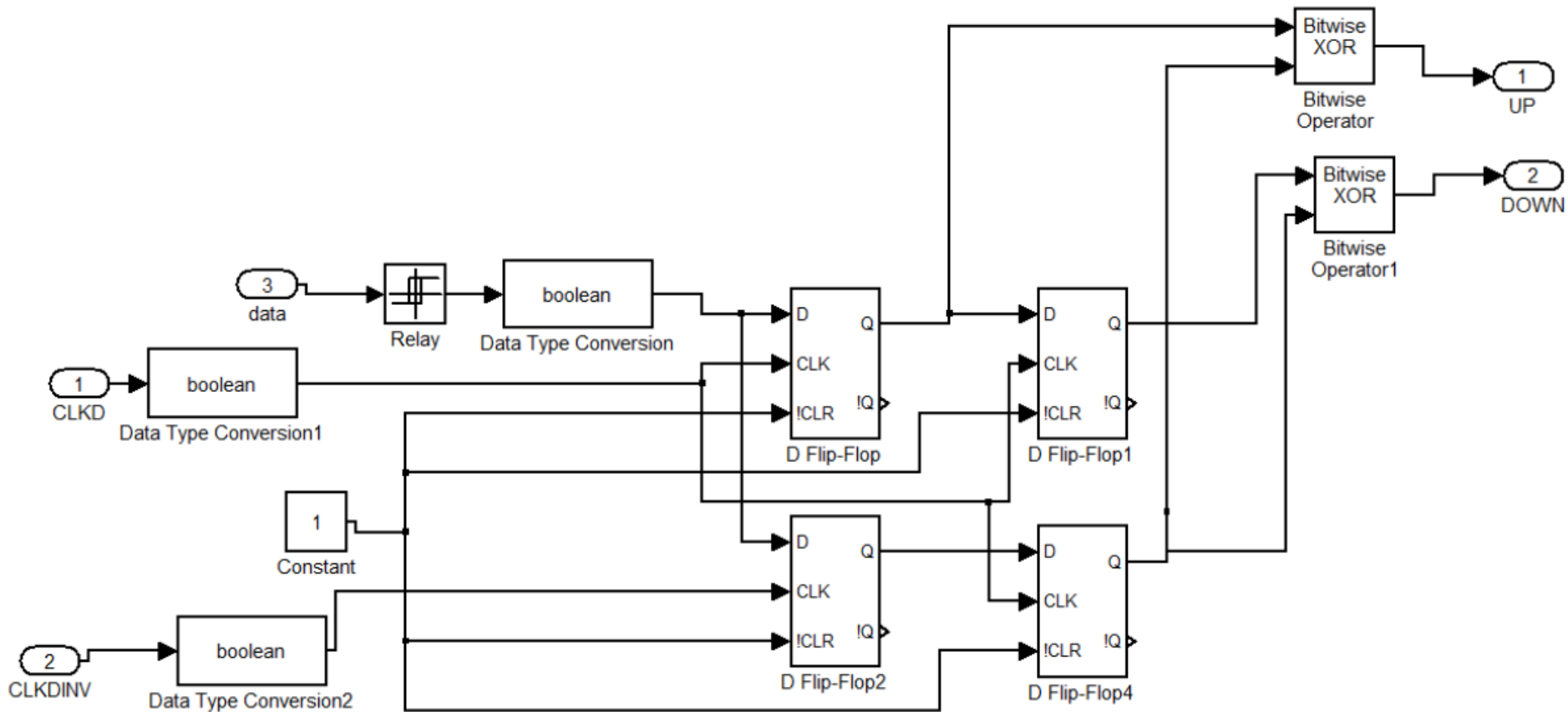


# Loop Filter Model

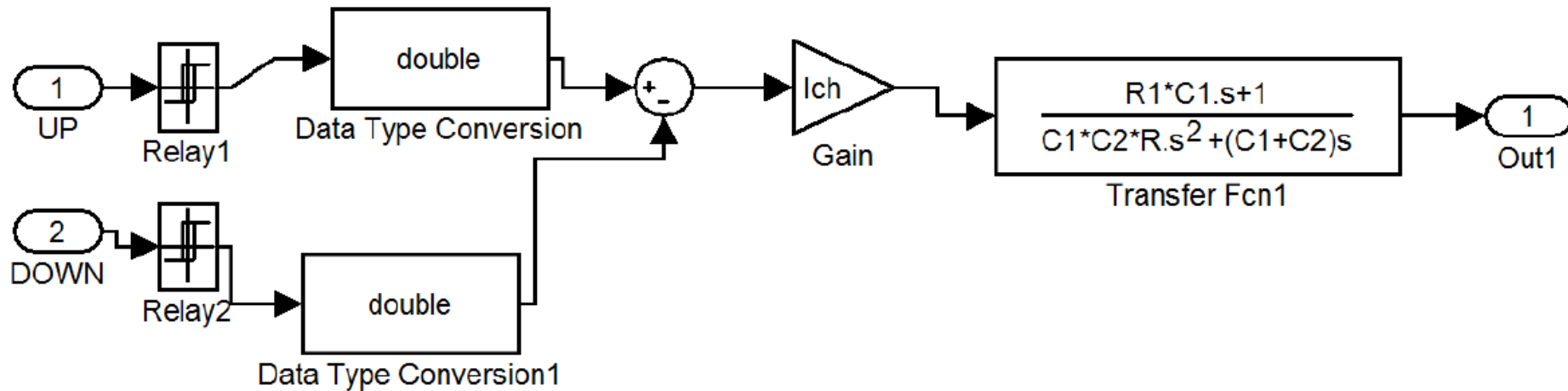

# CDR VCO Model

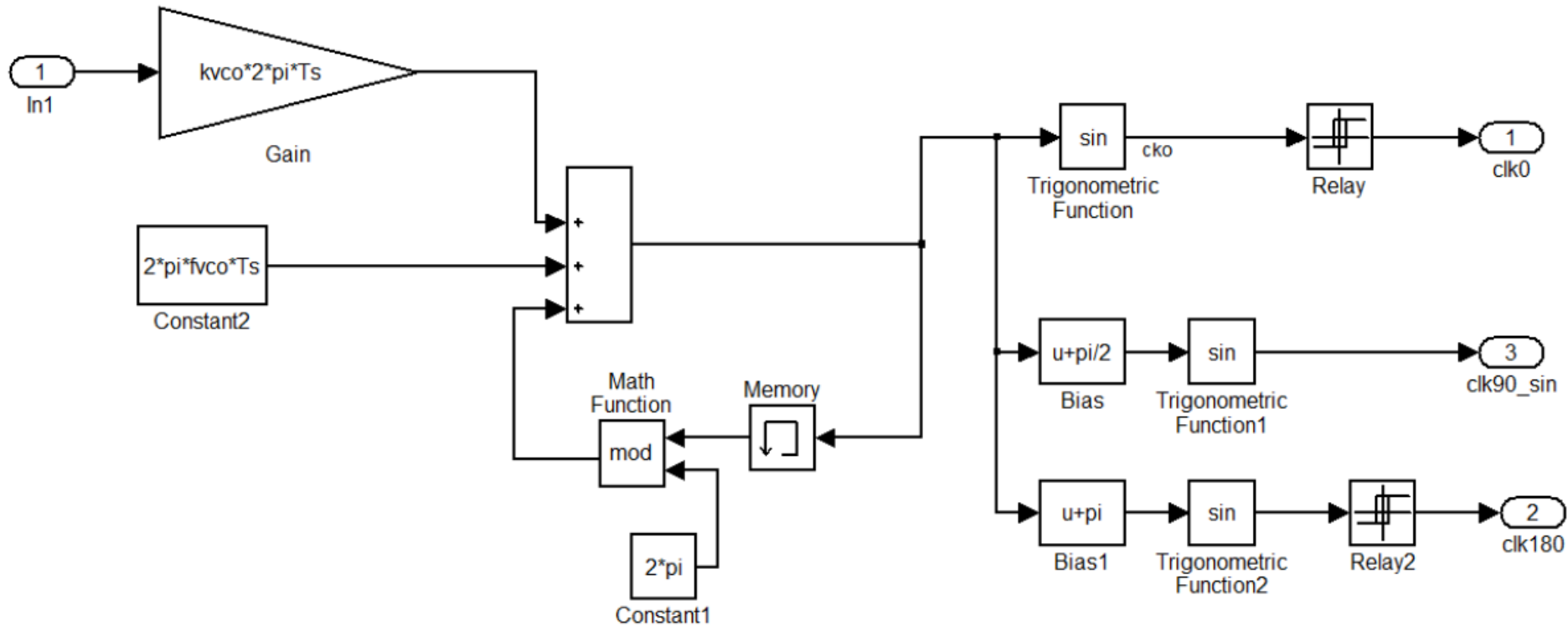

# Phase Error Calculation Block

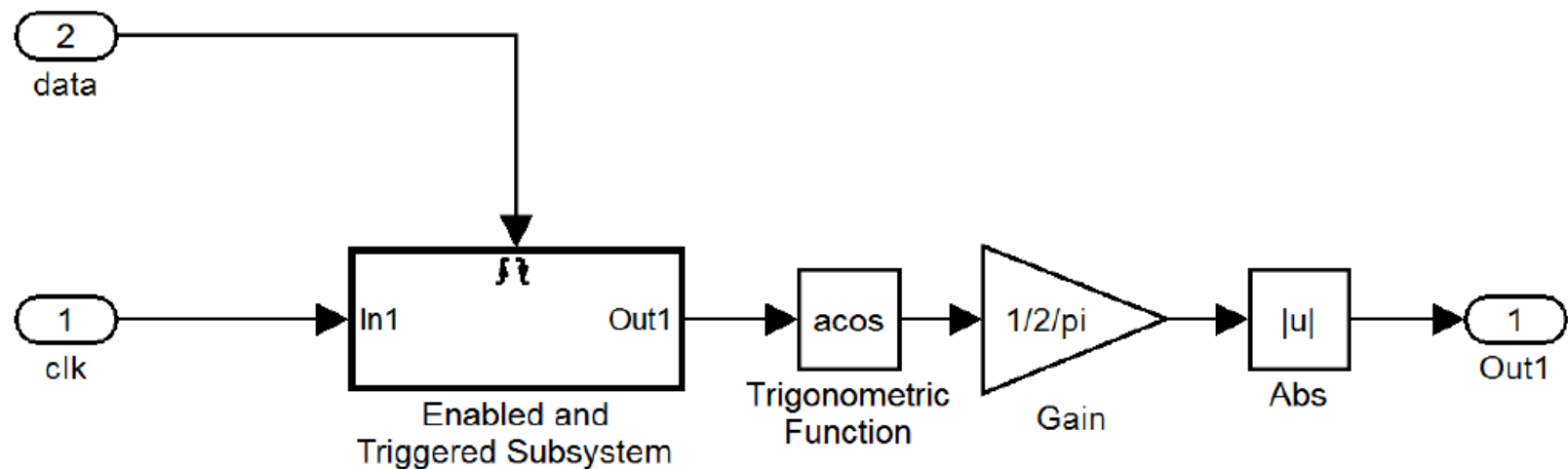



# Simulation Results

