

Wireline Transceiver Circuits

Dr. Mohamed Salah Mobarak


Email: mohamedmobarak@eng.cu.edu.eg

Department of Electronics and Electrical
Communications Engineering
Cairo University

VCO Phase Noise Summary


- To reduce VCO phase noise
 - Improve quality factor and reduce loss
 - Improve symmetry
 - Select topology that has current injected at voltage peaks
 - Increase power consumption
- Ring oscillator is used in application where area is most critical and phase noise is not very stringent

PLL Phase Noise Contributions

 


- Reference oscillator noise, and PFD/dividers has low pass response, while VCO has high pass response
- Large division ratio causes high noise
 - Use fractional dividers to avoid large N

Frequency Dividers

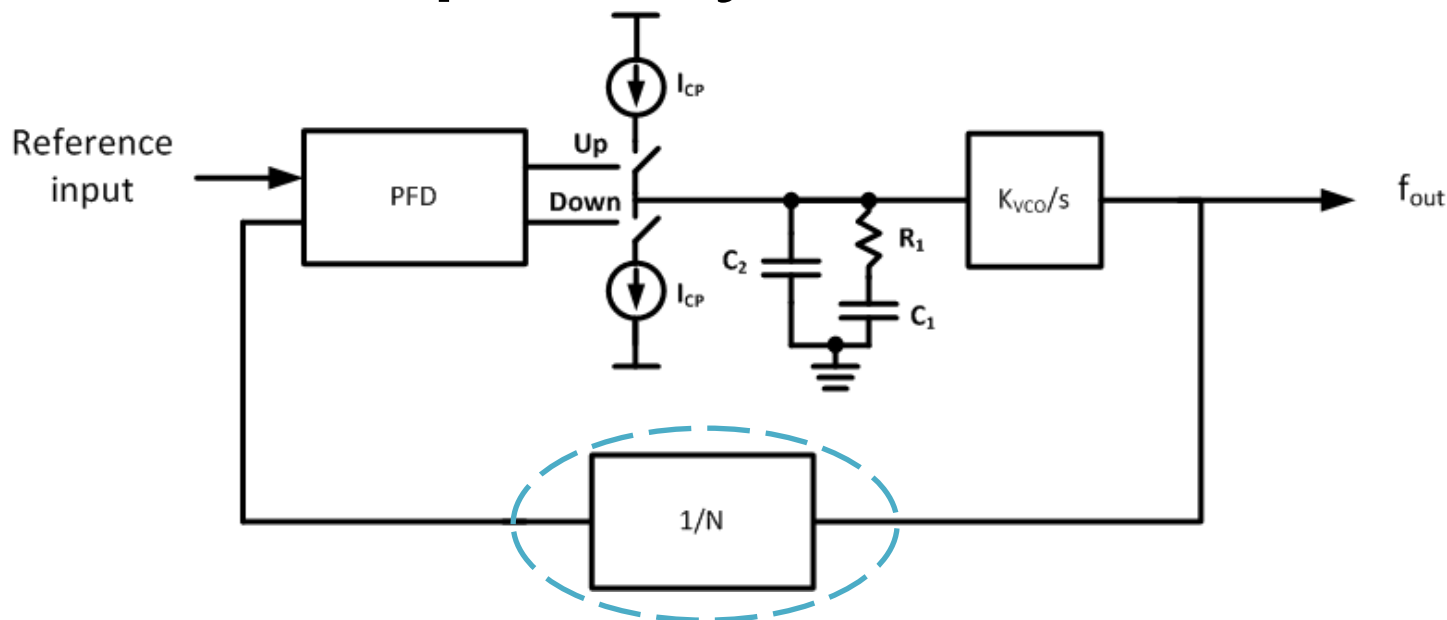

- Frequency divider takes the form of a counter
- VCO frequency is usually very high
- Divider power consumption is proportional to its frequency
 - Power consumption of single CMOS inverter $P = fCV_{DD}^2$


Frequency Dividers

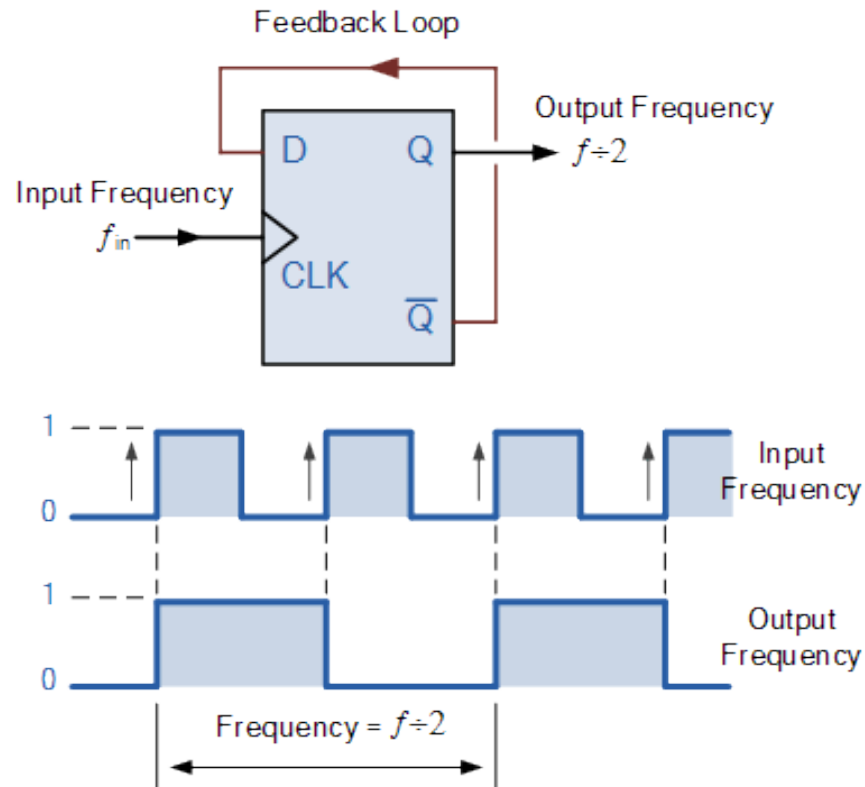

- Divide by 2 circuit


Counter Types

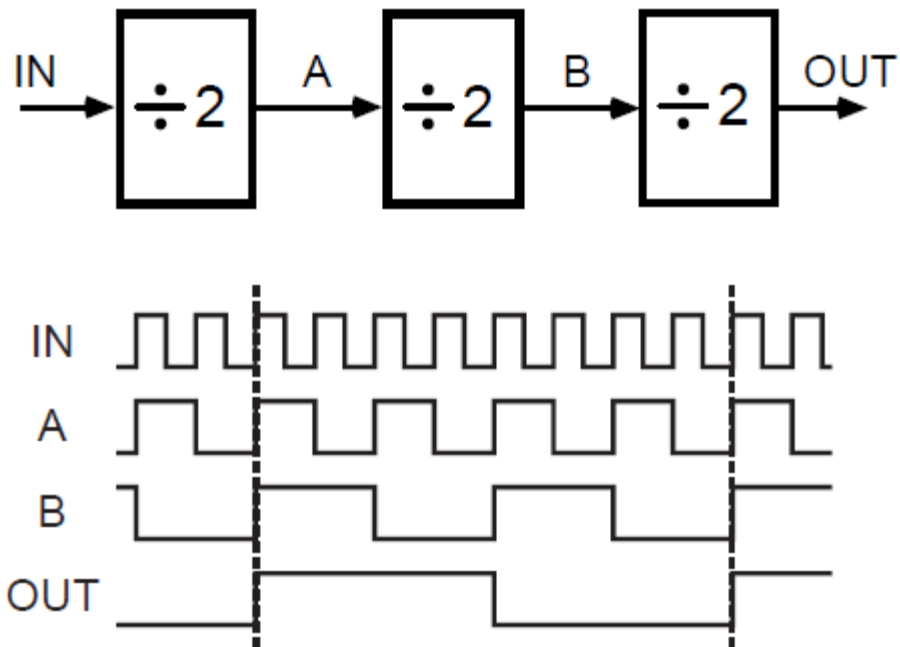- Counters can be asynchronous or synchronous
- Asynchronous counters have
 - Less loading on the clock
 - Lower power consumption
- Asynchronous counters suffer from higher noise




Counter Types

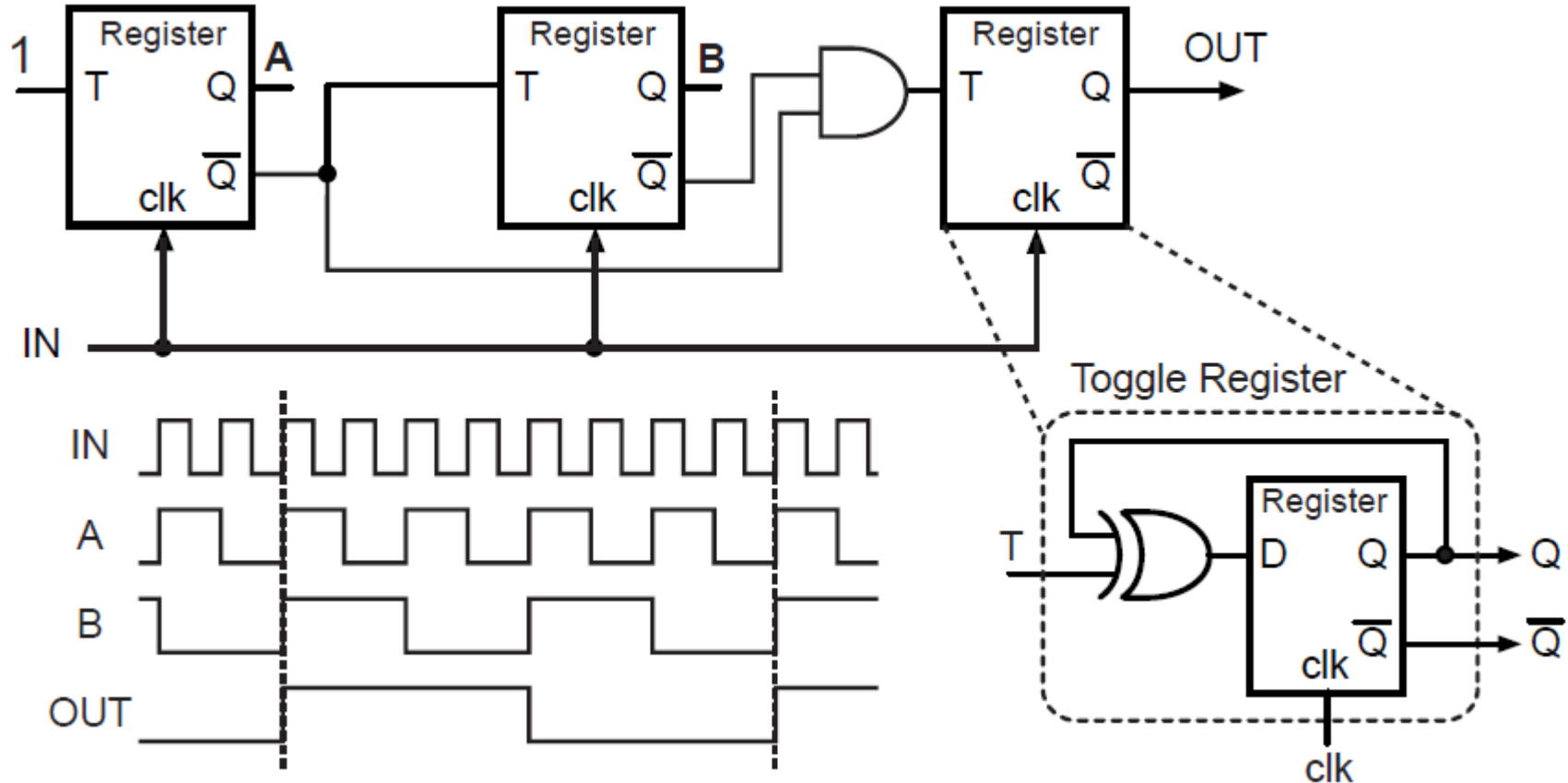- Synchronous counters have less noise but more power consumption




Program Counter

- Divide by 7 counter

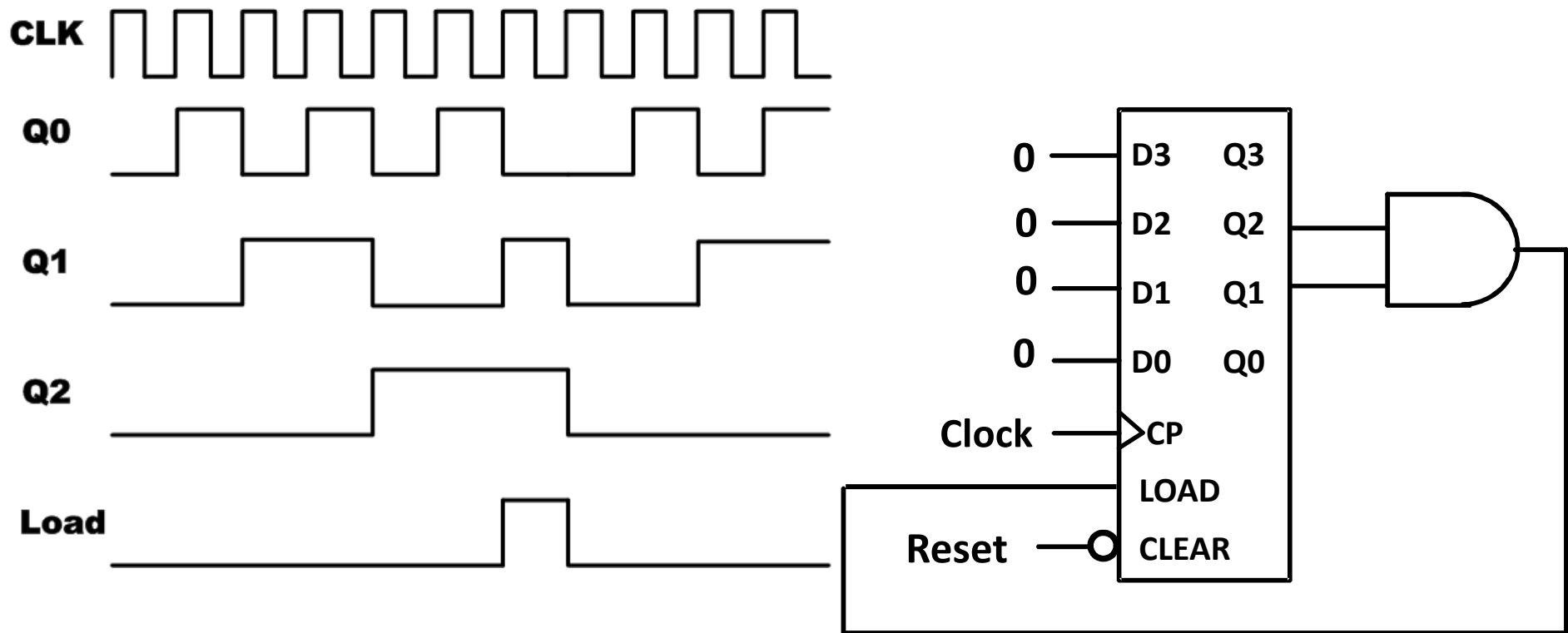


Program Counter

 - Programmable counter can be done using count up or count down counters




Program Counter

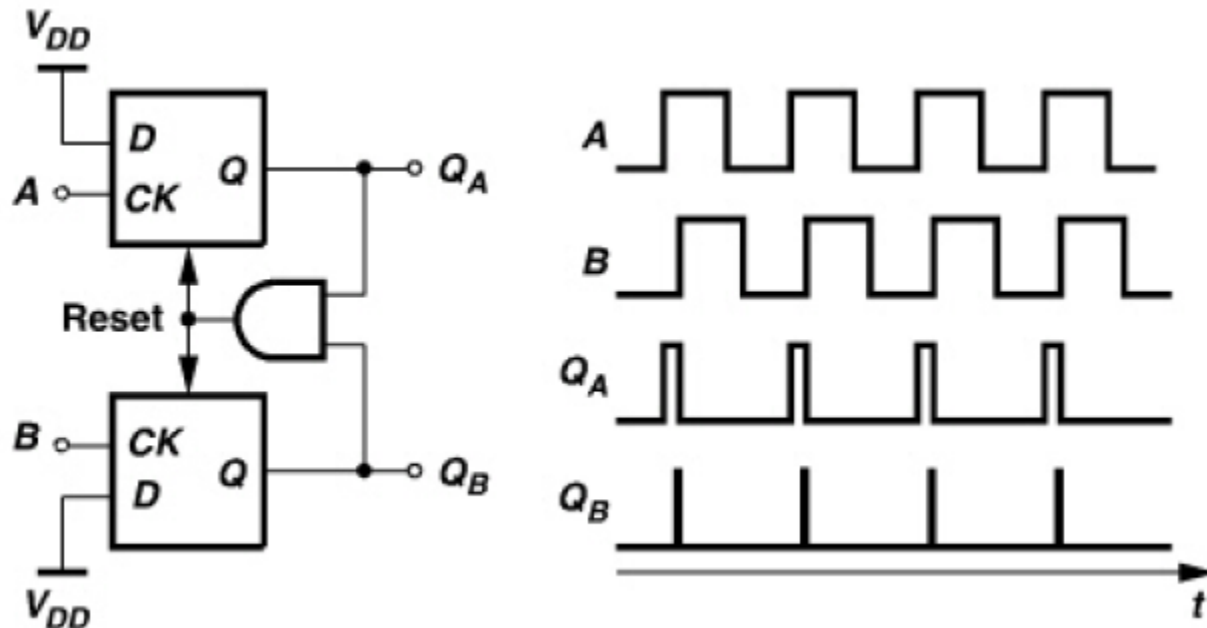- Note that output pulse of divider does not have 50% duty cycle
 - Works fine with PFD




Pulse Swallow Counter

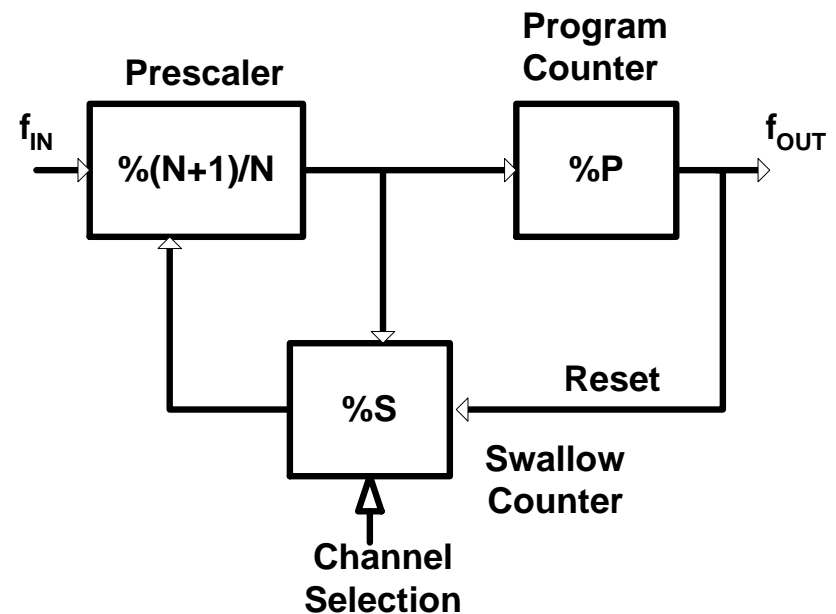- Pulse swallow counter is used to lower power consumption of synchronous divider
- Counter consists of
 - Dual modulus prescaler which divides by $N+1$ or N according to its logic input
 - Pulse swallow counter which divides the input frequency by S
 - Program counter which divide the input by P




Pulse Swallow Counter

- Prescaler divides the input by $N+1$ then gives S counter one pulse
- After the S counter receives S pulses it changes the modulus of prescaler to divide by N and holds its state
 - The main input require to receive $(N+1) \times S$ pulses
- The P counter so far received S pulses and requires $(P-S)$ pulses to return to its starting state
 - The main input require to receive $N \times (P-S)$ pulses
- The total number of pulses needed is $(N+1)S + N(P-S) = PN + S$
- Note that P must be greater than S ($P > S$)

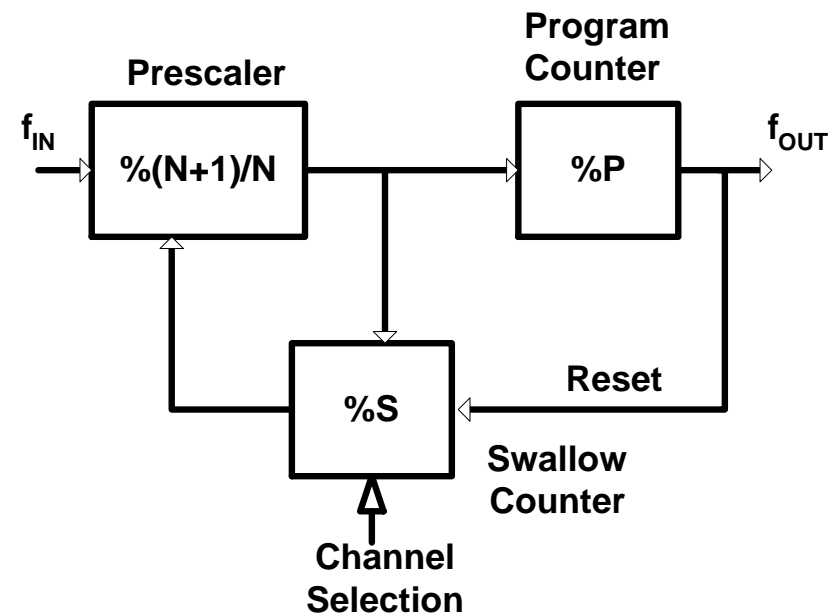


Swallow Counter

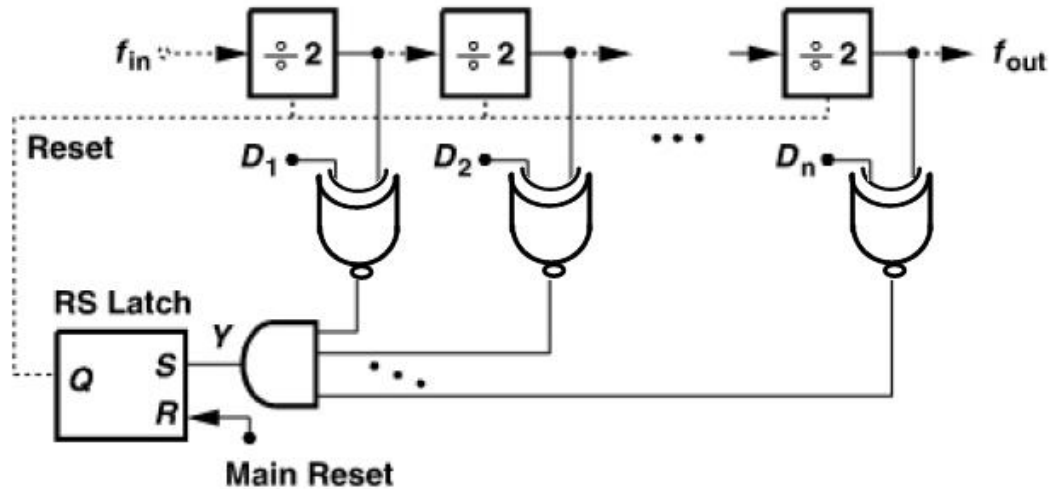

- Asynchronous logic
- After reaching the desired division ratio the counter holds its state
- After receiving reset pulse counter goes back to active mode


Dual Modulus Prescaler

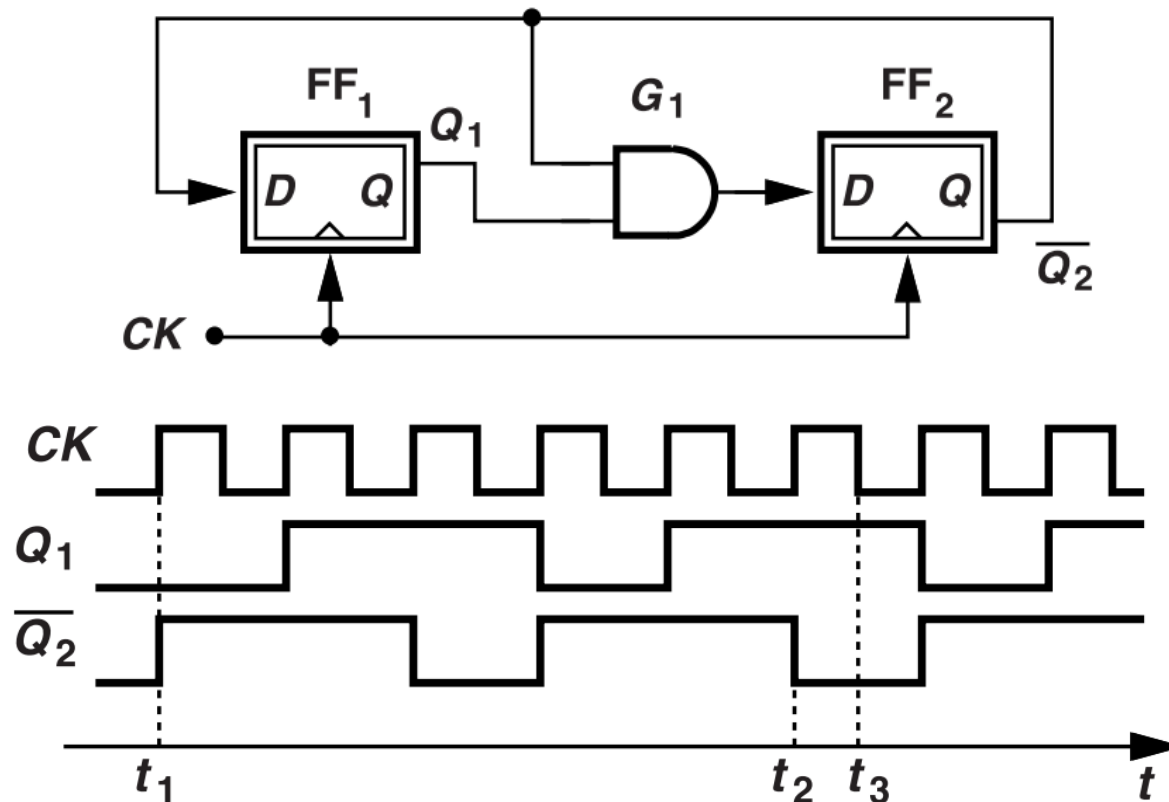- Divide by 3
- Suppose that \overline{Q}_2Q_1 initially is 10
- $\overline{Q}_2Q_1 = 11, 01, 10$ and then repeats




Dual Modulus Prescaler

 
- If $MC=0$ circuit is a divide by 3
- If $MC=1$ circuit is a divide by 2 (feedback from Q_2 to D_2).




Modular Divider

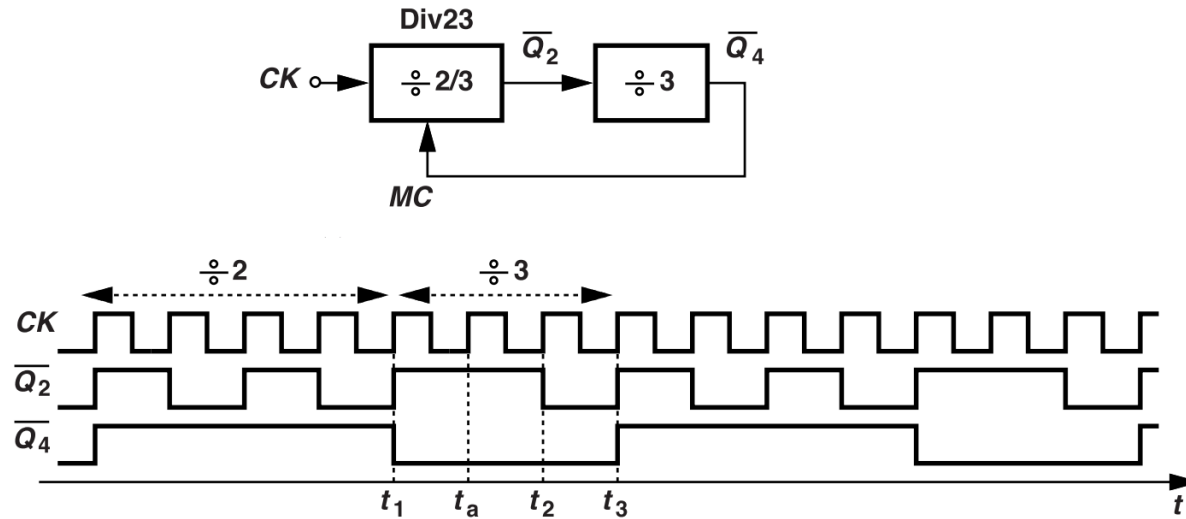

 - Divide by 7 can be obtained by cascading divide by 2/3 and divide by 3
- If divide by 3 is replaced by divide by 2 then we obtain divide by 5




Modular Divider

 


- If $MC_2=0$, then total division by 7. If $MC_2=1$, so division by 5
- If both $MC_1, MC_2=1$ then divide by 4
 - Need to force $MC_1=1$
- If $MC_1=1, MC_2=0$ then divide by 6

Modular Divider

 


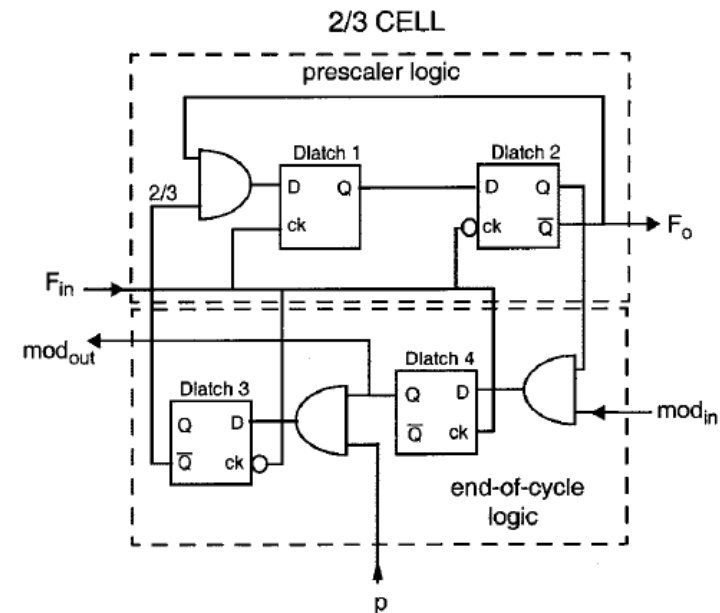- Saves layout time
- Output is sampled at input clock speed
 - Low jitter on output
- $T_{out} = 2^n T_{in} + 2^{n-1} p_{n-1} T_{in} + \dots + 2 T_{in} p_1 + T_{in} p_0$
- Slow response if division ratio change, might be challenge for fractional PLL




Modular Divider

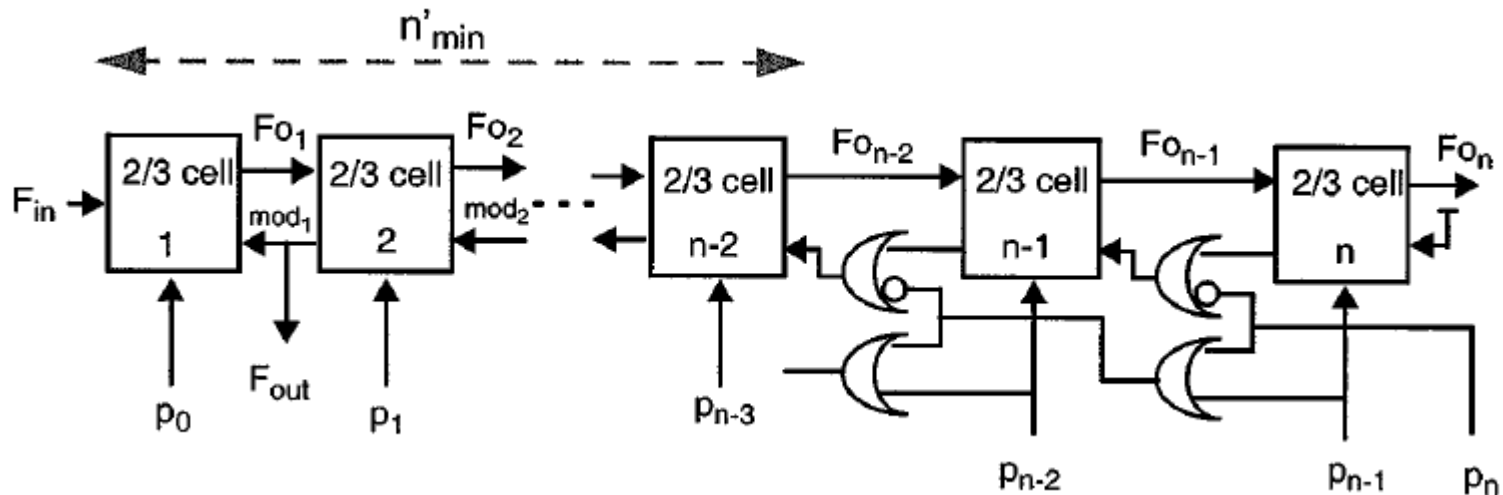- Modified architecture to extend division ratio



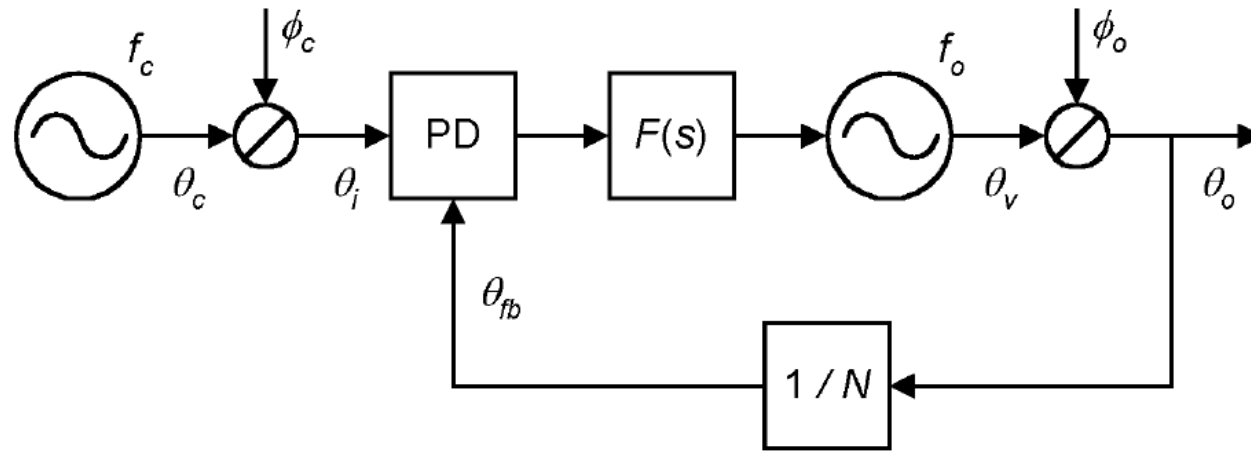
- C. S. Vaucher, I. Ferencic, M. Locher, S. Sedvallson, U. Voegeli and Z. Wang, "A family of low-power truly modular programmable dividers in standard 0.35- μ m CMOS technology," in IEEE Journal of Solid-State Circuits, vol. 35, no. 7, pp. 1039-1045, July 2000

Effect of Frequency Division on Phase Noise



- Phase noise also gets divided by division ratio
- Assume timing jitter is the same, if frequency is lower the relative error is less
 - $\phi_n = 2\pi f_0 t_n$

Crystal Oscillator

 

- PLL reference signal should be
 - Very accurate (0.01%-0.001%)
 - Has very low noise
- Crystals are used to achieve both requirement

E. A. Vittoz, M. G. R. Degrauwe and S. Bitz, "High-performance crystal oscillator circuits: theory and application," in IEEE Journal of Solid-State Circuits, vol. 23, no. 3, pp. 774-783, June 1988


Crystal Oscillator

- Crystal are made of piezoelectric material
 - Piezoelectric Material converts electric signals to mechanical vibrations
 - Mechanical resonance frequency is set by physical dimensions
 - Quartz is the most commonly used material
 - There are many different ways to cut crystal, most common is AT cut




Crystal Model

 - Crystals can be modeled as RLC circuit
- Has very high quality (10^4 to 10^6)
- For example a 10MHz crystal
 - $R=100\Omega$, $L=159\text{mH}$, $C=1.59\text{fF}$, $Q=10^5$



Basic Three Point Oscillator

 
- Ground can be at source or drain of gate
- If ground is chosen to be at source node, topology is called Pierce oscillator
- Pierce oscillator requires two external pins on chip while Colpitts/Clapp oscillator require only one external pin




Small Signal Model of Crystal Oscillator

Ignoring the affect of Z_3

 - $V_t = I_t(Z_1 + Z_2 + g_m Z_1 Z_2)$
- $Z_{in} = \frac{V_t}{I_t} = Z_1 + Z_2 + g_m Z_1 Z_2$
- If Z_1 and Z_2 are capacitors then
- $Z_{in} = \frac{V_t}{I_t} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} - \frac{g_m}{\omega^2 C_1 C_2}$
- To form oscillator inductance is needed between drain and gate




Crystal Impedance

 


- $Z_m = R + j\omega L_m - \frac{j}{\omega C_m} = R + \frac{j}{\omega_m C_m} \left(\frac{\omega}{\omega_m} - \frac{\omega_m}{\omega} \right)$
- Define pulling factor $p = \frac{\omega - \omega_m}{\omega_m}$, usually $p \ll 1$
- $Z_m \approx R + \frac{j2p}{\omega C_m}$
- Oscillation condition $Z_{\text{total}} = 0$
- $R + \frac{j2p}{\omega C_m} + \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} - \frac{g_m}{\omega^2 C_1 C_2} = 0$
- If $C_1 = C_2 = 1 \text{ PF}$, $C_m = 1 \text{ fF}$, then $p = 0.001$

Crystal Oscillator Circuit

 - Start up R_m is higher than steady state R_m
- Current at startup need to be higher than current at steady state
- Automatic gain control can be also used
- What the relationship between V_G and V_D ?
- Where is the output?




Effect of Z_3

 


- $$Z_{in} = \frac{Z_1 Z_3 + Z_2 Z_3 + g_m Z_1 Z_2 Z_3}{Z_1 + Z_2 + Z_3 + g_m Z_1 Z_2}$$
- If Z_1 , Z_2 and Z_3 are capacitors then
- $$\text{Re}(Z_{in}) = \frac{-g_m C_1 C_2}{(g_m C_3)^2 + \omega^2 (C_1 C_2 + C_2 C_3 + C_1 C_3)^2}$$
- $$\text{Im}(Z_{in}) = \frac{g_m^2 C_3 + \omega^2 (C_1 + C_2)(C_1 C_2 + C_2 C_3 + C_1 C_3)}{\omega [(g_m C_3)^2 + \omega^2 (C_1 C_2 + C_2 C_3 + C_1 C_3)^2]}$$

Effect of Z3

 

- $\text{Re}(Z_{in}) = \frac{-g_m C_1 C_2}{(g_m C_3)^2 + \omega^2 (C_1 C_2 + C_2 C_3 + C_1 C_3)^2}$
- Max -ve impedance is obtained when
- $g_m = g_{mopt} = \omega \left(C_1 + C_2 + \frac{C_1 C_2}{C_3} \right)$
 - Max -ve impedance $\text{Re}(Z_{in}) = \frac{-1}{2\omega C_3 \left(1 + \frac{C_1 + C_2}{C_1 C_2} C_3 \right)}$

Which Topology is Better?

 

- Where should we put ground?