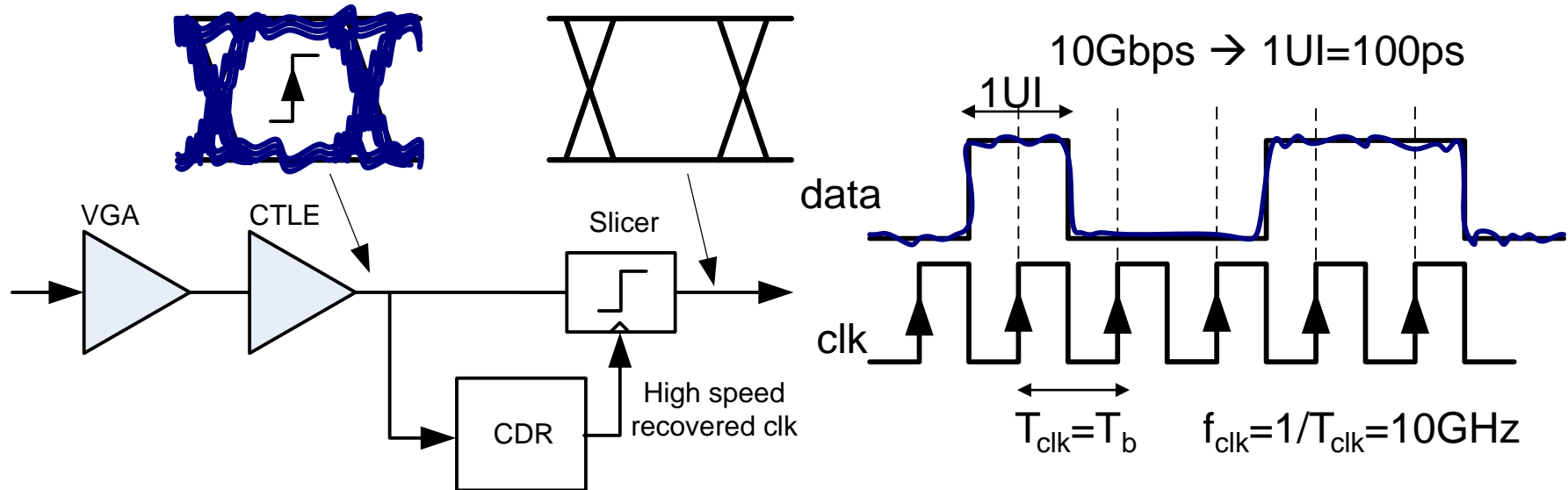


Clock and Data Recovery

Lecture 8

Clock & Data Recovery




- The CDR senses the equalizer output and produces a clock typically with the same frequency centered at the eye opening to minimize the BER
- The slicer (decision circuit) is a flip-flop driven by the recovered clock
- Re-timing the data with the recovered clock reduces the jitter accumulated on the received data
- To produce a clock centered at the eye opening the CDR can employ a PD that compares the recovered clock with the input **random data**

Common CDR Architectures

- Feedback-based CDRs can be classified according to their **architecture**:
 - PLL-based CDRs
 - Reference-less CDRs or CDRs with External Reference Clock
 - Delay Lock Loop (DLL) based CDRs
 - Phase Interpolator (PI) based CDRs
 - All Digital CDRs
- Feedback-based CDRs can be classified according to their **nature** into:
 - Linear/non-linear (band-bang) CDRs
- Feed Forward-based:
 - Over-sampling based CDRs


[Ref]: “Architectures for Multi-Gigabit Wire-Linked Clock and Data Recovery,” IEEE Circ. & Sys. Magazine, 2008

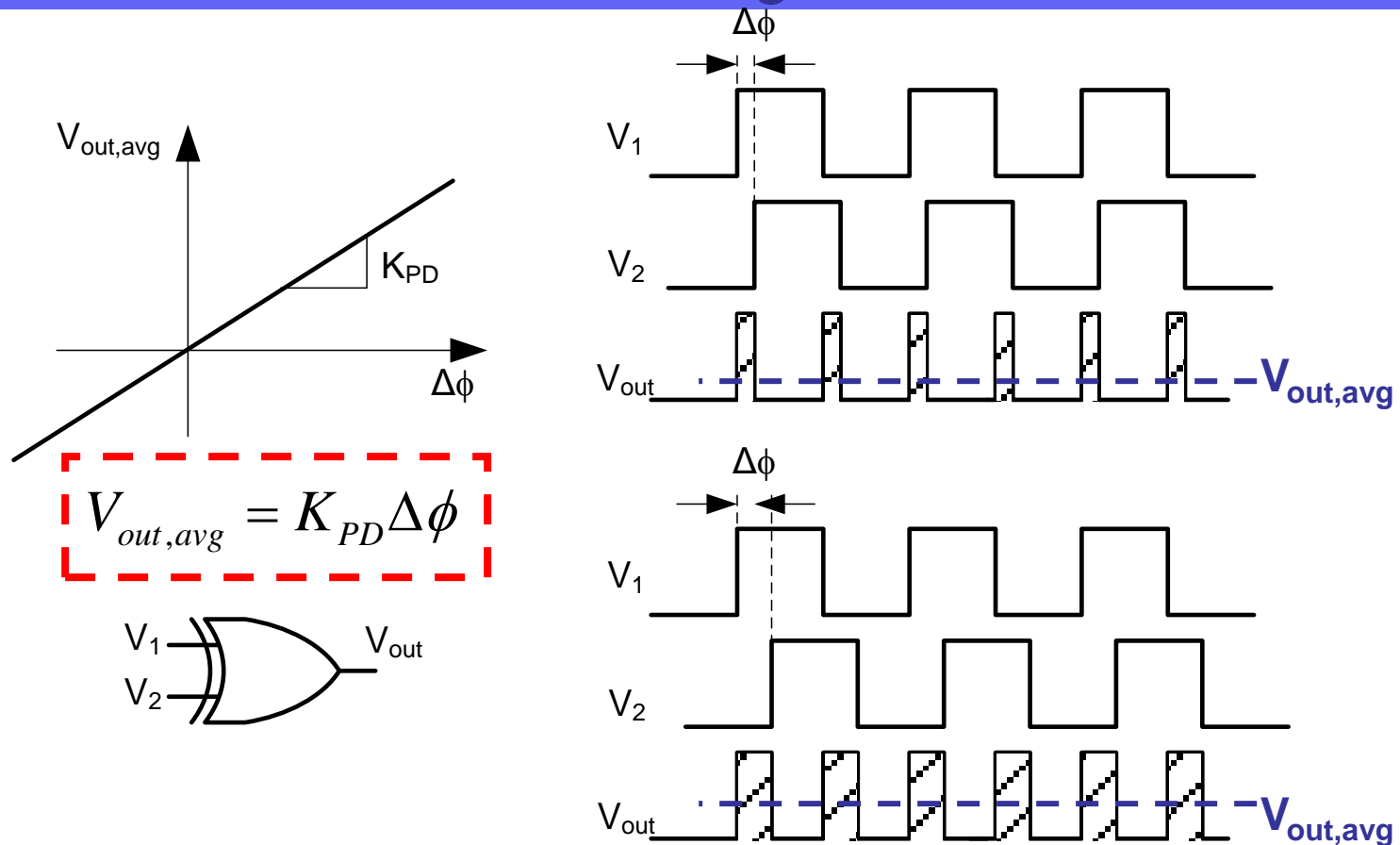PLL-based CDRs: XOR as a Phase Detector for Periodic Signals





- A Phase detector is circuit which produces an output voltage V_{out} with an average value proportional to phase difference $\Delta\phi$ between its inputs
- The gain of the phase detector, K_{PD} , is the slope of the PD characteristics

Random Data PDs: XOR

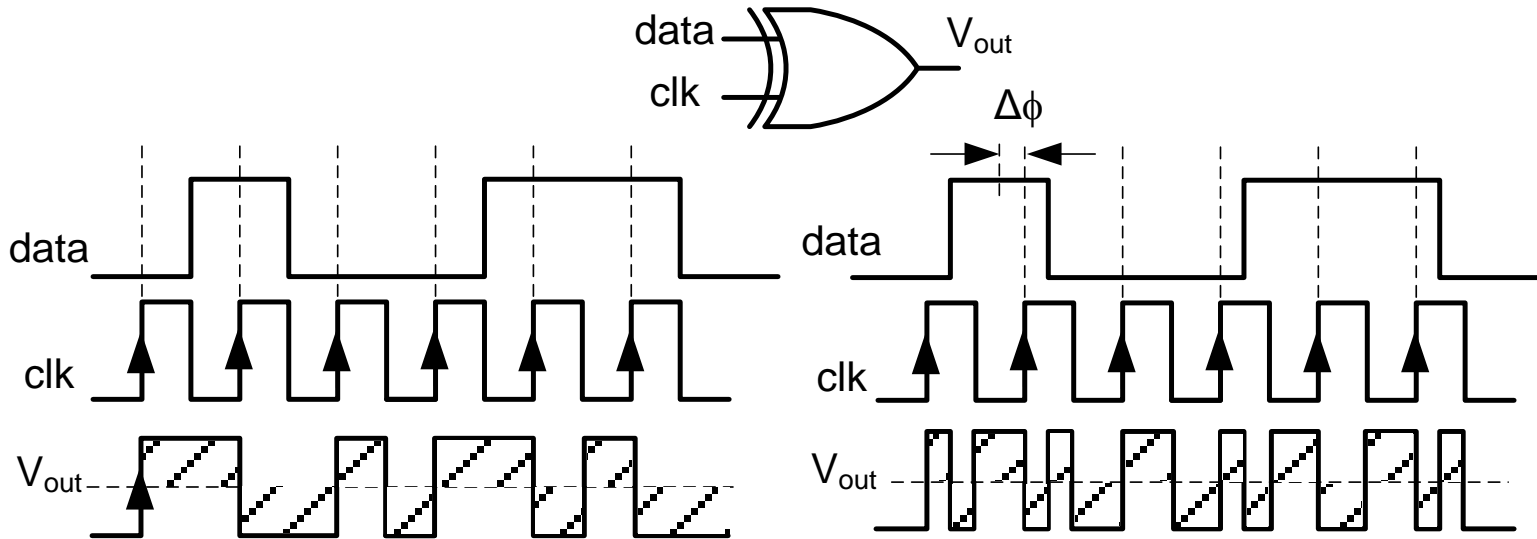



- If clock and data are aligned: the XOR produces a zero average at the output if the 1's and 0's occur with equal probabilities
- If clock is late by $\Delta\phi$: the XOR produces a zero average at the output if the 1's and 0's occur with equal probabilities
- The XOR fails to operate as a PD for random data

Linear Detectors: Hogge Phase Detector

  


- Sampling the data with the clock produces a delayed version of the data (B)
- The output of the XOR is pulses which only occur at the data transitions → “edge detection”
- The width of the output pluses is linearly proportional to the delay between data and clock edges → linear phase detector
- The average value of the output is a function in the phase difference as well as the transition density failing to uniquely represent the phase difference

Linear Detectors: Hogge Phase Detector

  


- The 2 outputs have the same average value although the phase error is doubled in the right graph
- 2 different phase errors having the same average output could result in a false lock



Linear Detectors: Hogge Phase Detector

 

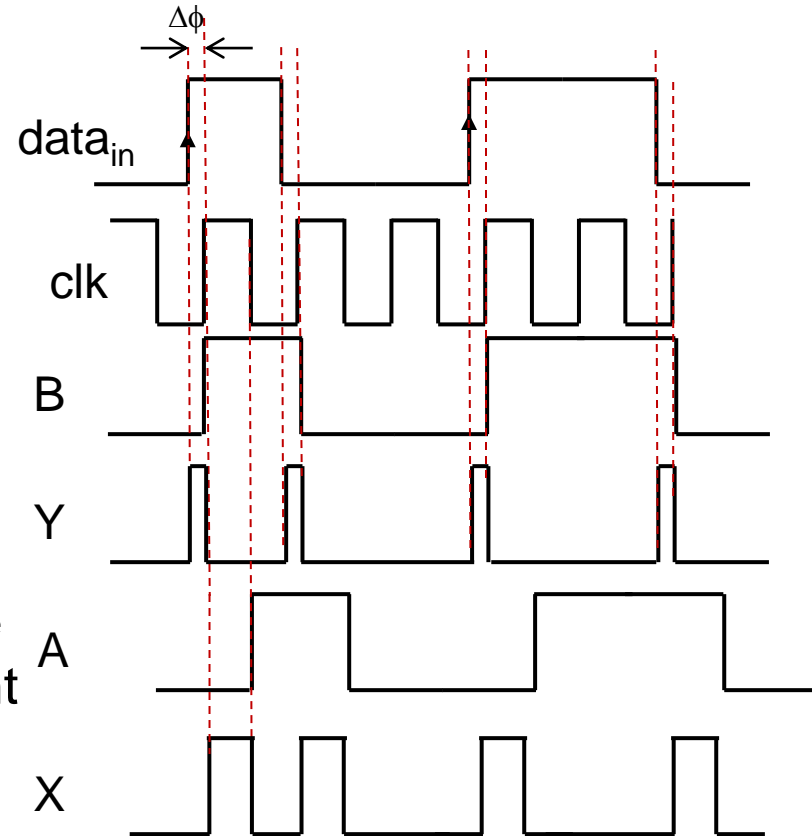- To eliminate the pattern dependency, reference pulses are generated at the data transitions which have a constant width
- If the delayed signal B is re-sampled with the falling clock edge and the result is XOR-ed with B, pulses $T_{clk}/2$ wide are produced at data transitions




Linear Detectors: Hogge Phase Detector

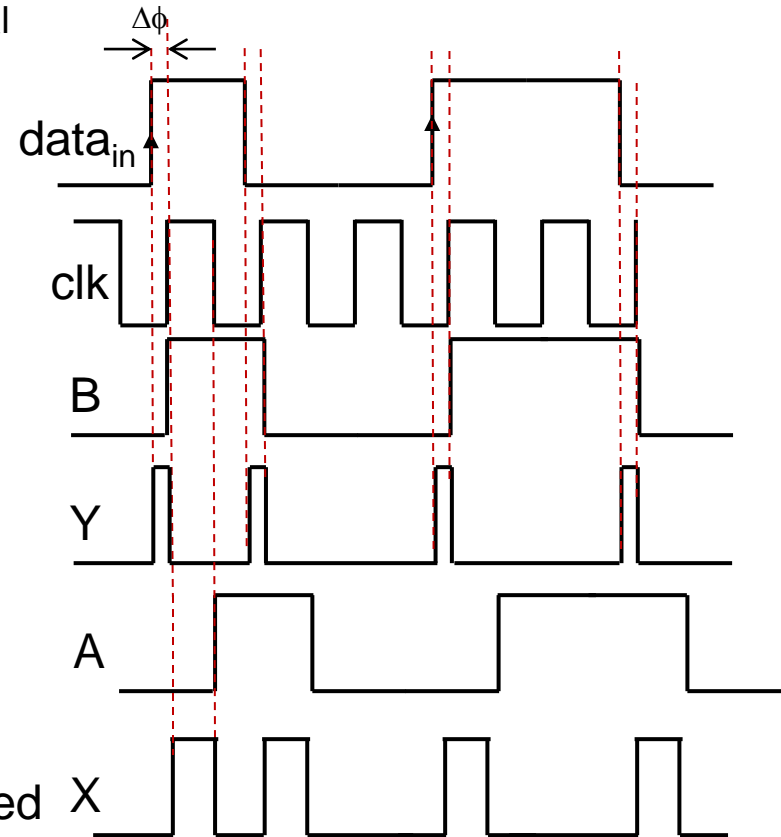 

- The difference between the area under the 2 signals X and Y is considered the PD output
- Under lock condition X and Y have pulses with equal width
- The DFF inside the Hogge phase detector automatically re-times the data with the recovered clock
- Disadvantage: Linear phase detectors need to handle very narrow pulses which requires circuits with very wide bandwidths


CDR Based on Hogge PD

 


- The Y and X pulses can be subtracted and averaged using a charge pump and loop filter as in charge pump PLLs
- If the clock leads the data: the PD output $\text{avg}(Y-X)$ will generate negative current pulse, reducing the VCO control voltage and running the VCO at a slower frequency until the phase of the clock aligns with the data reducing the phase error to zero
- As the Phase difference approaches zero the average of the PD output remains unchanged with little activity

CDR Based on Hogge PD: Under lock Condition


- The drawback of this Hogge PD is the $T_{\text{clk}}/2$ skew between the two XOR outputs
- When the proportional pulses appear the top current source turns on for $T_{\text{clk}}/2$ forcing V_{out} to rise by $I_{\text{CP}}/C_P * T_{\text{clk}}/2$
- Following that the reference pulse turns on the bottom current source bringing down the V_{out} to its original value
- The triangular pulse that is generated has a non-zero net area, which disturbs the VCO phase (proportional to the integral of the control voltage)

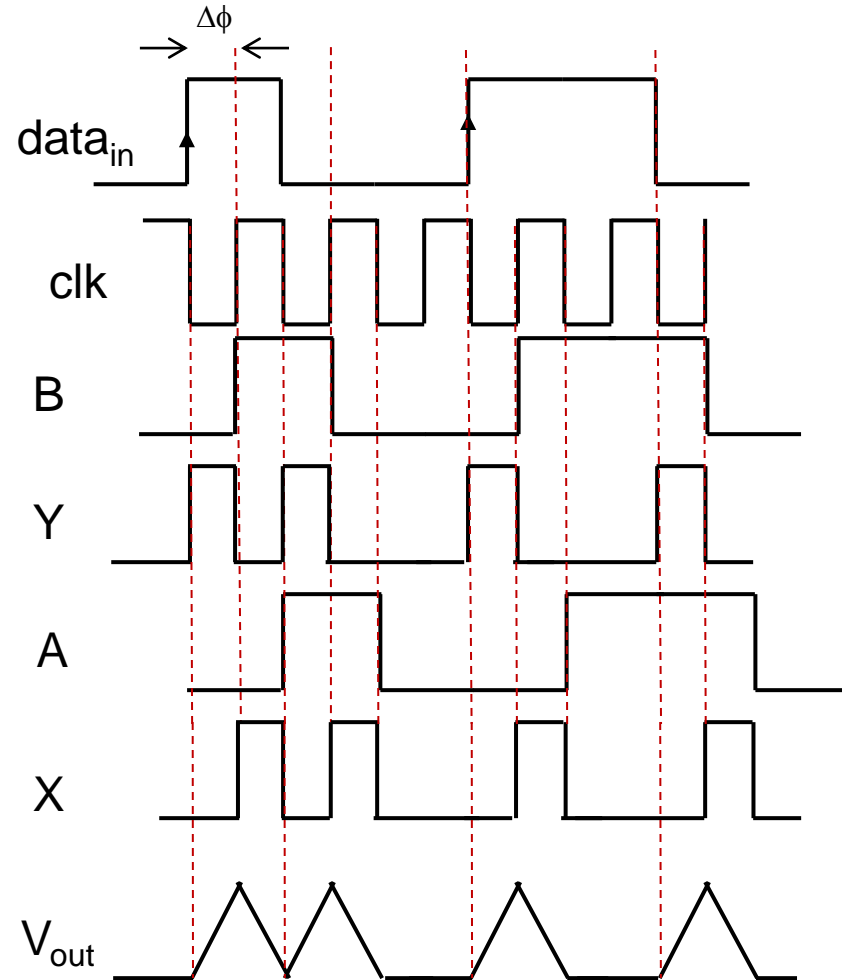

Tri-wave Phase Detector

 

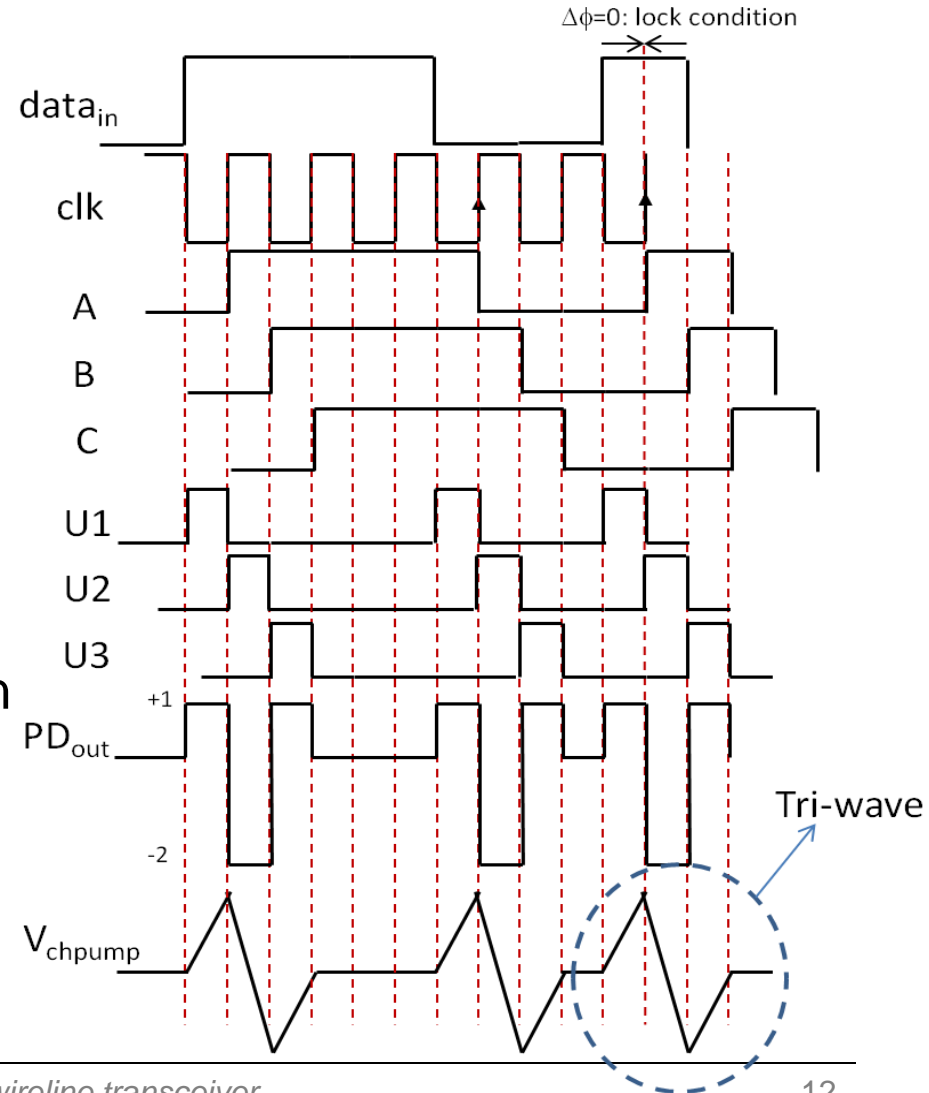
- The tri-wave phase detector reduces this problem; by replacing the triangular correction pulses with tri-waves whose net is 0 during the lock condition
- Pulses out of U1 & U3 are weighted by 1 while pulses out of U2 are weighted by -2



Hogge CDR Loop Dynamics: CP Model

- Step response is obtained by applying a phase step $\Delta\phi u(t)$ to one of the PD inputs
- The width of the proportional pulses is $T_{\text{clk}}/2 + \Delta\phi$, whereas the reference pulses are $T_{\text{clk}}/2$
- Note that the phase detector will have a zero slope in the absence of data transitions, hence its gain is proportional to the data transition density D_T
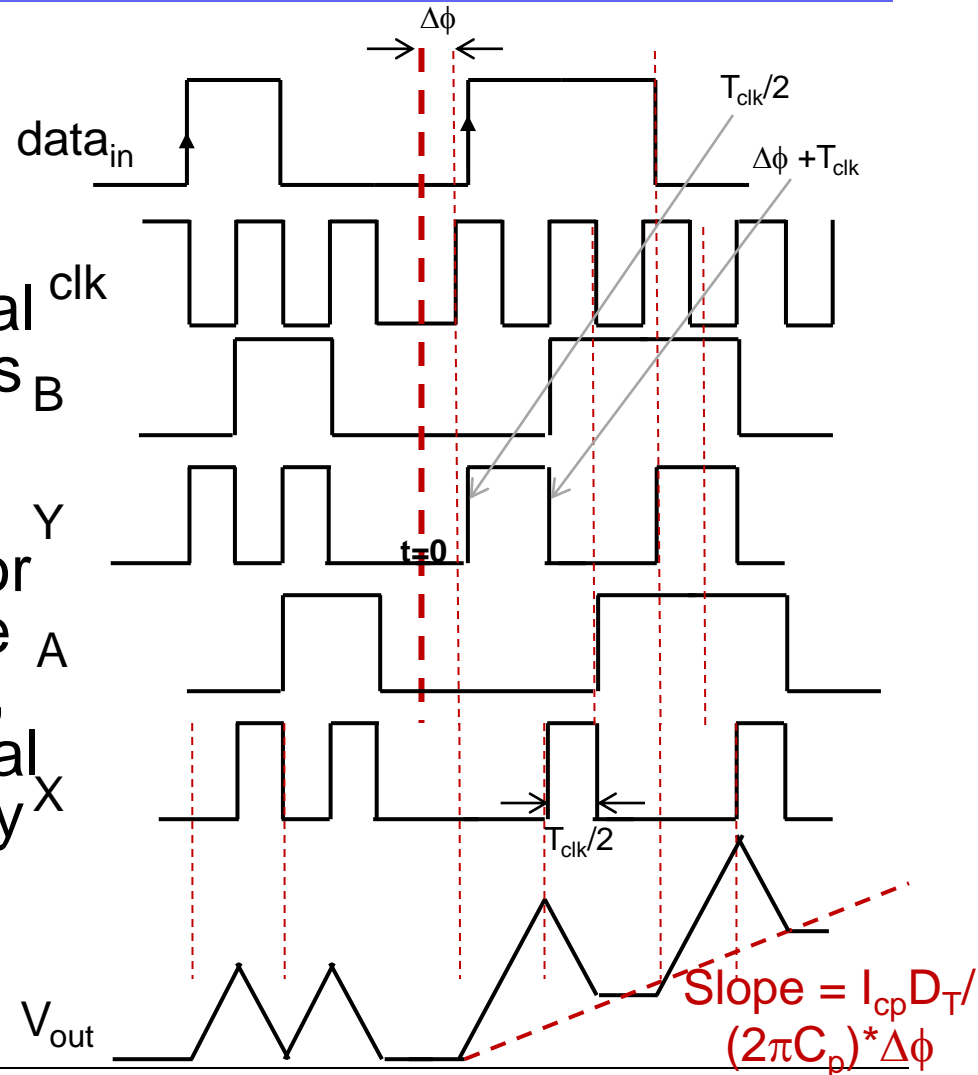
$$V_{\text{step}}(t) = \frac{I_{\text{cp}} D_T}{2\pi C_p} t \times \Delta\phi u(t)$$



Hogge CDR Loop Dynamics: CP Model

- For a random signal with equal probabilities for 1s and 0s $D_T=0.5$
- Impulse response is the derivative of the step response


$$h_{PD_CP}(t) = \frac{I_{cp} D_T}{2\pi C_p} u(t)$$

- Transfer function $H_{PD_CP}(s)$:

$$H_{PD_CP}(s) = \frac{V_{out}}{\Delta\phi}(s) = \frac{I_{cp} D_T}{2\pi} \frac{1}{s C_p}$$

- The equation is very similar to the charge pump PLL except for the effect of the data transition density
- The CP-PLL handles periodic signals and guarantees a transition each clock cycle, i.e. $D_T=1$

Hogge CDR Loop Dynamics

 

- Replacing the PD & charge pump with their linear model, one can write the expression of the CDR open loop gain:

$$H(s)\Big|_{open} = \frac{\phi_{out}}{\phi_{in}}(s)\Big|_{open} = \frac{I_{cp} D_T}{2\pi} \left(R_p + \frac{1}{sC_p} \right) \frac{K_{VCO}}{s}$$

- Adding a resistor in series with the capacitor adds a zero to the loop gain and helps stabilize the CDR


Hogge CDR Loop Dynamics (Cont'd)

$$H(s)\Big|_{closed} = \frac{\phi_{out}}{\phi_{in}}(s)\Big|_{closed} = \frac{I_{cp} D_T K_{VCO} / 2\pi C_p (1 + s C_p R_p)}{I_{cp} D_T K_{VCO} / 2\pi C_p + I_{cp} D_T K_{VCO} R_p / 2\pi s + s^2}$$

$$\omega_n = \sqrt{\frac{I_{CP} D_T K_{VCO}}{2\pi C_p}}, \quad \zeta = \frac{R_p}{2} \sqrt{\frac{I_{CP} D_T C_p K_{VCO}}{2\pi}}$$


- If the phase of the input data varies slowly ($s \sim 0$) the output phase tracks the input phase with a unity gain
- As the rate of change of the input phase increases the output phase fails to track the input, i.e. CDR will have a LPF response
- As $I_{CP} K_{VCO}$ decreases ζ decreases and stability degrades
- The loop settling time is proportional to $1/(\zeta \omega_n) = 4\pi / R_p I_{CP} D_T K_{VCO}$

Jitter Transfer in CDRs

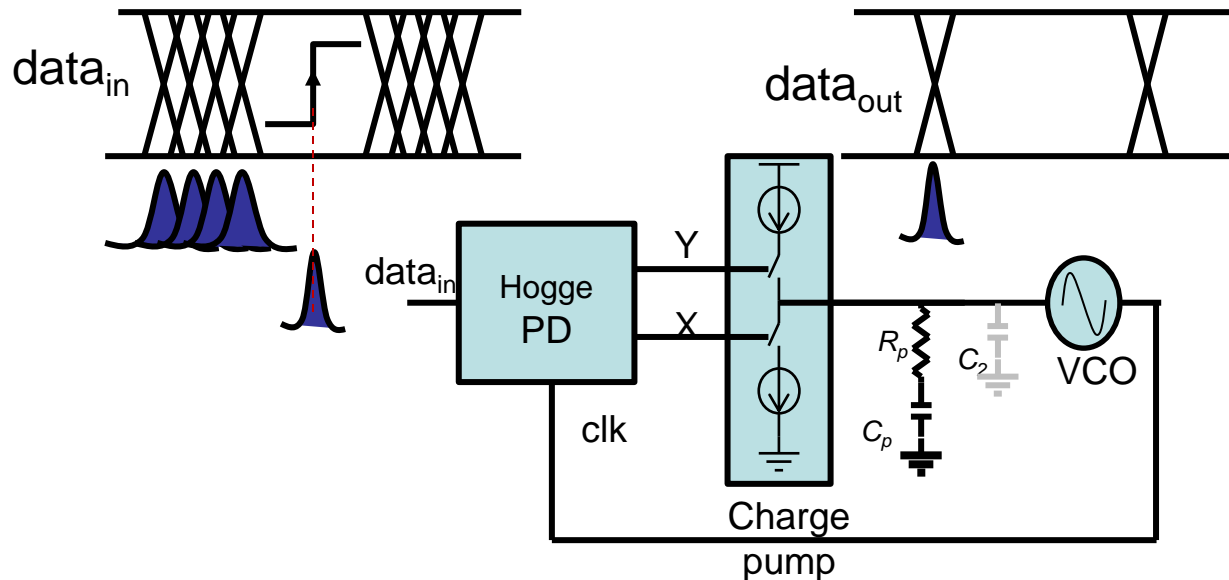

- Jitter Transfer: represents the output jitter as the input jitter is varied at different rates (frequencies) – same as PLL closed loop transfer function
- If the input jitter varies slowly then the output should follow the input to ensure phase locking and reduce bit errors
- If the input jitter varies rapidly the CDR should filter the jitter to avoid having a jittery clock and output eye
- The CDR jitter transfer function exhibits a low pass response (similar to PLLs)

Jitter Transfer in CDRs (Cont'd)

 

- ISI is one of the main sources of high frequency jitter, and should be removed by equalization before clock recovery → CDR can't track it
- SONET OC-192 standard specifies a BW of 120KHz, and requires the jitter peaking to be less than 0.1dB
- Jitter peaking: is defined as the amount of peaking in the jitter transfer function
- Jitter peaking is a very important spec. for repeaters in long-haul networks where 10 or more repeaters may be cascaded to regenerate the signal eliminating the non-idealities of the fiber. This is important to limit the overall system jitter bandwidth

Jitter Transfer in CDRs: Loop BW

$$H(s) = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \longrightarrow \omega_{3dB}^2 = \left(1 + 2\zeta^2 + \sqrt{4 + (1 + 2\zeta^2)^2}\right)\omega_n^2$$


$$\omega_n = \sqrt{\frac{I_{CP}D_T K_{VCO}}{2\pi C_p}}, \quad \zeta = \frac{R_p}{2} \sqrt{\frac{I_{CP}D_T C_p K_{VCO}}{2\pi}}$$

- To achieve a small loop BW ω_n must be decreased without decreasing ζ due to loop stability ($\zeta > 1/\sqrt{2}$ for a critically damped system)
- If ω_n is decreased by via $I_{CP} * K_{VCO}$ the loop stability will also be affected
- C_p is the only parameter that can be used to decrease the loop bandwidth without compromising stability \rightarrow large off chip capacitors can be employed to achieve small loop BWs

Jitter Transfer in CDRs: Loop BW


- For very large loop capacitors, ω_n will be very small and the square term can be neglected
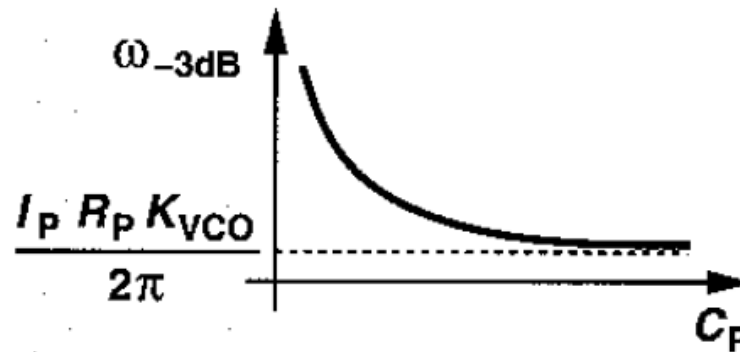
$$H(s) \approx \frac{2\zeta\omega_n}{s + 2\zeta\omega_n} \longrightarrow \omega_{3dB} \approx 2\zeta\omega_n = \frac{R_p I_{CP} D_T K_{VCO}}{2\pi}$$



- This indicates that as the capacitor C_p is increased beyond a certain point the value of ω_{3dB} becomes independent of C_p
- However, this result might be misleading, since in order to reduce the BW further we need to lower R_p which entails a significantly larger C_p in order to keep ζ constant

Jitter Transfer in CDRs: Jitter Peaking

 

$$\omega_z = -\frac{\omega_n}{2\zeta} = -\frac{1}{R_p C_p}$$

- Assuming that $\zeta \gg 1$

$$\omega_{p1} = -\frac{\omega_n}{2\zeta} - \frac{\omega_n}{8\zeta^3}, \omega_{p2} = -2\zeta\omega_n + \frac{\omega_n}{2\zeta} + \frac{\omega_n}{8\zeta^3}$$


$$\omega_{3dB} \approx 2\zeta\omega_n$$

- The zero always appears before the poles inevitably leading to peaking
- The first pole is very close to the zero because $\zeta \gg 1$

$$J_p|_{dB} = 20\log\left(\frac{\omega_{p1}}{\omega_z}\right) \approx 20\log\left(1 + \frac{1}{4\zeta^2}\right)$$


- If R_p is lowered to obtain a smaller loop bandwidth we should increase C_p in order to maintain a constant ζ and J_p

CDR Jitter Transfer/Generation

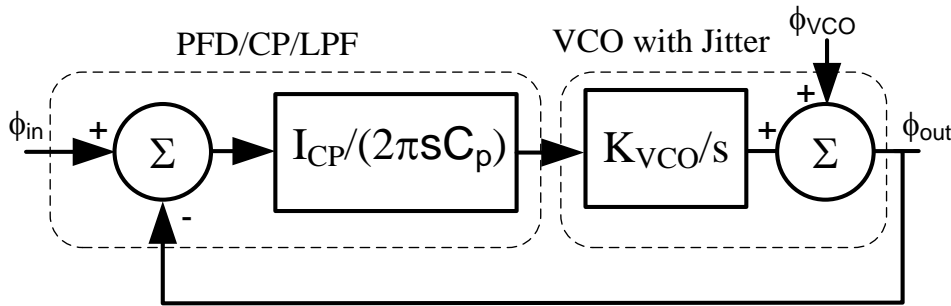



$$\frac{\phi_{out}}{\phi_{in}} = \frac{I_{cp} D_T K_{VCO} / 2\pi C_p (1 + s C_p R_p)}{I_{cp} D_T K_{VCO} / 2\pi C_p + s I_{cp} K_{VCO} R_p / 2\pi + s^2}$$
 
$$\frac{\phi_{out}}{\phi_{VCO}} = \frac{s^2}{K_{VCO} I_{cp} D_T / 2\pi C_p + s K_{VCO} I_{cp} D_T R_p / 2\pi + s^2}$$




- Jitter generation refers to the jitter produced by the CDR itself when the input data contains no input jitter
- The 2 main sources of output jitter are the input and the VCO phase noise ϕ_{VCO}
- The total output jitter is the rms sum of both sources
- The input jitter ϕ_{in} is shaped with the PLL's low pass transfer function
- The VCO phase noise ϕ_{VCO} is shaped with a high pass transfer function

CDR Jitter Transfer/Generation (Cont'd)

  

- Increasing the CDR bandwidth results in integrating more input jitter and less VCO phase noise
- Whereas decreasing the CDR bandwidth results in less input jitter and higher jitter due to VCO phase noise
- A typical CDR design would target the maximum allowable BW by the standard to improve the CDR's jitter tracking capability, and minimize the VCO phase noise impact

CDR Jitter Tolerance

 

- Jitter tolerance: specifies how much jitter a CDR will tolerate for different jitter frequencies without increasing the bit error rate beyond a given limit set by the standard
- At a given jitter frequency, if the error between the input data phase ϕ_{in} and the recovered clock phase ϕ_{out} exceeds $0.5UI$ a sampling error occurs resulting in high BERs

$$\phi_{in} - \phi_{out} < 0.5UI \rightarrow \phi_{in} (1 - H(s)) < 0.5UI \rightarrow \phi_{in} < \frac{0.5UI}{(1 - H(s))}$$


CDR Jitter Tolerance (Cont'd)

- We define $G_{JT}(s)$ as the largest jitter (phase modulation) at the input before the BER start to increase:



$$G_{JT}(s) = \frac{0.5}{1 - H(s)} = \frac{1}{2} \frac{s^2 + 2\zeta\omega_n s + \omega_n^2}{s^2}$$

- G_{JT} has 2 poles at DC and two zeros which co-inside with the poles of $H(s)$ (ω_{p1} and ω_{p2})
- G_{JT} drops with -40dB/dec for $\omega < \omega_{p1}$ then with -20dB/dec for $\omega_{p1} < \omega < \omega_{p2}$, and approaches 0.5 for $\omega > \omega_{p2}$
- For $\zeta \gg 1$ we can approximate the pole locations as:

$$\omega_{p1} \approx -\frac{\omega_n}{2\zeta}, \omega_{p2} \approx -2\zeta\omega_n \longrightarrow |G_{JT}(j\omega_{p1})| \approx 2\sqrt{2}\zeta^2 UI$$

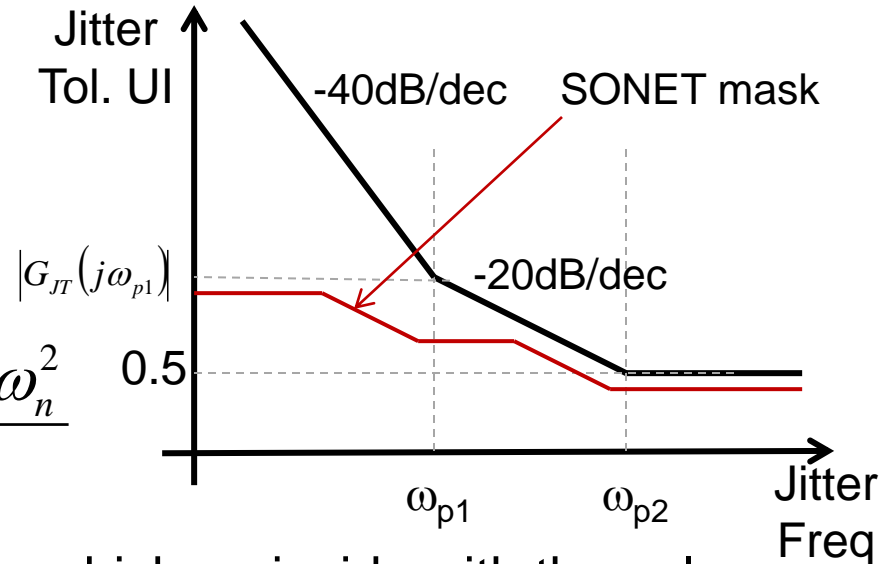

CDR Jitter Tolerance (Cont'd)

  

$$\left| G_{JT}(j\omega_{p1}) \right| \approx 2\sqrt{2}\zeta^2 UI$$

- As ζ increases with a constant ω_n it is easier to meet the jitter tolerance mask (clearing the knee)
- Increasing ω_n with a constant ζ improves the jitter tolerance, but at the same time increases the jitter transfer BW, which might not be desirable for some applications → further jitter filtering using a second PLL can be used

ISSCC 2010: A 12Gb/s 39dB Loss-Recovery Receiver

